

\$19.95 [U.S.]

Price May Vary Outside U.S.

Electronics

Over 750,000 Forrest Mims Fans Can't Be Wrong!

That's right, previous editions of *The Forrest Mims Engineer's Notebook* have sold over 750,000 copies worldwide. Continuing in that winning tradition, this updated edition is a goldmine of integrated circuit applications and ideas!

This isn't like any other book about IC applications. Forrest has carefully hand-drawn and hand-lettered the pages to recreate the "feel" of one of his actual laboratory notebooks. He has built and tested each circuit in this book. Forrest also includes numerous tips on parts substitutions, possible modifications, and circuit operation. The result is a practical, no-nonsense guide based on his years of intensive hands-on experience with IC circuits.

You'll find a wide array of proven circuit designs in this book, ranging from simple digital logic networks and amplifiers to rhythm pattern generators, tone decoders, temperature sensors, digital to analog converters, counters, bus transceivers, and many other useful circuit ideas. Each comes complete with IC pin numbers, values for other components, and supply voltages clearly indicated.

Over the years, *The Forrest Mims Engineer's Notebook* has been an essential reference for professional design engineers, educators, technicians, students, circuit hobbyists, or anyone else who needs concise, accurate information on different chip applications. This is one book that won't sit on the bookshelf—it will find a permanent place next to the logic probe, multimeter, and breadboard in your electronics lab!

LLH
Technology Publishing

Route 2, Box 99M
Eagle Rock, Virginia 24085

ISBN 1-878707-03-5



9 781878 707031

Look for other HighText titles at your favorite book dealer, or write for our latest catalog!

ARCHER®


Cat. No. 276-5002

• Engineer's Notebook II

COMPLETELY
REVISED
&
UPDATED

INTEGRATED
CIRCUIT
APPLICATIONS

Forrest M. Mims III

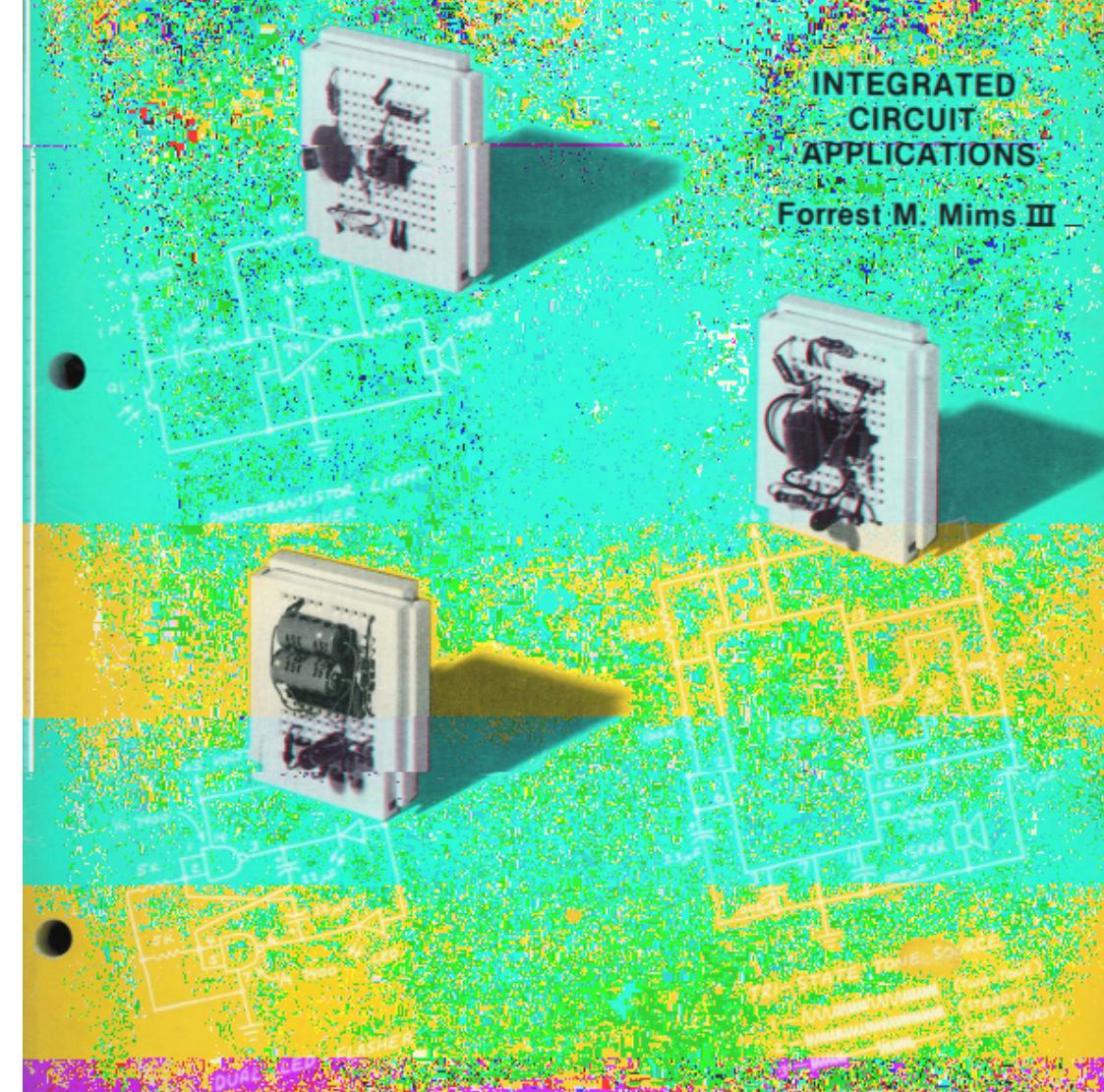

The Forrest Mims Engineer's Notebook

Forrest M. Mims, III



Technology Publishing
Eagle Rock, Virginia

1.5-5 V	91	debouncer	43
5 V line powered	86	touch	9, 114
Preamplifier:		Temperature sensor	134
low-Z	99	Timebase:	
microphone	99	1 Hz	38
Programmable gate	63	10 Hz	38
Programmable light meter	103	60 Hz	38
Pseudorandom voltage generator	79	Timer:	
Public address system	137	digital	38
Pulse delay	27	interval	116
Pulse generator	14, 97, 100, 113, 119	long duration	119
Pulse source	72	programmable count down	74
Pulse width modulator	131	simple	91
Ramp synthesizer	75	two-stage	117
Random number generator	30	ultra-long delay	114
Register	82, 83	with relay	112
Rhythm pattern generator	142-143	0-9 second	34
Sample and hold	98	0-9 second/minute	58
SCR driver	149	Tone burst generator	123
Sequencer:		Tone detector	124
chirp burst	122	Tone sources	10, 55, 116, 130, 133, 139
generator	78	Touch-Tone decoder	126
programmable	118	Touch-Tone generator	127
pseudorandom	36	Toy organ	113
tone	37	Triangle wave generator	14, 115
1 of 4	24	Troubleshooting:	
2 to 8 step	69	CMOS circuits	7
10 note tone	57	TTL/LS circuits	41
Shift register:		TTL interfacing	41
serial in/out, parallel out	24, 69	TTL operating requirements	41
4-bit serial	25, 67	TTL power source	41
Siren	122	Unanimous vote detector	44, 50
Sound generator		VGP page-detector	
"homatron"	149	VHF voltage-regulator	
flanges	245	adjustable	
shake/brush	393	adjustable-negative	
"steam engine"	141	precision-LED	
"ultimate siren"	141	1.2-20_V	
variable	147	1.28-25_V	
square-wave generator	10	2.7_V	
staircase generator	26, 163	3.7-15_V	
stair-step	84	4.7-20_V	
stepper motor	90	5.0_V	
VU-bar-graph display	140	Stepped-tone generator	
Wave-shaper	45	Stepped-wave generator	
XOR gate	13, 32	Storage register	
XOR gate	8, 10, 12	Switch	
		bounceless	1

Data bus, bidirectional	54, 55	octal	63
Data bus control	18	Lamp flasher	104
Data bus selector	62	Latch:	
Data latch	26, 68, 71	gated RS	43, 48
Data register	69	RS	43, 47
Data selector	18, 46, 49, 51, 54	with enable input	51
Decimal to BCD encoder	48	LED bargraph readout	103
Decoder:		LED drivers:	
BCD	16, 44, 48	CMOS	7
1 of 4	16, 17	TTL	41
1 of 8	34	LED flasher	9, 10, 43, 52, 55, 61, 104, 110, 113
8-bit	50	Level detector	93
Delay line	36	Light detector	114
Demultiplexer:		Light probe for the blind	120
1 of 2	53	Light wave receiver	95
1 of 8	37, 60	Logic probe	15
1 to 16	61	Missing pulse detector	64, 113
Differentiator	94	Multiplexer	1 of 8, 37
Dot/bar display driver	106-107, 109	Multivibrator:	
Electronic bell	96	astable	101
Enable input	16	monostable	27, 47, 64, 112, 118
Event failure alarm	120	monostable with tone	115
Expander, universal	53	NAND gate	8, 11, 17, 42, 44, 45, 46, 50
Filter:		NiCad charger	88
bandpass	100	Noise source:	
low pass active	95	pink	39
high pass active	95	white	39
60 Hz notch	95	NOR gate	8, 11, 42, 45, 46, 47
Flip-flop:		Octave synthesizer	146
D	43	Optical power meter	96
toggle	101	OR gate	8, 10, 17, 42, 47, 49
Frequency counter	32	Oscillator:	
Frequency detector	125	audio	53
Frequency divider	31, 115	"chirper"	105
Frequency meter	120	gated	52
Frequency synthesizer	123	light controlled	104
FSK data transmitter	128	phase shift	14
FSK generator	130	square wave	103
Function generator:		sun powered	105
programmable	19	two frequency	125
variable	130	two phase	125
1 kHz three output	97	tunable	122
1.2 kHz pulse/ramp	101	variable square wave	119
Gated threshold detector	52	10 MHz	13
Infrared remote control	124	Oscilloscope, solid state	108
Infrared transmitter	100, 104	Output drive, increasing	9, 10, 15
Infrared voice communicator	99, 121	Output expander	15
Integrator	94	Pattern generator	63
Interfacing:		Peak detector	97, 98
calculator to computer	147	Percussion synthesizer	138
CMOS to CMOS at different voltages	7	Phase detector	12, 65
CMOS to CMOS at lower Vdd	15	Phototransistor receiver	52
CMOS to TTL/LS at lower Vcc	15	Power pulse generator	92
CMOS to TTL/LS at equal Vdd	7	Power supply:	
TTL/LS to CMOS at equal Vdd	7	adjustable negative	87
Inverter	8, 12	programmable	88
Keyboard encoder:			
BCD	29, 31		

Copyright © 1992, 1986, 1982, 1979 by Forrest M. Mims III.
All rights reserved under the United States Copyright Act of 1976.

ISBN: 1-878707-03-5

Library of Congress Catalog Card Number:
U.S. - 1-878707-03-5

Printed in the United States of America

NOTE: No circuit in this book is intended for use in any life-support system, nor in any application in which life or property may be subject to injury. It is your responsibility to determine if use, manufacture, or sale of any device incorporating one or more circuits in this book infringes on any patents, copyrights, or other rights.

HighText is a registered trademark of HighText Publications Inc.

HighText

publications inc.

P.O. Box 1489
Solana Beach, CA 92075

CONTENTS

Foreword	v
Introduction	vii
About the Author	ix
Parts Sources	xi
REVIEWING THE BASICS	1
DIGITAL INTEGRATED CIRCUITS	5
MOS/CMOS Integrated Circuits	6
Gate Packages	8
RAMs (memory chips)	20
Sequential Logic	24
Combinational Logic	34
Timebase	38
Noise Generator	39
TTL/LS Integrated Circuits	41
Gate Packages	42
Combinational Logic	56
Sequential Logic	64
LINEAR INTEGRATED CIRCUITS	85
Voltage Regulators	86
Operational Amplifiers	93
LED Flasher Chip	104
LED Dot/Bar Drivers	106
LCD Clock Module	111
Timers	112
Phase-Locked Loops	121
Pushbutton Tone Module	127
Voltage/Data Conversion	128
Audio Amplifiers	135
Sound Effects Chips	138
Optoisolators	147
Index of Integrated Circuits	152
Index of Circuit Applications	153

AC signal isolator	149	noninverting	102
Adder:		noninverting with hysteresis	102
binary full	12	three-state output	102
half	43	using operational amplifier	93
Alarm clock	111	window	103
Amplifier:		1-bit	12
bridge	94	4-bit	12
clipping	94	8-bit	56
difference	94	Computer output port	148
high gain	135	Control gate	8, 42
inverting	93	Converter:	
linear 10X	14	decimal to BCD	17
noninverting	93	digital to analog	18
programmable gain	19, 98	parallel to serial data	36
single polarity supply	93	voltage to frequency	128
stereo	137	4-bit digital to analog	95
summing	94	8-bit analog to digital	131
unity gain follower	93	8-bit digital to analog	132
4-watt	137	8-bit serial to parallel	79
8-watt	136	Counters:	
10X	101	cascaded BCD	29, 74
16-watt bridge	136	count down from N and recycle	76
20X	135	count to N and halt	30, 34
200X	135	count to N and recycle	30
AND gate	8, 11, 42, 45, 47	count up to N and halt	76
AND-OR gate	11, 42, 45, 46, 51	decade	71
Analog data link	149	decimal	35, 68
Analog data transmission system	129	divide by 2	24, 25, 65, 66
Audible alarm	135	divide by 3	25, 66
Audible light sensor	96	divide by 4	25, 66
Audio frequency meter	129	divide by 5	25, 70, 71
Audio mixer	98	divide by 6	70
Bargraph light meter	96	divide by 7	70, 72
Bargraph generator	78	divide by 8	70
Bass booster	135	divide by 9	70, 72
Binary HI-LO game	56	divide by 10	70, 71, 73
Buffer	11, 45	divide by 11	73
Bus buffer	80	divide by 12	72, 73
Bus register	82, 83	divide by 16	73
Bus transceiver	84	divide by 120	72
Bus transfer:		modulo-8	24, 69
4-bit	80, 81	0-99 two digit	59
8-bit	81	1 of 10 decoded	57
Calculator output port	148	3-digit	32
CMOS interfacing	7	4-bit binary	73
CMOS logic clock	7	4-bit binary up	67
CMOS operating requirements	6	6-digit	33
CMOS power source	6	8-bit	75
Coin tosser	38	14-bit binary	28
Comparator:		Current regulator	86
inverting	101	Dark detector	114
inverting with hysteresis	102		

INTEGRATED CIRCUIT INDEX

TTL/LS		CMOS/MOS		LINEAR	
DEVICE	PAGE	DEVICE	PAGE	DEVICE	PAGE
7400/74LS00	42-44	4001	10	555	112-115
7402/74LS02	47	4011	8-9	556	116-117
7404/74LS04	53	4012	16	558	118-119
7408/74LS08	45	4013	24	565	121
74LS13	52	4017	30-31	566	130
74LS20	48	4020	28	567	124-126
74LS27	49	4021	36	741C	93-96
74LS30	50	4023	17	1458	97
74LS32	46	4027	25	3909	104-105
7441	57	4028	34	7555	120
7447/74LS47	58	4042	26	7805	86
7448	59	4046	122-123	7812	86
74LS51	51	4049	14	7815	86
7473	66	4050	15	7905	87
7474/74LS74	65	4051	37	9400	128-129
7475/74LS75	68	4066	18-19	DAC801	132-133
7476	67	4070	12-13	LF353N	98
74LS85	56	4081	11	LM317	88
7490/74LS90	70	4511	35	LM324N	100
7492	72	4518	29	LM334	134
7493/74LS93	73	4528	27	LM337T	89
74LS123	64	4553	32-33	LM339	102-103
74LS138	60	2102L	20-21	LM350T	92
74LS151	63	2114L	22-23	LM377	137
74LS154	61	CEX-4000	127	LM383	136
74LS157	62	MC14553	32-33	LM386	135
74LS161	75	MM5369	38	LM723	90
74LS164	79	MM5837	39	LM1877	137
74LS175	69	MM5871	142-143	LM3900N	101
74192	74	S2688	39	LM3914N	106-108
74193/74LS193	76	S50240	146	LM3915N	109
74LS194	78			MOC 3010	148
74LS196	71			MOC 5010	149
74LS240	80	NOTE: The Linear		NSM 3916	110
74LS244	81	index includes some		PCIM-161	111
74LS245	84	CMOS/MOS chips.		SAD 1024	144-145
74LS367	54			SCS11C3	148
74LS368	55			SN76477	138-139
74LS373	82			SN76488	140-141
74LS374	83			TDA2002	136
				TIL-111	147
				TIL-119	147
				TL084C	99
				TL431	91
				U507C	121

NOTE: TTL and LS chips are generally interchangeable. LS chips consume less power than TTL equivalents. Use LS chips for battery-powered circuits.

FOREWORD

It's a real shame that the millions who have read Forrest's articles, columns, and books over the years have never had the chance to get to know him personally. I've been lucky enough to be able to call him my friend for several years. This book is special to me because the first edition of this book was the reason why I met and got to know Forrest.

I first met Forrest in 1979. I can't recall the exact date, but it was a fearsomely hot mid-summer day in Fort Worth, Texas. I was working at Radio Shack's national headquarters in their technical publications department. My boss, Dave Gunzel, had spearheaded an effort for Forrest to generate a book of IC applications circuits that were similar to Forrest's actual working laboratory notebooks. Forrest was carefully preparing each page by hand on transparent Mylar sheets using a fine-tip pen. I monitored his progress eagerly, and one day Dave told me that Forrest Mims would be arriving the following week with the last of his Mylar originals.

Wow! I was going to really meet Forrest Mims! I hadn't seen a photo of Forrest before, nor had Dave told me much about how he looked or acted. (In retrospect, I now realize that was deliberate on Dave's part—he wanted me to "discover" Forrest on my own.) I had my own mental picture of Forrest, though. Obviously, a serious fellow. Anyone who came up with all those electronic circuits couldn't have much time for laughter. Probably sharply focused and not interested in anything other than electronics. An older gentleman, certainly, with a white beard and a fondness for jackets with elbow patches. A pipe and slight Germanic accent were also likely. He would probably think I was really stupid and not have a lot of patience with me.


The Big Day quickly arrived. Forrest was due in that afternoon. I had carefully rehearsed my welcoming speech: "Hello, Mr. Mims. It is certainly good to see you. Would you like an ashtray for your pipe?"

I was alone in the technical publications office that afternoon when someone I didn't recognize stuck his head into the office doorway. He was wearing normal business attire, smiled easily, spoke with a slight Texas accent, and was looking for Dave Gunzel. Oh brother! I thought, another new employee who's lost it. Tandy Center... Doesn't this guy know that Forrest Mims is going to show up this afternoon and I don't have any time to waste on him???. I mumbled something about Dave being gone for a few minutes and that we were expecting a visitor later that afternoon.

The stranger seemed apologetic. He didn't want to waste any of my time or Dave's if we were expecting someone important; he said, he just needed to tend to a couple of matters quickly and wouldn't bother us.

OPTOCOUPLER MOC5010 LINEAR AMPLIFIER

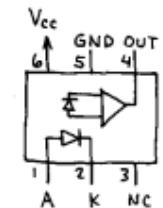CONVERTS CURRENT FLOW THROUGH LED INTO OUTPUT VOLTAGE.
IDEAL FOR TELEPHONE LINE COUPLING AND VARIOUS AUDIO APPLICATIONS.



any further. He approached my desk and extended his hand toward me.

"Hi," he said, "I'm Forrest Mims; you must be Harry."

I don't recall my reply, but I think it was the unmistakable sound of self-mortification.

Forrest had work to do and wondered if I could help. He needed to spray the Mylar sheets with a protective coating before turning them over to us for printing. We commandeered a vacant area of the then-new Tandy Center, spread out the Mylar sheets, and spent the next couple of hours emptying aerosol cans of clear lacquer while discussing the state of the universe.


That afternoon, I discovered what a remarkably unpretentious guy Forrest is. Here was one guy who had earned the right to a massive ego, yet he was straightforward, down to Earth, and almost skeptical of his achievements. Our conversation ranged from electronics to lasers to politics to Texas history to computers to religion to . . . well, you name it. It was incredible how many subjects Forrest was interested in, and how insatiable his curiosity was about everything in the natural world. By the end of that afternoon, I felt as if I had known Forrest for years.

A lot has happened since then. I eventually left Texas to become a book editor in New York and, a few years after that, moved to California where I became a founding partner in HighText Publications. Throughout, Forrest remained a valued friend and trusted confidant. The intelligence and insight that are apparent in his circuits extends to many other areas, and he has a wit and sense of irony that are delicious. While we don't get to spend much time physically in each other's company, it's a rare week when we don't have at least two or three lengthy telephone conversations. As technology has advanced, so have our modes of interaction; we often exchange a couple of faxes per day on various subjects.


We had no idea that the book we worked on back on that hot summer afternoon in 1979 would go on to sell over 750,000 copies in its various editions. Some of the pages we worked on back in 1979 appear in this book, a testimony to the enduring quality and relevance of Forrest's work. For readers such as yourself, this book will be a valuable reference to contemporary, real-world IC applications. For me, it brings back a lot of good memories. And, no, Forrest doesn't smoke a pipe; doesn't wear jackets with elbow patches; and doesn't have a beard.

Harry L. Helms


ISOLATED ANALOG DATA LINK

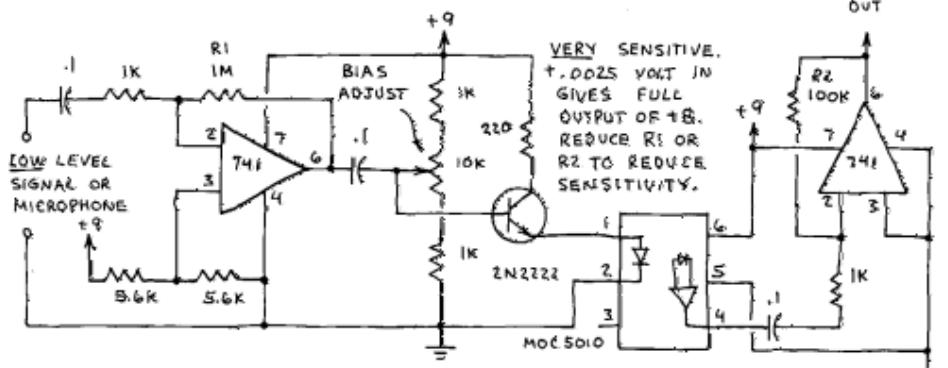


SCR DRIVER

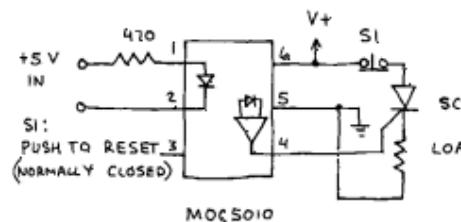

TTL INTERFACING

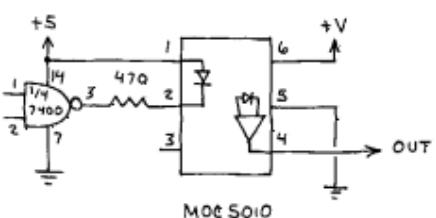

AC SIGNAL ISOLATOR

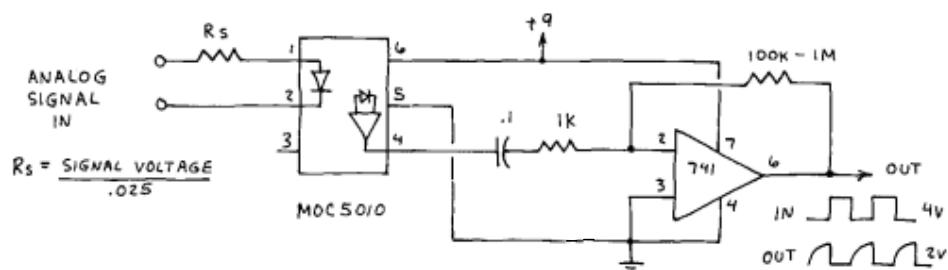


OPTOCOUPERS

MOC3010 - SCR


SCS11C3 - TRIAC

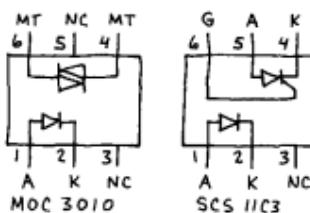INFRARED LED SWITCHES
TRIAC (MOC3010) OR SCR
(SCS11C3). MOC3010 WILL
SWITCH 120 VOLTS AC AT
100 mA. SCS11C3 WILL
SWITCH 200 VOLTS DC AT
300 mA.



CALCULATOR OUTPUT PORTS


SCR (DC) PORT

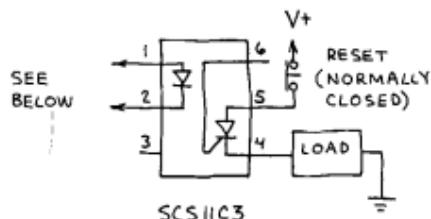

CONNECT PINS 1 AND 2 TO DECIMAL POINT OF LOWEST ORDER READOUT DIGIT. BE SURE TO OBSERVE POLARITY. USE ONLY WITH CALCULATOR HAVING LED READOUT. TYPICAL OPERATION: KEY IN NUMBER WHICH PLACES DECIMAL ANYWHERE BUT FINAL DIGIT. THEN PRESS $\boxed{-}$ $\boxed{1}$ $\boxed{.}$ $\boxed{0}$. NUMBER IN DISPLAY WILL BE DECREMENTED EACH TIME $\boxed{-}$ IS PRESSED. WHEN COUNT REACHES 0, DECIMAL MOVES TO LAST DIGIT AND ACTUATES OUTPUT PORT. FOR MORE INFORMATION SEE POPULAR ELECTRONICS, DEC. 1979 (PP. 86-87).


SOME CALCULATORS WILL REQUIRE DIFFERENT KEYSTROKE SEQUENCE.
IMPORTANT: THESE CIRCUITS MAY VOID THE WARRANTY OF YOUR CALCULATOR OR COMPUTER. FOLLOW MOS HANDLING PROCEDURES TO AVOID DAMAGING CALCULATOR OR COMPUTER PORTS DESIGNED TO INTERFACE WITH TTL OR RS-232-C BUSINESSES.

TRIAC (AC) PORT

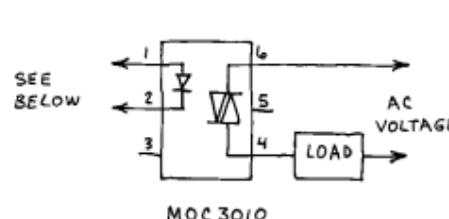


THE LOAD FOR ALL THESE CIRCUITS MAY BE LAMP, MOTOR OR OTHER DEVICE WHICH DOES NOT EXCEED RATING OF OPTOCOUPLER.

COMPUTER OUTPUT PORTS

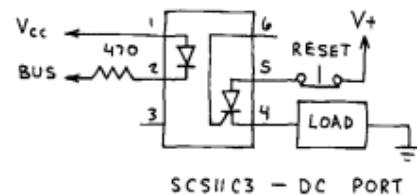

SCS11C3 - DC PORT

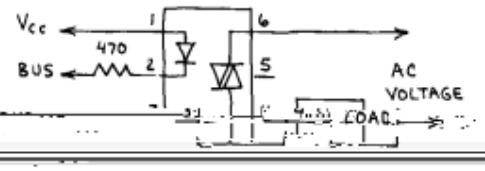

MOC3010 - AC PORT

INTRODUCTION

Since my student days at Texas A&M University I have kept a series of laboratory notebooks. In these notebooks I record details about experiments, measurements, and new ideas. Also included are many electronic circuit diagrams. Dave Gunzel, formerly the director of technical publications at Radio Shack, took an interest in my notebooks in the mid-1970s and suggested that Radio Shack might someday want to publish a book of electronic circuits based on their hand-drawn format. Several years later, Radio Shack assigned me to produce Engineer's Notebook, a 128-page book of electronic circuits. The book soon became a Radio Shack bestseller. As new integrated circuits were added to Radio Shack's product line and others were dropped, I revised the book as necessary. Later, Radio Shack authorized me to do an edition of the book for McGraw-Hill.

This revised edition for HighText Publications represents the best and most interesting circuits from all previous editions.

The integrated circuits described in this book remain among the most popular ever introduced. Most of them are readily available from Radio Shack, electronics parts suppliers, and mail-order dealers. Magazines such as Radio-Electronics carry ads from mail-order IC dealers. A few of the chips are specialized and finding sources for them may be more difficult. Four of the devices—the CEX-4000, S50240, PCIM-161, and SAD-1024—may be available only from dealers in surplus and discontinued ICs. However, the overwhelming majority of chips described in this book are readily available from many different sources. In fact, prices for some of the more common devices have fallen substantially since the first edition of this book. Some are available today for pennies!

Most of the part numbers given for the integrated circuits in this book are generic, and various manufacturers may add additional letters or numbers or even use a completely different number. For example, the 4011 is a quad of CMOS NAND gates. An "A" suffix (4011A) means this chip can operate from a 3- to 12-volt supply. A "B" suffix (4011B) means the chip can operate from a 3- to 18-volt supply. The high-voltage version of the chip is by far the most common. National Semiconductor adds a CD prefix to its versions of the 4011B (CD4011B), while Motorola adds an MC prefix (MC4011B). Nevertheless, both chips are functionally identical.

For additional information about chip identification and specifications, see the data books published by the various integrated circuit manufacturers. These books are available directly from manufacturers of integrated circuits and from industrial supply companies that represent integrated circuit manufacturers. They are also available from some mail-order electronics parts dealers.

Forrest M. Mims II

ABOUT THE AUTHOR

Forrest Mims has been an electronics hobbyist since building a one-tube radio kit at the age of 11. Following graduation from Texas A&M University in 1966 and service as a photointelligence officer in Vietnam, he worked for three years with high-powered lasers, solid-state instrumentation, and trained monkeys with the Air Force Weapons Laboratory in New Mexico. Since becoming a full-time writer in 1970, he's written several hundred magazine articles and scholarly papers. His articles and columns have appeared in virtually every significant electronics magazine, including *Popular Electronics*, *Radio-Electronics*, and *Modern Electronics*. His articles on other scientific topics have appeared in a wide range of other publications, including *National Geographic World*, *Science Digest*, *Highlights for Children*, and *Scientific American*. His editorial exploits have included an assignment from the *National Enquirer* to evaluate the feasibility of eavesdropping on Howard Hughes by laser (it was possible, but Forrest declined to take part) and getting dropped by *Scientific American* as their "The Amateur Scientist" columnist because he admitted to the magazine's editors that he was a born-again Christian. His book sales total in the millions, and he is likely the most widely-read electronics writer in the world.


Forrest is currently busy as the founding editor of *Science PROBE!*, a new magazine aimed at amateur scientists. In this role, Forrest is creating the sort of magazine that he wishes had been available in his youth while acquiring a new understanding of the frustrations of being an editor. He still keeps up a hectic pace of electronics and science experimentation and writing.

Forrest and his wife Minnie have three children, and they currently live in the Texas countryside near San Antonio. They are active in church activities, and Forrest is a Baptist deacon. He has his office and electronics lab in an old restored farmhouse adjacent to his home.

OPTOCOUPLED DEVICES


TIL 111 - PHOTOTRANSISTOR TIL 119 - PHOTODARLINGTON

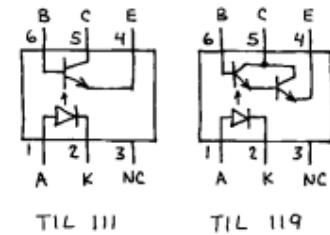INFRARED LED TURNS ON PHOTOTRANSISTOR WHEN LED IS FORWARD BIASED. USE TO REDUCE ELECTRICAL NOISE AND SHOCK HAZARD. IDEAL FOR ISOLATING AND INTERFACING MICROCOMPUTER BUS LINES.




USE TIL 119 WHEN INPUT SIGNAL IS SMALL.

TIL 111 / TIL 119 TEST CIRCUIT

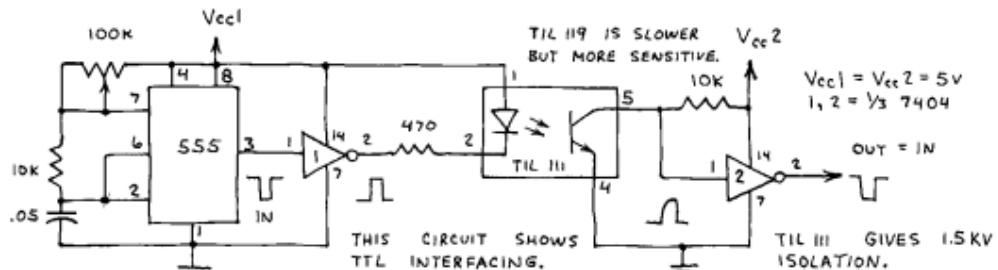


CALCULATOR / COMPUTER INTERFACING

KEYBOARD INPUT

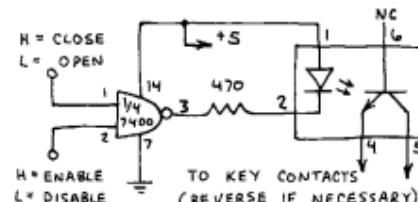

IMPORTANT: THESE CIRCUITS MAY VOID YOUR CALCULATOR'S WARRANTY. I HAVE USED BOTH WITH A LOW COST CALCULATOR WITH LED READOUT. SEE *POPULAR ELECTRONICS*, DEC 1979 (PP. BS-87) FOR DETAILS. ALWAYS FOLLOW MOS HANDLING PROCEDURES WHEN WORKING WITH CALCULATORS! IF NOT, YOU MAY DAMAGE THE UNIT'S PROCESSING CHIP.

CALCULATOR TIMER

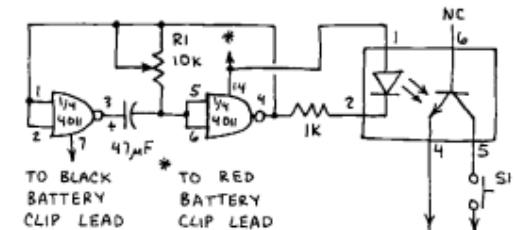

TOP OCTAVE SYNTHESIZER S50240

THIS PMOS CHIP ACCEPTS AN INPUT FREQUENCY (ϕ), AND THEN DIVIDES IT INTO A FULL OCTAVE PLUS ONE NOTE ON THE EQUALY TEMPERED SCALE. THIS CHIP IS IDEAL FOR MUSIC SYNTHESIZERS, ORGANS, ETC. FOR TOP OCTAVE OPERATION, ϕ SHOULD BE 2.00024 MHZ; LOWER FREQUENCIES GIVE LOWER OCTAVES.

$\frac{1}{478} \frac{1}{239} \frac{1}{253} \frac{1}{268} \frac{1}{284} \frac{1}{301} \frac{1}{319} \frac{1}{338}$
16| 15| 14| 13| 12| 11| 10| 9|


NOTE:
CHIP NUMBER 8

PMOS BEING INVERTER.


1 2 3 4 5 6 7 8
TUNING ϕ GND

HSL 426 402-379-358

ADJUSTABLE OCTAVE SYNTHESIZER

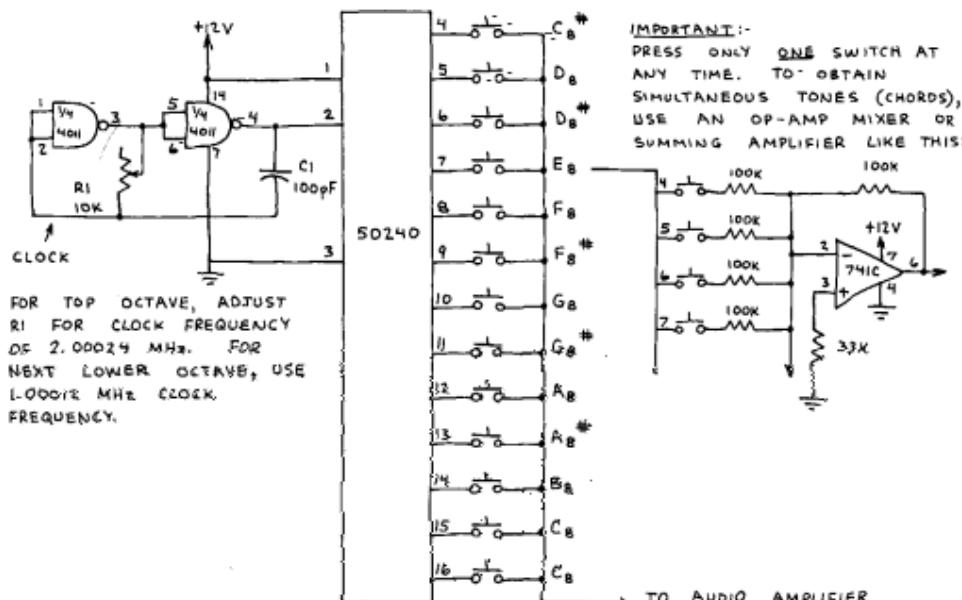

SPECIAL EFFECTS

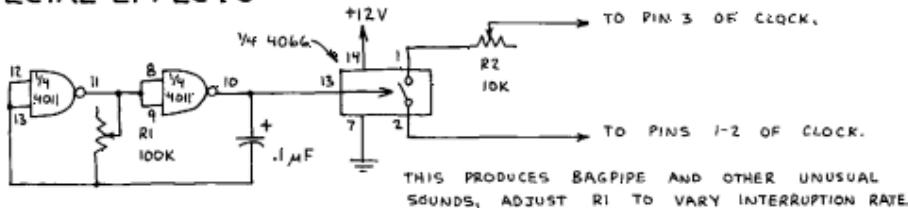

PARTS SOURCES

The chips and related components (resistors, capacitors, etc.) used in this book are available from a variety of sources, including electronics stores (such as Dick Smith Electronics in Australia and David Reid stores in New Zealand), advertisers in electronics magazines, and industrial electronics suppliers. Some chips—such as the SN76477N, SN76488N, and SAD-1024A—are a bit "rarer" and you may have to look for them at companies specializing in surplus and discontinued devices.

Manufacturers of integrated circuits publish "data sheets" giving the bare-bones specifications for a chip and "applications notes" that give additional information, including circuit schematics using the chip. These can be obtained by contacting the national headquarters of the chip manufacturer or their nearest sales office.


The manufacturer of an integrated circuit is identified by a prefix in front of the actual part number. For example, "LM741" and "MC741" would both indicate the device was the common 741 operational amplifier found on pages 93 to 96 of this book. However, the "LM" would indicate the device was manufactured by National Semiconductor while the "MC" would denote a device manufactured by Motorola. Here are some common prefixes and manufacturers:

AD	Analog Devices	M	Mitsubishi
Am	Advanced Micro Devices	MB	Fujitsu
Bx	Sony	MC	Motorola
CA	RCA (now Harris)	MM	Motorola
CD	RCA (now Harris)	NE	Signetics
Cx	Sony	PM	Precision Monolithics
DM	National Semiconductor	T	Toshiba
F	Fairchild (now National Semiconductor)	TL	Texas Instruments
FSS	Ferranti	TMS	Texas Instruments
HA	Harris	XR	Exar
HA	Hitachi	μ PB	NEC
HD	Hitachi		
HG	Hitachi		
HI	Harris		
IR	Sharp		
KA	Samsung		
LF	National Semiconductor		
LM	National Semiconductor		
LT	Linear Technology		

NOTES


DUAL ANALOG DELAY LINE (CONTINUED) SAD-1024A

ADJUSTABLE FLANGER OR PHASER

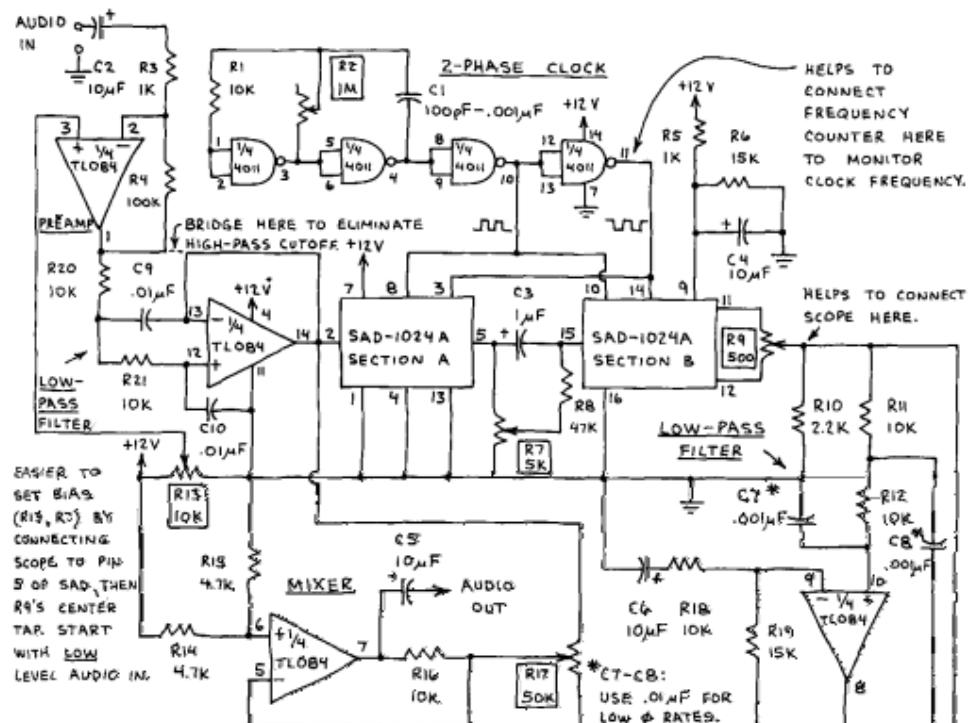

ADJUST CIRCUIT FOR DESIRED EFFECT BY CONNECTING TRANSISTOR RADIO TO AUDIO INPUT. TUNE RADIO TO A TALK SHOW FOR BEST RESULTS. R13 AND R7 CONTROL BIAS TO SECTIONS A AND B OF THE SAD. R9 BALANCES THE SAD OUTPUTS. R2 CONTROLS THE CLOCK RATE. R17 IS THE MAIN BALANCE CONTROL. IT CONTROLS THE RELATIVE AMPLITUDES OF THE ORIGINAL AND DELAYED SIGNAL APPLIED TO THE MIXER. CONNECT THE OUTPUT TO A POWER AMPLIFIER. YOU MUST ADJUST BIAS CONTROLS PROPERLY FOR BEST RESULTS. SET R2 FOR LOW FREQUENCIES (3-8KHz) FOR SINGLE ECHO. USE HIGHER CLOCK FREQUENCIES (20-100KHz) FOR HOLLOW, SWISHY SOUNDS. NOTE: THIS CIRCUIT IS NOT FOR BEGINNERS.

REVERBERATOR

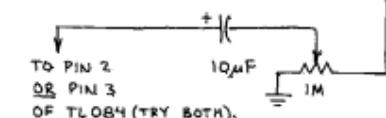


ADD THIS FEEDBACK CIRCUIT FOR UNUSUAL REVERBERATION EFFECTS. SLOW CLOCK FREQUENCIES GIVE MOST STRIKING REVERBERATIONS. TRY 5-20 KHz. FASTER CLOCK (20-100 KHz) AND CAREFUL ADJUSTMENT GIVES ROBOT-LIKE SOUND USED IN SOME SCIENCE FICTION MOVIES.



DUAL ANALOG DELAY LINE SAD-1024A

CONTAINS TWO INDEPENDENT 512 STAGE SERIAL ANALOG DELAY (SAD) LINES (ALSO CALLED ANALOG SHIFT REGISTERS). OK TO USE EACH 512 STAGE SAD SEPARATELY OR IN SERIES. ANALOG DELAYS OF UP TO $\frac{1}{2}$ SECOND CAN BE ACHIEVED. A 2-PHASE CLOCK IS REQUIRED TO DRIVE INPUTS ϕ_1 AND ϕ_2 . INPUT DATA RIDES THROUGH THE SAD ON ALTERNATING CLOCK PULSES AND APPEAR AT THE TWO OUTPUTS AFTER PASSING THROUGH ALL 512 STAGES. CONNECT V_{bb} TO V_{dd} (PIN 7) OR, FOR OPTIMUM RESULTS, TO 1 VOLT BELOW V_{dd} . THIS CHIP CAN BE TRICKY TO USE SINCE SEVERAL EXTERNAL ADJUSTMENTS ARE REQUIRED. CIRCUITS ON THIS PAGE EXPLAIN OPERATING REQUIREMENTS WHILE A COMPLETE CIRCUIT IS SHOWN ON FACING PAGE.

SAD IN/OUT CONTROLS

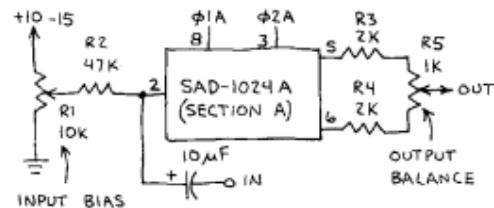


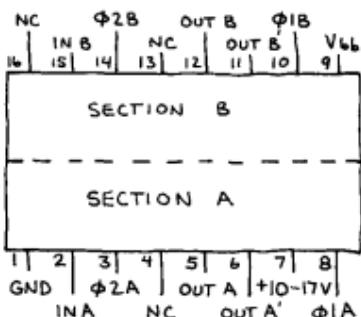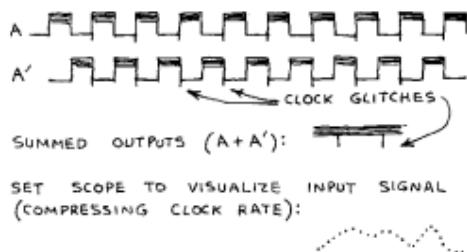ADJUST R_1 (INPUT BIAS) FOR OPTIMUM AUDIO OUTPUT. OUTPUTS APPEAR LIKE THIS ON A SCOPE:




CAUTION: THIS NMOS CHIP IS VULNERABLE TO DAMAGE FROM STATIC DISCHARGE! FOLLOW CMOS HANDLING PROCEDURES.

SERIAL OPERATION

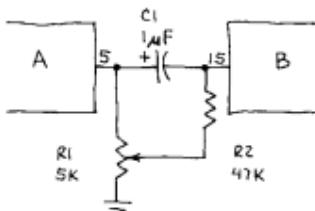

R_1 CONTROLS BIAS TO SECTION B. NOTE THAT ONLY ONE OUTPUT OF A IS CONNECTED TO INPUT OF B.

OUTPUT SUMMER

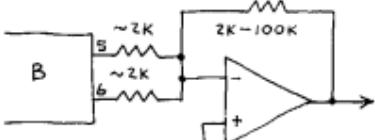

ANY OP-AMP CAN BE USED, BUT LOW NOISE FET INPUT TYPES ARE BEST.

REVIEWING THE BASICS

INTRODUCTION

"Can I use a $0.22 \mu F$ capacitor instead of a $0.01 \mu F$ unit?"

"Is it okay to substitute a 12,000 ohm resistor for a 10,000 ohm unit?"

This section will tackle these common questions and many others. Master them, and you will be well prepared to tackle the circuits in this book.

RESISTORS

Resistors limit the flow of electrical current. A resistor has a resistance (R) of 1 ohm if a current (I) of 1 ampere flows through it when a potential difference (E) of 1 volt is placed across it. In other words:

$$R = \frac{E}{I} \quad (\text{or}) \quad I = \frac{E}{R} \quad (\text{or}) \quad E = IR$$

These handy formulas form Ohm's law. Memorize them. You will use them often.

Resistors are identified by a color code:



COLOR	1	2	3 (Multiplier)
BLACK	0	0	1
BROWN	1	1	10
RED	2	2	100
ORANGE	3	3	1,000
YELLOW	4	4	10,000
GREEN	5	5	100,000
BLUE	6	6	1,000,000
VIOLET	7	7	10,000,000
GRAY	8	8	100,000,000
WHITE	9	9	(none)

A fourth color band may be present. It specifies the tolerance of the resistor. Gold is $\pm 5\%$ and silver is $\pm 10\%$. No fourth band means $\pm 20\%$.

Since no resistor has a perfect tolerance, it's often okay to substitute resistors. For example, it's almost always okay to use a 1.8k resistor in place of a 2k unit... Just try to stay within $\pm 20\%$ of the specified value.


What does K mean? It's short for 1,000. 20K means $20 \times 1,000$ or 20,000 ohms. M is short for meg-ohm or $1,000,000$ ohms. Therefore a 2.2M resistor has a resistance of 2,200,000 ohms.

Resistors which resist lots of current must be able to dissipate the heat that's produced. Always use resistors with the specified power rating. No power rating specified? Then it's usually okay to use 1/4 or 1/2 watt units.

Almost every electronic circuit uses resistors. Here are three of the most important applications for resistors:

1. Limit current to LEDs, transistors, speakers, etc.


2. Voltage division. For instance:

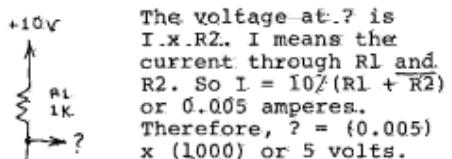


The voltage at $?$ is $I \times R_2$. I means the current through R_1 and R_2 . So $I = 10 / (R_1 + R_2)$ or 0.005 amperes. Therefore, $? = 0.005 \times 1000$ or 5 volts.

Note that the total resistance of R_1 and R_2 is simply $R_1 + R_2$. This rule provides a handy trick for making custom resistances.

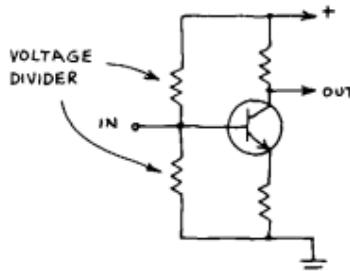Voltage dividers are used to bias transistors:



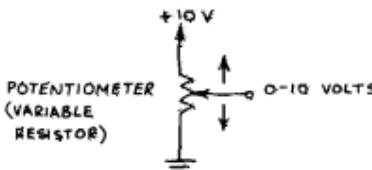They're also a convenient source of variable voltage:



And they're useful in voltage sensing circuits. See the comparator circuits in this notebook.

3. They control the charging time of capacitors. Read on...

CAPACITORS

Capacitors store electrical energy and block the flow of direct current while passing alternating current. Capacitance is specified in farads. One farad represents a huge capacitance so most capacitors have values of small fractions of a farad:

$$1 \text{ microfarad } (\mu\text{F}) = 10^{-6} \text{ farad}$$

$$1 \text{ picofarad } (\text{pF}) = 10^{-12} \text{ farad}$$


$$\text{or}$$

$$1 \mu\text{F} = 1,000,000 \text{ pF}$$

The value of a capacitor is usually printed on the component. The μF and pF designations may not be present. Small ones marked 1-1000 are rated in μF ; larger ones

marked .001-1000 are rated in μF .

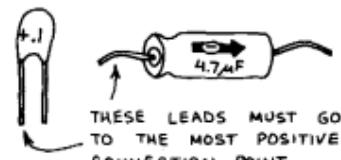Electrolytic capacitors provide high capacity in a small space. Their leads are polarized and must be connected into a circuit in the proper direction.




Capacitors have a voltage rating. It's usually printed under the capacity marking. The voltage rating must be higher than the highest expected voltage (usually the power supply voltage).

Caution: A capacitor can store a charge for a considerable time after power is removed. This charge can be dangerous! A large electrolytic capacitor charged to only 5 or 10 volts can melt the tip of a screwdriver placed across its leads! High voltage capacitors can store a lethal charge! Discharge a capacitor by carefully placing a resistor (1K or more; use Ohm's law) across its leads. Use only one hand to prevent touching both leads of the capacitor.

Important capacitor applications:

1. Remove power supply spikes. (Place 0.01-0.1 μF across power supply pins of digital ICs. Stops false triggering.)

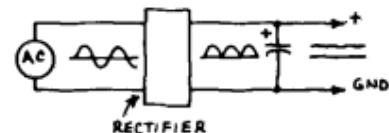2. Smooth rectified AC voltage into steady DC voltage. (Place 100-10,000 μF across rectifier output.)




RHYTHM PATTERN GENERATOR (CONTINUED)

MM5871


PERCUSSION SYNTHESIZERS:

OK TO TUNE BY MAKING SLIGHT CHANGES TO RC COMPONENTS.


BASS DRUM

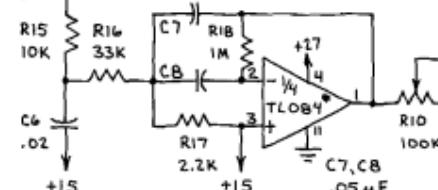


BLOCK

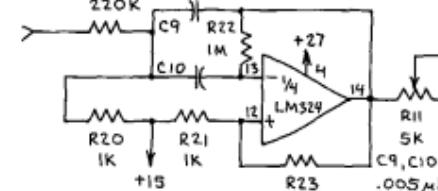


BONGO

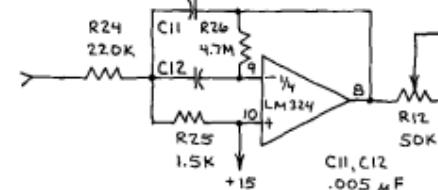

SNARE

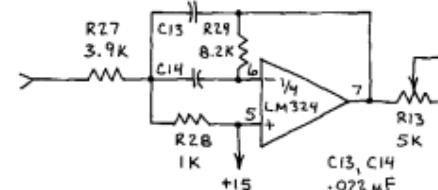

BRUSH

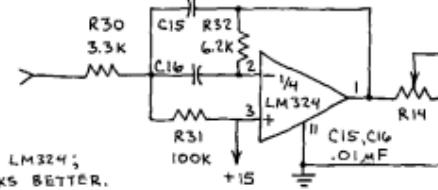

* OK TO USE LM324; TL084 WORKS BETTER.

MM5871 PIN EXPLANATIONS:

- 1 - V_{GG} (-27V \pm 2V)
- 2 - TEMPO CONTROL (RC NETWORK)
- 3 - TRIGGER OUTPUT PULSE WIDTH CONTROL (RC NETWORK)
- 4 - V_{pp} (-14V \pm 2V)
- 5 - V_{ss} (0V)

PATTERN SELECT INPUTS -

- 6 - ROCK 8 - MARCH 15 - C/W
- 7 - LATIN 14 - WALTZ 16 - SWING


TRIGGER OUTPUTS -

- 9 - BASS 11 - BONGO 13 - SNARE
- 10 - BLOCK 12 - BRUSH


RHYTHM BOX OPERATION:

POTS R10-R14 CONTROL VOLUME OF EACH INSTRUMENT. EXPERIMENT WITH SETTINGS FOR BEST RESULTS. OK TO SELECT TWO OR MORE PATTERNS SIMULTANEOUSLY!

SUMMING AMPLIFIER / PREAMPLIFIER

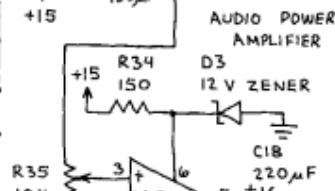



B/L SPKR

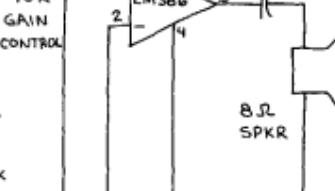

RHYTHM PATTERN GENERATOR MM5871

PRODUCES SIX DIFFERENT RHYTHM PATTERNS AND TRIGGERS FIVE DIFFERENT INSTRUMENTS. ADJUSTABLE TEMPO. COMPlicated TO USE, BUT WELL WORTH THE EFFORT.

RHYTHM BOX

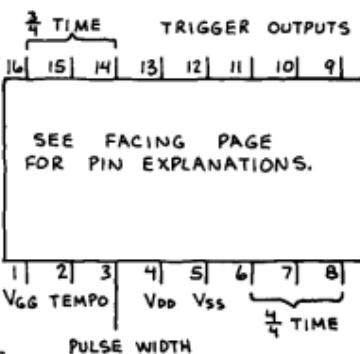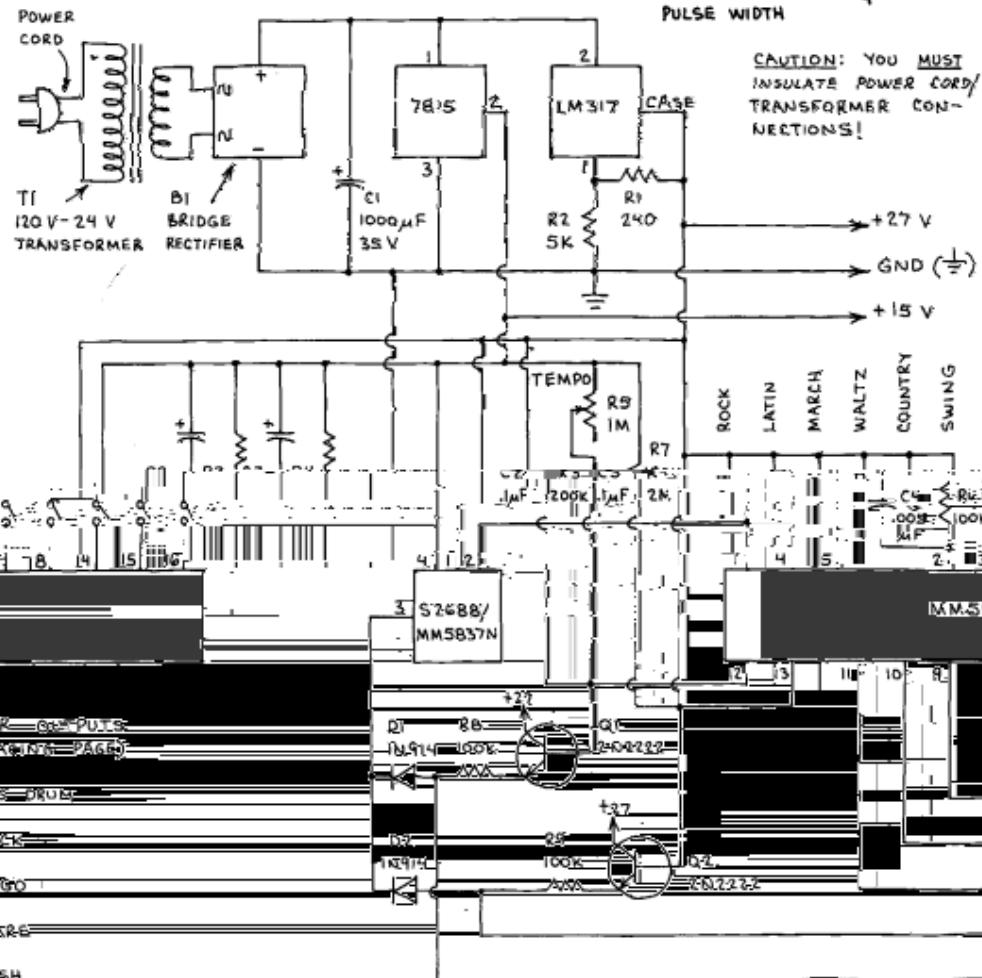

3. Block DC signal while passing AC signal.

4. Bypass AC signal around a circuit or to ground.

5. Filter out unwanted portions of a fluctuating signal.

SEMICONDUCTORS

Usually made from silicon. Be sure to observe all operating restrictions. Brief descriptions of important semiconductor devices:


DIODES

Let current to flow in but one direction (forward bias). Used to rectify AC, allow current to enter a circuit but block its return, etc.


grate a fluctuating signal:



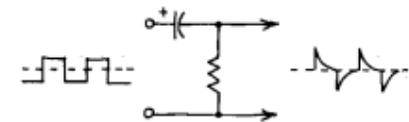7. Or-to differentiate a fluctuating signal:



8. Perform a timing function:

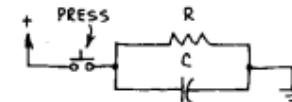

C will quickly charge...then slowly discharge through R.

9. Store a charge to keep a transistor turned off or on.


10. Store a charge to be dumped through a flashtube or LED in a fast and powerful pulse.

Can you substitute capacitors? In most cases changing the value of a capacitor 10% or even 100% will not cause a malfunction, but circuit operation may be affected. In a timing circuit, for example, increasing the value of the timing capacitor will increase the timing period.

Changing the capacitors in a filter will change the filter's frequency response. Be sure to use the proper voltage rating. And don't worry about the difference between 0.47 and 0.5 μF.

ZENER DIODES

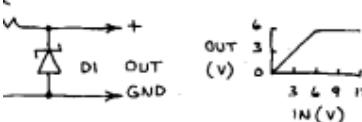Zener diode is a voltage regulator. In this typical circuit, any exceeding the diode's breakdown voltage is shunted to ground:



6 VOLT ZENER DIODE
rs can also protect voltage sensitive components and provide convenient reference voltage.

LIGHT EMITTING DIODES

emit green, yellow, red or infrared when forward biased. A series resistor should be used to limit current to less than the maximum allowed:

$$R_s = \frac{V_{cc} - V_{LED}}{I_{LED}}$$

Example: V_{LED} of red LED is 1.7 volts. For a forward current (I_{LED}) of 20 mA at $V_{cc} = 5$ volts, $R_s = 165$ ohms. Don't exceed I_{LED} !!


Infrared LEDs are much more powerful than visible LEDs, but their radiation is totally invisible. Use them for object detectors and communicators.

TRANSISTORS


In this notebook, transistors are used as simple amplifiers and switches that turn on LEDs. Any general purpose switching transistors will work.

INTEGRATED CIRCUITS

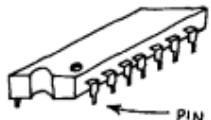
Since an IC is a complete circuit on a silicon chip, you must observe all operating restrictions. Reversed polarity, excessive supply voltage and sourcing or sinking too much current can destroy an IC. Be sure to pay close attention to the location of the power supply pins! Most ICs are packaged in 8, 14 or 16 pin plastic DIPs (Dual In-line Packages). A notch or circle is near pin 1:



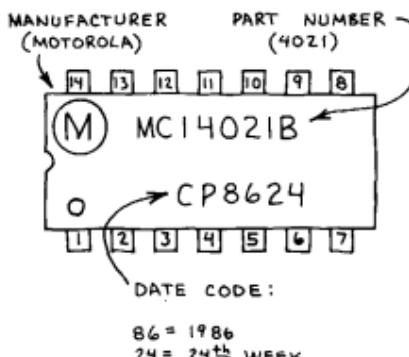When the IC is right side up, pin 1 is at lower left:



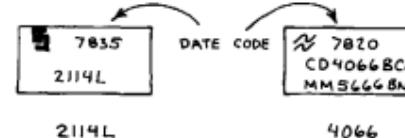
Incidentally, a date code may not be present, but other numbers may be...and the date code is not always below the device number:




Store ICs in a plastic cabinet if you can afford one. Or insert them in rows in a styrofoam tray (the kind used for meat in a grocery store). CAUTION: Never store MOS/CMOS ICs in ordinary non-conductive plastic.

COMPLEX SOUND GENERATOR (CONTINUED) SN76488N

IMPROVED STEAM ENGINE AND WHISTLE

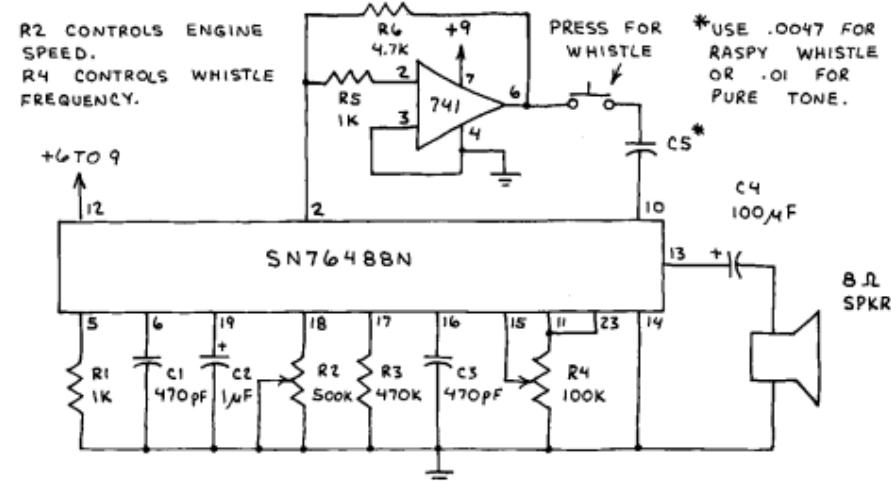

THE ULTIMATE SIREN

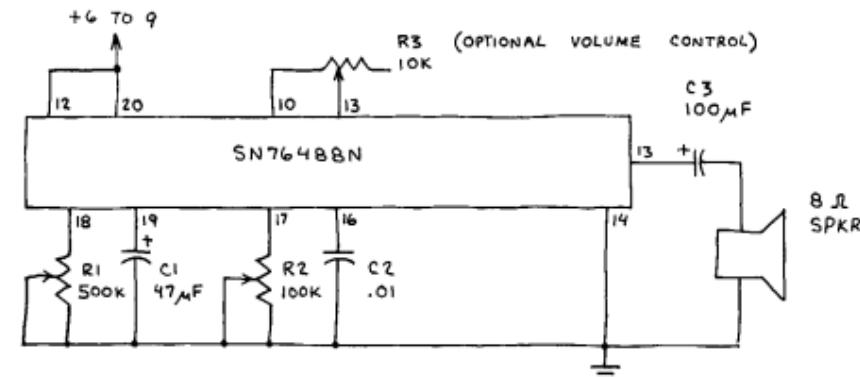

R1 CONTROLS CYCLE RATE.
R2 CONTROLS FREQUENCY.


ADJUST R1 FOR HIGH RESISTANCE TO GIVE
ULTRA SLOW SIREN.

COMPLEX SOUND GENERATOR SN76488N


MODIFIED VERSION
OF SN76477N.
INCLUDES BUILT-IN
AMPLIFIER FOR
DIRECT SPEAKER
DRIVE. NOTE
THAT SN76488N
AND SN76477N
HAVE DIFFERENT
PINOUTS

MANY DIFFERENT
SOUNDS CAN BE
CREATED. FOR
BEST RESULTS,
STUDY CAREFULLY
THE TECHNICAL
DATA SUPPLIED
WITH CHIP.

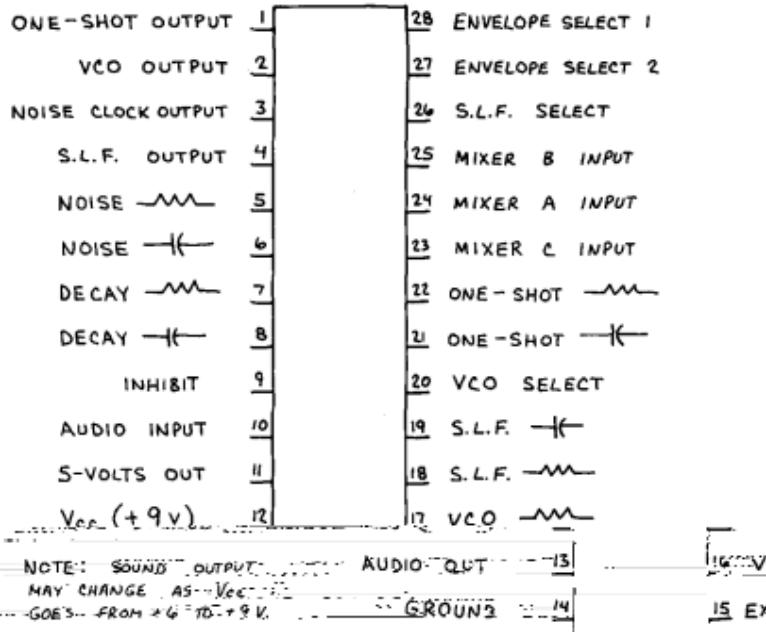VERY EASY TO
DEVISE YOUR OWN
UNIQUE SOUNDS!



BOMB-DROP PLUS EXPLOSION

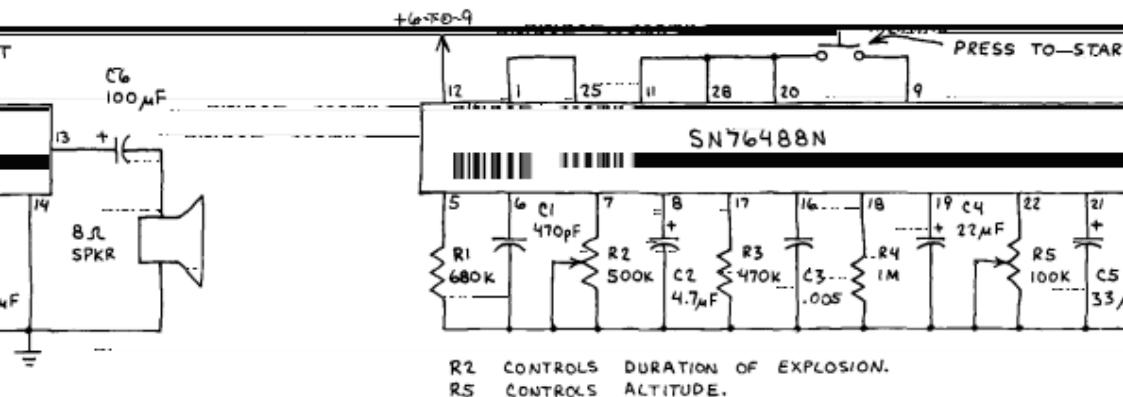

DIGITAL INTEGRATED CIRCUITS

INTRODUCTION

DIGITAL IC'S ARE 2-STATE DEVICES. ONE STATE IS NEAR 0 VOLTS OR GROUND (LOW OR L) AND THE OTHER IS NEAR THE IC'S SUPPLY VOLTAGE (HIGH OR H). SUBSTITUTE 0 FOR L AND 1 FOR H AND DIGITAL IC'S CAN PROCESS INDIVIDUAL BINARY DIGITS (BITS) OR MULTIPLE BIT WORDS. A 4-BIT WORD IS A NIBBLE AND AN 8-BIT WORD IS A BYTE.

THE BINARY SYSTEM

IT'S VERY HELPFUL TO KNOW THE FIRST 16 BINARY NUMBERS. IF 0=L AND 1=H, THEY ARE:

0 - LLLL	8 - HLLL
1 - LLLH	9 - HLLH
2 - LLHL	10 - HLHL
3 - LLHH	11 - HLLH
4 - LHLL	12 - HALL
5 - LHHL	13 - HALH
6 - LHLH	14 - HHHL
7 - LHHH	15 - HHHH

NOTE THAT LLLL(0) IS AS MUCH A NUMBER AS ANY OTHER NUMBER.

LOGIC GATES

LOGIC CIRCUITS ARE MADE BY INTERCONNECTING TWO OR MORE OF THESE BASIC LOGIC GATES:

A	B	OUT
L	L	L
L	H	H
H	L	H
H	H	H

AND

A	B	OUT
L	L	H
L	H	H
H	L	H
H	H	H

NAND

A	B	OUT
L	L	L
L	H	H
H	L	H
H	H	H

OR

A	B	OUT
L	L	H
L	H	H
H	L	H
H	H	H

NOR

A	B	OUT
L	L	L
L	H	L
H	L	L
H	H	L

EXCLUSIVE-OR

A	B	OUT
L	L	L
L	H	H
H	L	H
H	H	L

EXCLUSIVE-NOR

A	OUT
L	L
H	H

YES (BUFFER)

A	OUT
L	L
H	H

NOT (INVERTER)

CONTROL	A	OUT
L	L	L
L	H	H
H	X	HI-Z

3-STATE LOGIC


CONTROL	A	OUT
L	L	L
L	H	H
H	X	HI-Z

HI-Z: OUTPUT IN HIGH IMPEDANCE STATE.

MOS/CMOS INTEGRATED CIRCUITS

INTRODUCTION

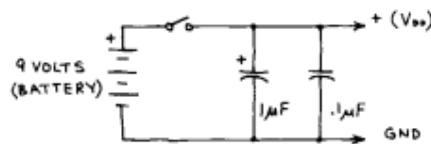MOS ICs CAN CONTAIN MORE FUNCTIONS PER CHIP THAN TTL/LS AND ARE VERY EASY TO USE. MOST CHIPS IN THIS SECTION ARE CMOS (COMPLEMENTARY MOS). THEY CONSUME VERY LITTLE POWER AND OPERATE OVER A +3-15 VOLT RANGE. CMOS CAN BE POWERED BY THIS:



OR YOU CAN USE A LINE POWERED SUPPLY MADE FROM A 7805/7812/7815. SEE THE LINEAR SECTION.


INCIDENTALLY, YOU CAN POWER A CMOS CIRCUIT FROM TWO SERIES CONNECTED PENLIGHT CELLS, BUT A 9-12 VOLT SUPPLY WILL GIVE BETTER PERFORMANCE.

OPERATING REQUIREMENTS

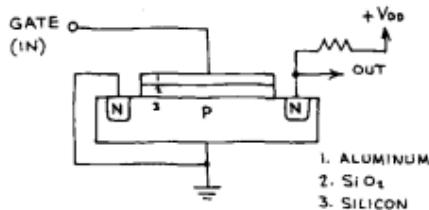
1. THE INPUT VOLTAGE SHOULD NOT EXCEED V_{DD} ! (TWO EXCEPTIONS: THE 4049 AND 4050.)
2. AVOID, IF POSSIBLE, SLOWLY RISING AND FALLING INPUT SIGNALS SINCE THEY CAN CAUSE EXCESSIVE POWER CONSUMPTION. RISETIMES FASTER THAN 15 MICROSECONDS ARE BEST.
3. ALL UNUSED INPUTS MUST BE CONNECTED TO V_{DD} (+) OR V_{SS} (GND). OTHERWISE ERATIC CHIP BEHAVIOR AND EXCESSIVE CURRENT CONSUMPTION WILL OCCUR.
4. NEVER CONNECT AN INPUT SIGNAL TO A CMOS CIRCUIT WHEN THE POWER IS OFF.
5. OBSERVE HANDLING PRECAUTIONS.

HANDLING PRECAUTIONS

A CMOS CHIP IS MADE FROM PMOS AND NMOS TRANSISTORS. MOS MEANS METAL-OXIDE-SILICON (OR SEMICONDUCTOR). P AND N REFER TO POSITIVE AND NEGATIVE CHANNEL MOS TRANSISTORS. AN NMOS TRANSISTOR LOOKS LIKE THIS:



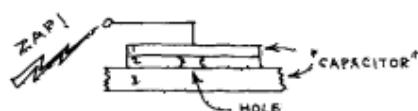A PMOS TRANSISTOR IS IDENTICAL EXCEPT THE P AND N REGIONS ARE EXCHANGED. THE SiO_2 (SILICON DIOXIDE) LAYER IS A GLASSY FILM THAT SEPARATES AND INSULATES THE METAL GATE FROM THE SILICON SUBSTRATE. THIS FILM IS WHY A MOS TRANSISTOR OR IC PLACES PRACTICALLY NO LOAD ON THE SOURCE OF AN INPUT SIGNAL. THE FILM IS VERY THIN AND IS THEREFORE EASILY PUNCTURED BY STATIC ELECTRICITY:




PREVENT STATIC DISCHARGE!

1. NEVER STORE MOS IC's IN NONCONDUCTIVE PLASTIC "SNOW," TRAYS, BAGS OR FOAM.
2. PLACE MOS IC's PINS DOWN ON AN ALUMINUM FOIL SHEET OR TRAY WHEN THEY ARE NOT IN A CIRCUIT OR STORED IN CONDUCTIVE FOAM.
3. USE A BATTERY POWERED IRON TO SOLDER MOS CHIPS. DO NOT USE AN AC POWERED IRON.


COMPLEX SOUND GENERATOR (CONTINUED) SN76477N /

NOISE GENERATOR

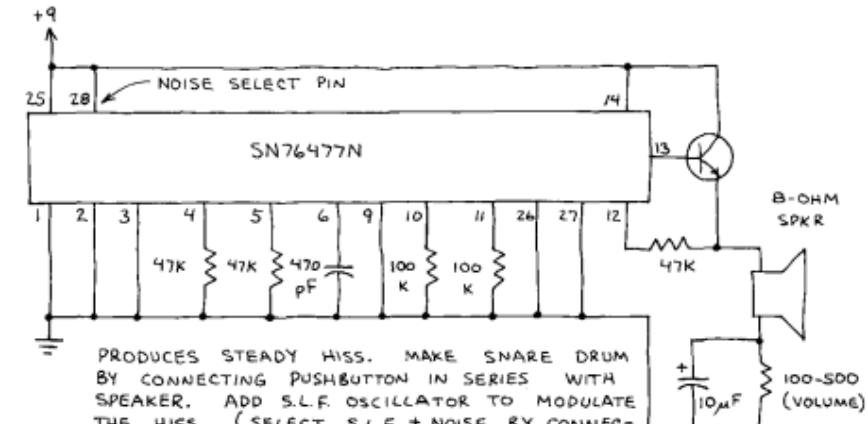

PRODUCES STEADY HISS. MAKE SNARE DRUM BY CONNECTING PUSHBUTTON IN SERIES WITH SPEAKER. ADD S.L.F. OSCILLATOR TO MODULATE THE HISS. (SELECT S.L.F. + NOISE BY CONNECTING PINS 25 AND 26 TO GND AND PIN 27 TO +9V. ADD 1M POT FROM PIN 20 TO GND AND 1μF CAPACITOR FROM PIN 21 TO GND.) SOUNDS LIKE STEAM TRAIN OR PROPELLER AIRCRAFT DEPENDING ON ADJUSTMENT OF 1M POT.

UNIVERSAL UP-DOWN TONE GENERATOR

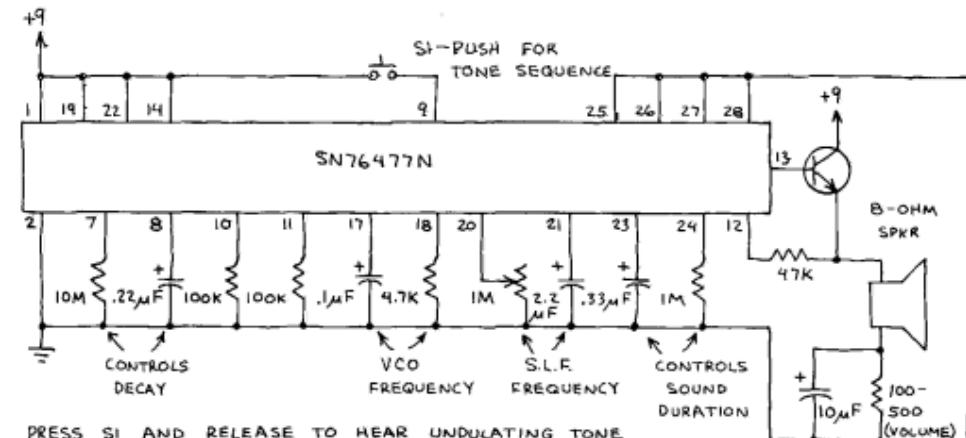

PRESS SI AND RELEASE TO HEAR UNDULATING TONE THAT GRADUALLY DECAYS AND STOPS. CHANGE VCO AND S.L.F. COMPONENTS FOR MANY DIFFERENT SOUND EFFECTS RANGING FROM SIREN TO SCIENCE FICTION MOVIE SOUNDS. FOR CONTINUOUS SOUND, OMIT COMPONENTS AT PINS 7, 8, 23, 24 AND GROUND PIN 9.


COMPLEX SOUND GENERATOR SN76477N

NOTE: THE SN76488 INCLUDES BUILT-IN SPEAKER AMPLIFIER. THE SN76477 DOES NOT.

INCORPORATES S.L.F.
 (SUPER LOW FREQUENCY
 OSCILLATOR), VCO
 (VOLTAGE CONTROLLED
 OSCILLATOR), NOISE
 GENERATOR AND A
 MIXER THAT ALLOWS
 THE OUTPUTS FROM
 ONE OR MORE OF
 THE ABOVE TO BE
 COMBINED. CAN BE
 OPERATED TOGETHER
 WITH APPROPRIATE
 RESISTORS AND
 CAPACITORS TO
 PRODUCE MANY KINDS
 OF SOUNDS. CAN BE
 CONTROLLED BY EXTERNAL
 LOGIC. SEE DATA
 SUPPLIED WITH CHIP FOR
 MORE INFO.



THIS CHIP IS EASY +4.5-12V (9V BEST)
TO USE IF YOU FOLLOW
DATA SHEET INSTRUCTIONS.

PERCUSSION SYNTHESIZER

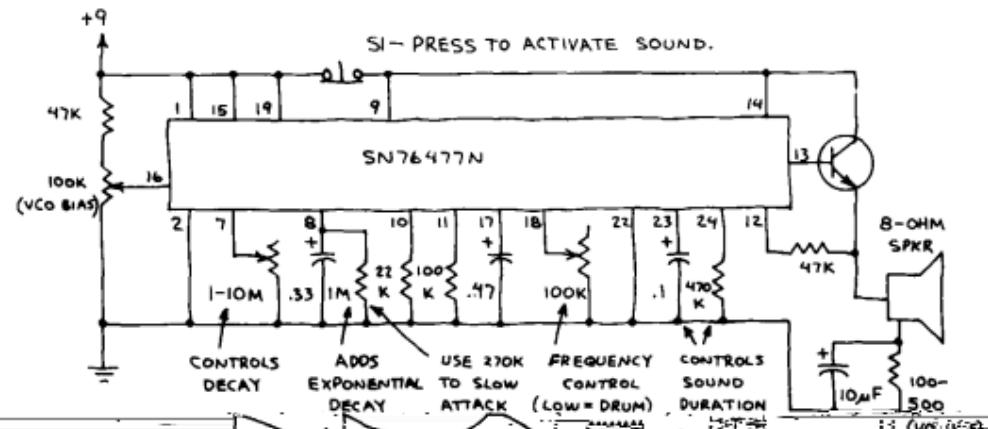


INTERFACING CMOS

I. IF SUPPLY VOLTAGES ARE EQUAL:

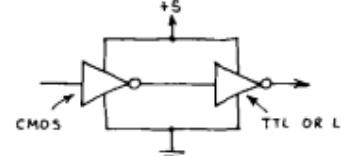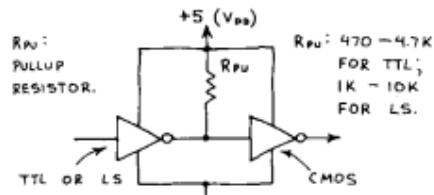


2. DIFFERENT SUPPLY VOLTAGES:

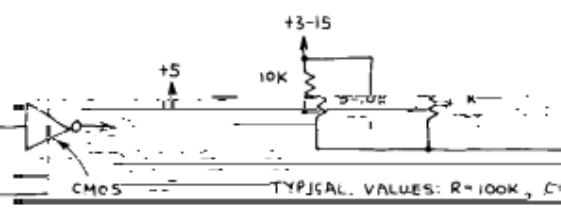

OK TO USE -4049 ... BUT MUCH MDR
CURRENT WILL BE REQUIRED.



CMOS TROUBLESHOOTING

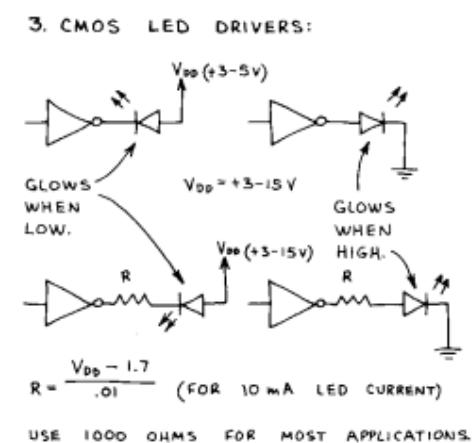1. DO ALL INPUTS GO SOMEWHERE?
 2. ARE ALL IC PINS INSERTED INTO THE BOARD OR SOCKET?
 3. IS THE IC HOT? IF SO, SEE 1-2 ABOVE AND MAKE SURE THE OUTPUT IS NOT OVERLOADED.
 4. DOES THE CIRCUIT OBEY ALL CMOS OPERATING REQUIREMENTS?
 5. HAVE YOU FORGOTTEN A CONNECTION?



CMOS LOGIC CLOCK

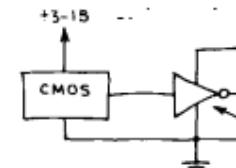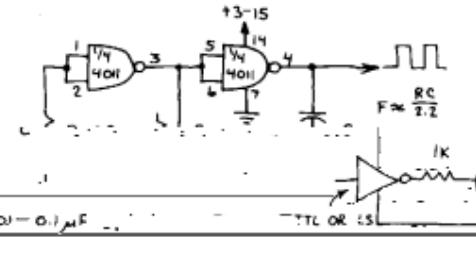MANY CIRCUITS IN THIS SECTION
REQUIRE A SOURCE OF PULSES.
HERE'S A SIMPLE CMOS CLOCK:





NOTE THAT CMOS
BY AT LEAST 5 VDD
CMOS IS INTERFACE
OTHERWISE THE CMOS
EXCEED VDD.

QUAD NAND GATE

4011


THE BASIC CMOS BUILDING BLOCK CHIP. MORE APPLICATIONS THAN TTL 7400/74LS00 QUAD NAND GATE.

CONTROL GATE

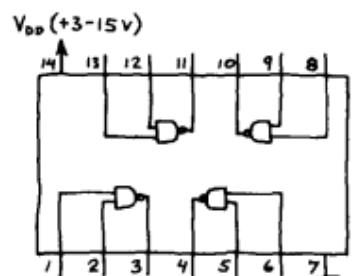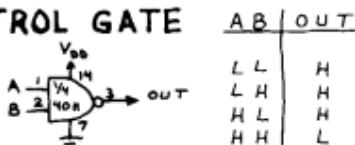


IMPORTANT: CONNECT ALL UNUSED INPUTS TO PIN 7 OR 14!


INVERTER

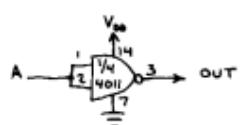



AND GATE

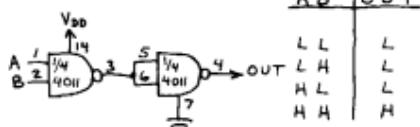


OR GATE

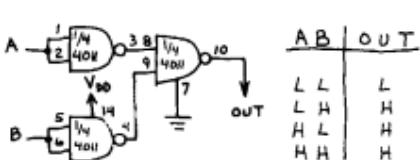


AND-OR GATE

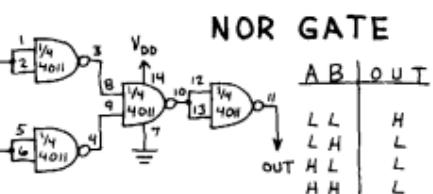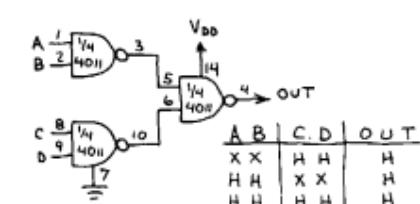


4-INPUT NAND GATE

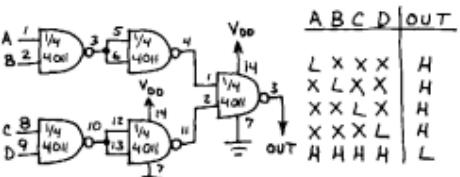

EXCLUSIVE-OR GATE

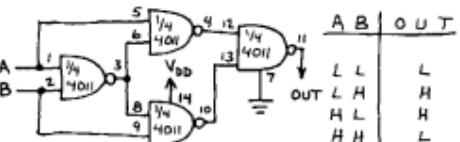

EXCLUSIVE-NOR GATE

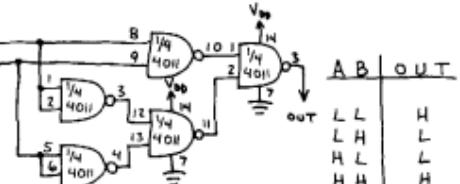

DUAL 2-WATT AMPLIFIER

LM1877/LM377

HIGH QUALITY, EASY TO USE POWER AMPLIFIER. IDEAL FOR DO-IT-YOURSELF STEREO, P.A. SYSTEMS, INTERCOMS, ETC. AUTOMATIC THERMAL SHUTDOWN PROTECTS AGAINST OVERHEATING. 70 dB CHANNEL SEPARATION MEANS.. VIRTUALLY NO

CROSSTALK. ONLY .5 MICROVOLTS NOISE INPUT.

HEAT SINKING UNNECESSARY IN MANY

APPLICATIONS SINCE AVERAGE POWER IS

USUALLY WELL BELOW BRIEF PEAKS.. IN

ANY CASE, PINS 3, 4, 5, 10, 11, AND 12 SHOULD

BE CONNECTED TOGETHER. IF LOAD EXCEEDS


DEVISER RATING, THERMAL SHUTDOWN WILL

OCURR.. AND WILL CAUSE SEVERE DISTORTION.

USE HEAT SINK (UP TO 10 SQUARE INCHES OF


COPPER FOIL ON PC BOARD OR METAL FIN)

IF THIS OCCURS,

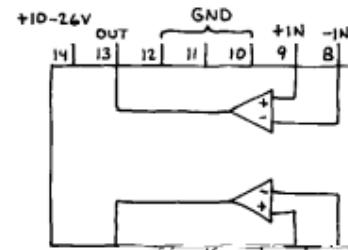


4-WATT AMPLIFIER

STEREO AMPLIFIER

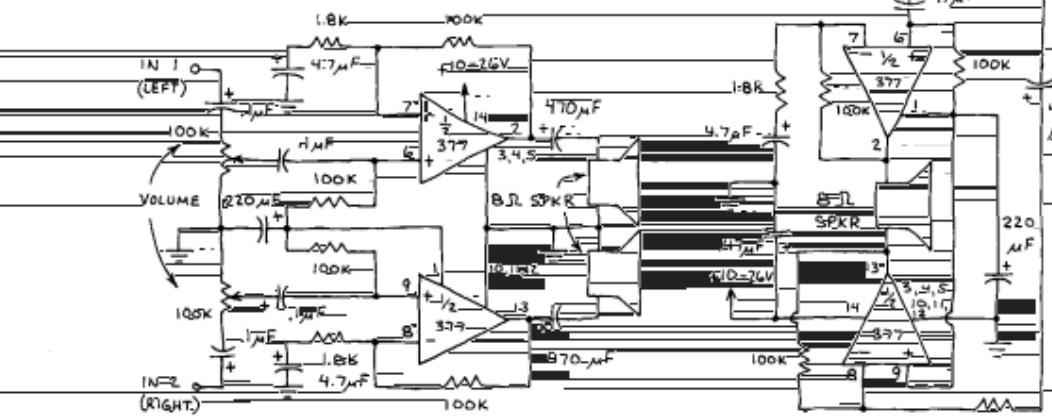


PUBLIC ADDRESS SYSTEM

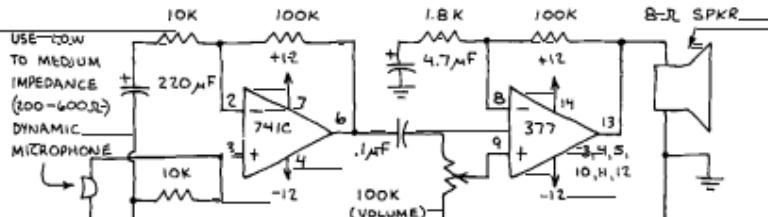


THIS CIRCUIT WORKS WELL.
NOTE FEWER PARTS IN
LM1877 / LM377 STAGE... THANKS
TO SPLIT POWER SUPPLY.

8-WATT POWER AMPLIFIER LM383 / TDA2002


POWER AMPLIFIER DESIGNED SPECIFICALLY FOR AUTOMOTIVE APPLICATIONS — BUT IDEAL FOR ANY AUDIO AMPLIFICATION SYSTEM. DESIGNED TO DRIVE A 4-OHM LOAD (EQUIVALENT TO A SINGLE 4-OHM SPEAKER OR TWO 8-OHM SPEAKERS IN PARALLEL). THIS CHIP CONTAINS THERMAL SHUTDOWN CIRCUITRY TO PROTECT ITSELF FROM EXCESSIVE LOADING. THIS WILL CAUSE SEVERE DISTORTION DURING OVERLOAD CONDITIONS. YOU MUST USE AN APPROPRIATE HEAT SINK.

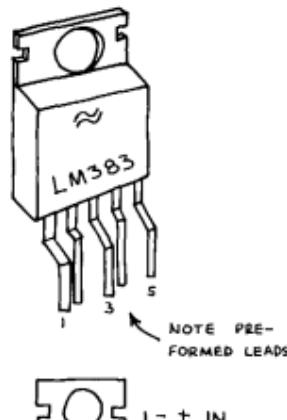

8-WATT AMPLIFIER

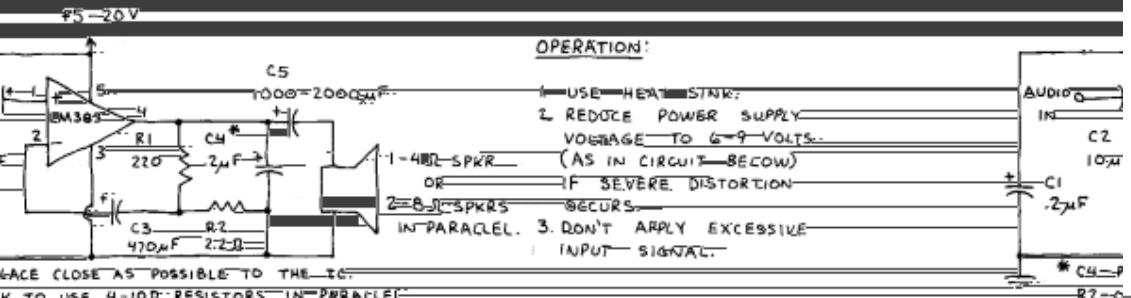


16-WATT BRIDGE AMPLIFIER

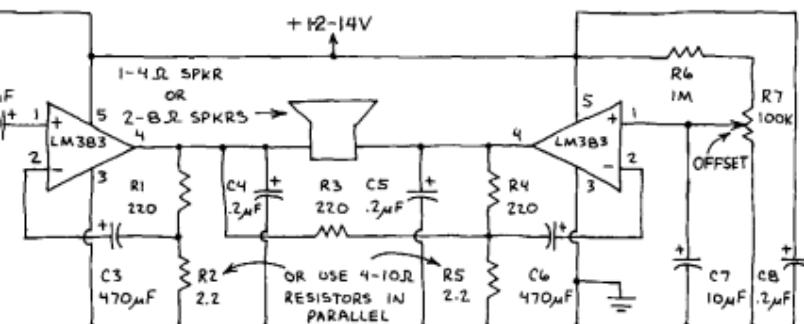


QUAD NAND GATE (CONTINUED) 4011

GATED OSCILLATOR

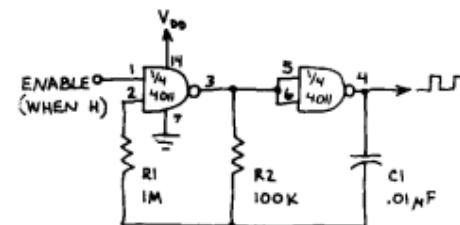


OUTPUT FREQUENCY IS 1 KHz SQUARE WAVE.

TOUCH SWITCH

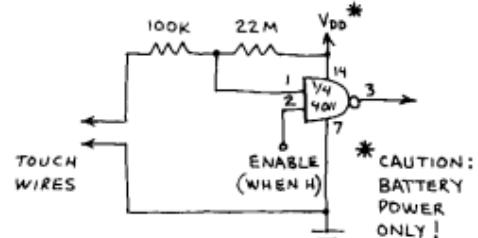


OUTPUT GOES HIGH WHEN TOUCH WIRES ARE BRIDGED BY A FINGER.

SIMPLE OSCILLATOR

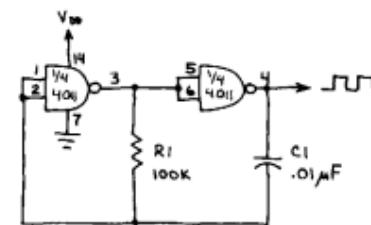


OUTPUT NOT AS SYMMETRICAL AS A 4046 CIRCUIT.

ONE-SHOT TOUCH SWITCH

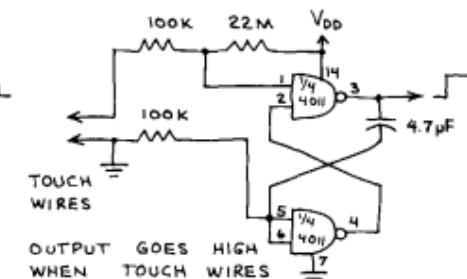


OUTPUT GOES HIGH WHEN TOUCH WIRES ARE BRIDGED BY A FINGER. OUTPUT THEN RETURNS LOW AFTER ABOUT 1 SECOND.

GATED FLASHER

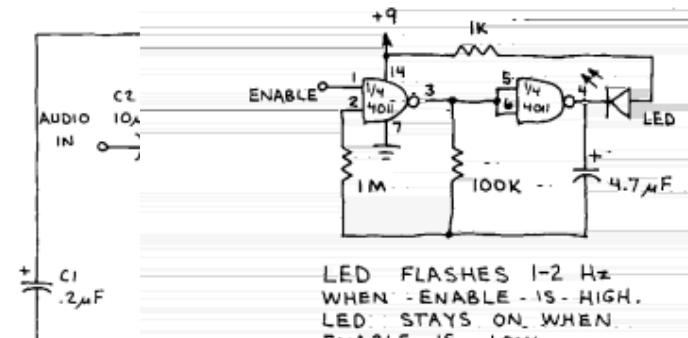

LED FLASHES 1-2 Hz WHEN ENABLE IS HIGH. LED STAYS ON WHEN ENABLE IS LOW.

INCREASED OUTPUT DRIVE

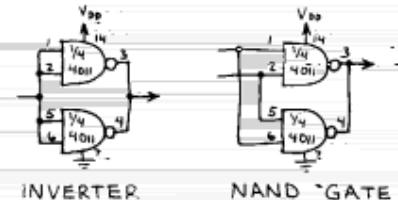



INVERTER. NAND GATE
USE THIS METHOD TO INCREASE CURRENT THE 4011 CAN SOURCE OR SINK. OK TO ADD MORE GATES.

QUAD NOR GATE

4001


AN IMPORTANT CMOS BUILDING BLOCK CHIP. ITS HIGH IMPEDANCE INPUT MAKES POSSIBLE MORE APPLICATIONS THAN THE TTL 7402/74LS02 QUAD NOR GATE.

BOUNCELESS SWITCH

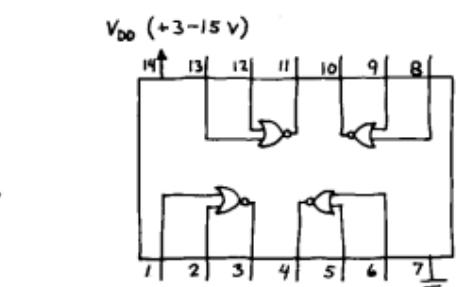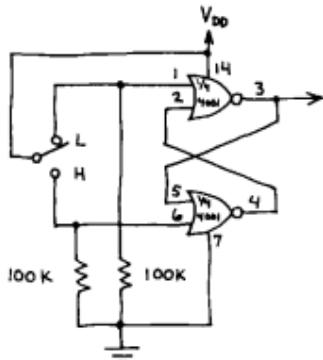


IMPORTANT: CONNECT ALL UNUSED INPUTS TO PIN 7 OR 14.

INCREASED OUTPUT DRIVE

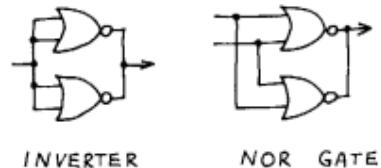


USE THIS METHOD TO INCREASE CURRENT THE 4001 CAN SOURCE OR SINK. OK TO ADD MORE GATES.

GATED TONE SOURCE

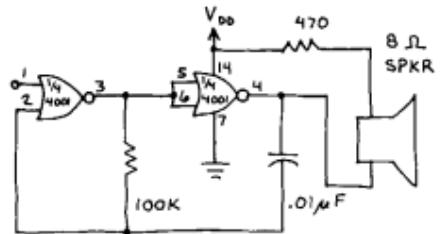


TONE FREQUENCY IS ABOUT 1KHz.

RS LATCH

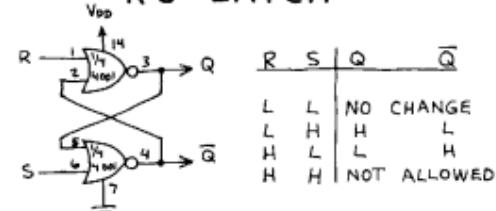


LED FLASHER

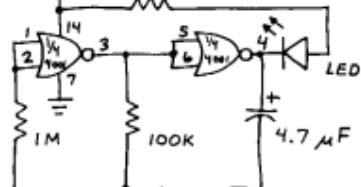

LED FLASHES 1-2 TIMES/SECOND.


OR GATE

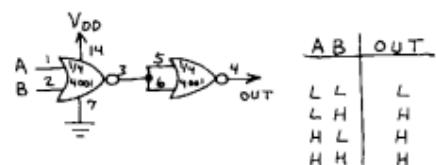


POWER AMPLIFIER

LM386

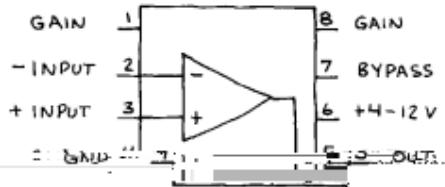
DESIGNED MAINLY FOR LOW VOLTAGE AMPLIFICATION. WILL DRIVE DIRECTLY AN 8-OHM SPEAKER. GAIN FIXED AT 20 BUT CAN BE INCREASED TO ANY VALUE UP TO 200.




X20 AMPLIFIER

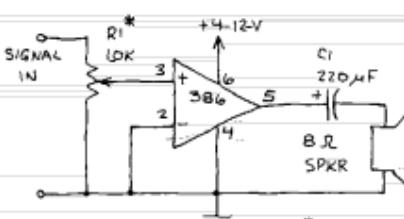


X200 AMPLIFIER

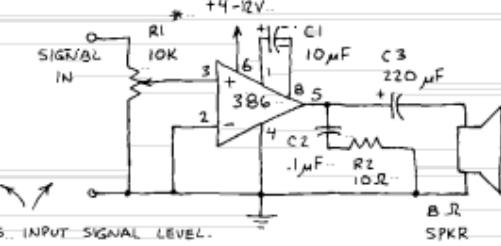


BASS BOOSTER

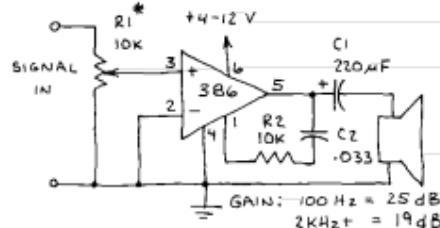

AUDIBLE ALARM

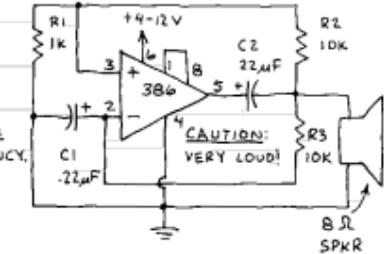


HIGH GAIN POWER AMPLIFIER

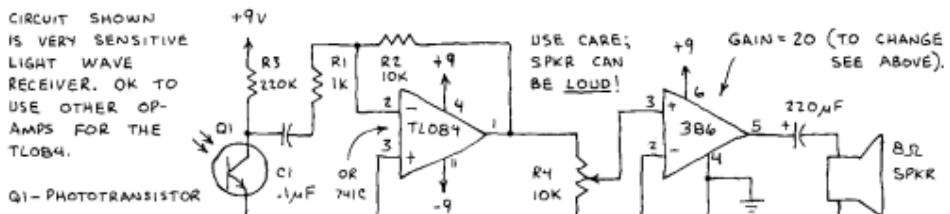


TEMPERATURE SENSOR AND ADJUSTABLE CURRENT SOURCE LM334

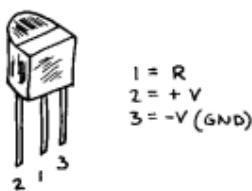
VERSATILE 3-LEAD COMPONENT THAT LOOKS MORE LIKE A TRANSISTOR THAN AN IC. CAN BE USED AS A TEMPERATURE SENSOR, CURRENT SOURCE FOR LEDs AND OTHER COMPONENTS OR CIRCUITS, VOLTAGE REFERENCE, ETC.




BASIC THERMOMETERS

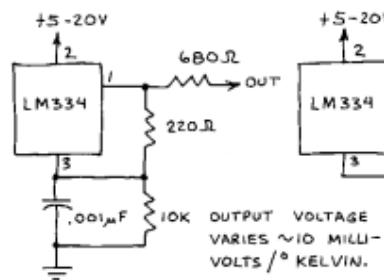


VOLTAGE REFERENCE

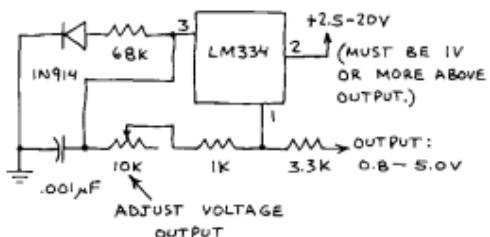


RAMP GENERATOR

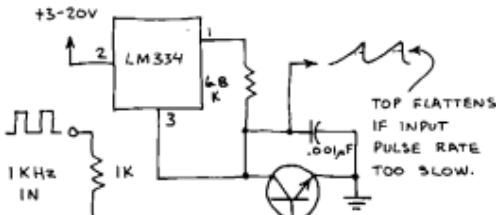


BASIC CURRENT SOURCE

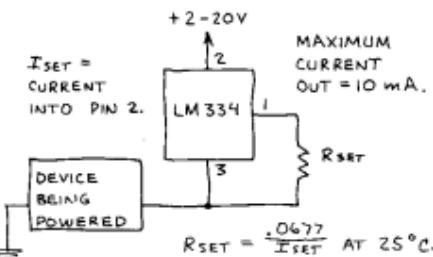

CALIBRATED LED

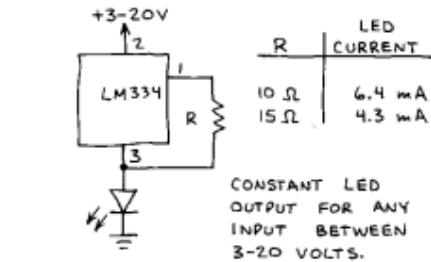


LIGHT METER

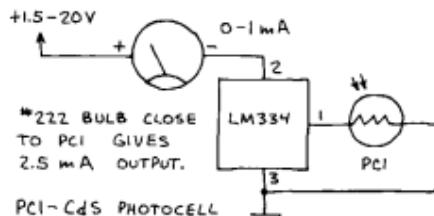


QUAD AND GATE 4081

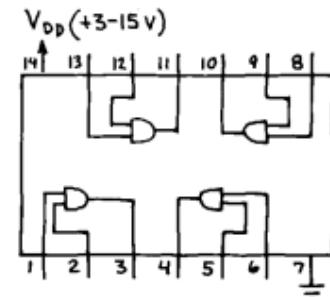
BUILDING BLOCK CHIP. USE FOR BUFFERING AND LOGIC. NOT AS VERSATILE AS 4011.




AND GATE BUFFER

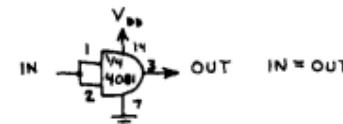


DIGITAL TRANSMISSION GATE

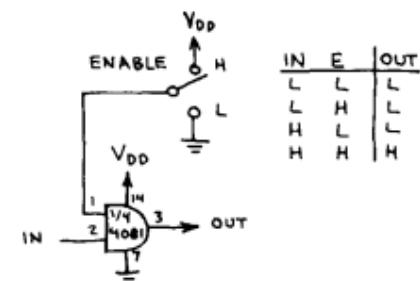


NAND GATE

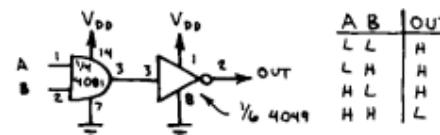


NOR GATE

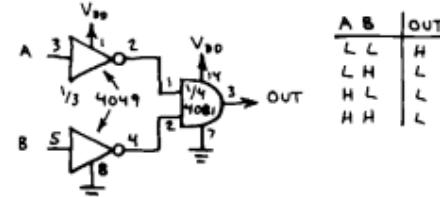


4-INPUT NAND GATE

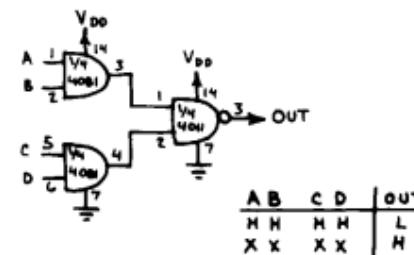

AND-OR-INVERT GATE

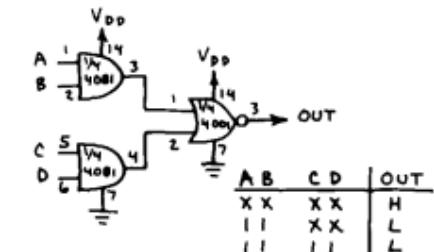


4-INPUT AND GATE

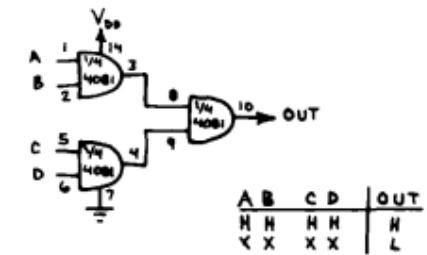

QUAD EXCLUSIVE-OR GATE 4070


THE OUTPUT OF EACH GATE GOES LOW WHEN BOTH INPUTS ARE EQUAL. THE OUTPUT GOES HIGH IF THE INPUTS ARE UNEQUAL. MANY APPLICATIONS INCLUDING BINARY ADDITION, COMPARING BINARY WORDS AND PHASE DETECTION.

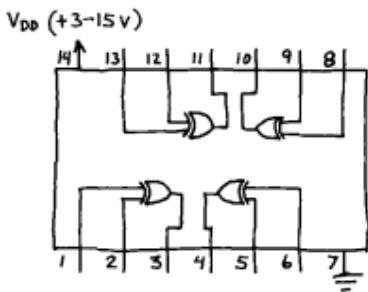IMPORTANT: CONNECT UNUSED INPUTS TO PIN 7 OR 14.




1-BIT COMPARATOR

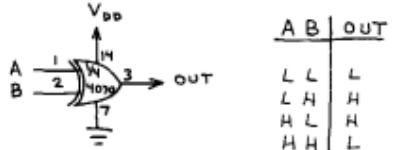THIS CIRCUIT IS ALSO A HALF-ADDER WITHOUT A CARRY OUTPUT.




4-BIT COMPARATOR


DETERMINES IF TWO 4-BIT WORDS ARE EQUAL.

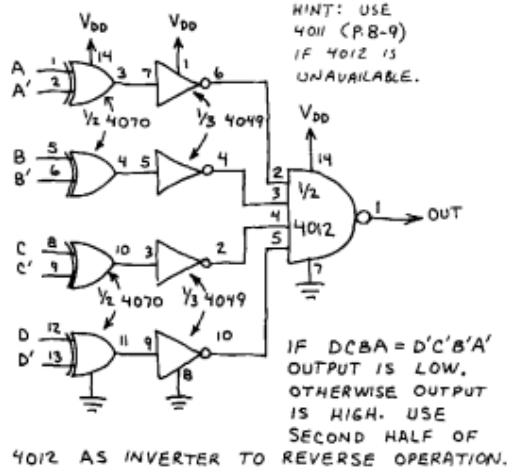


CONTROLLED INVERTER

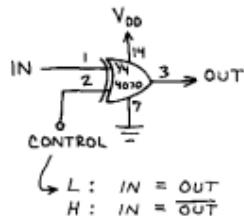

BINARY FULL ADDER

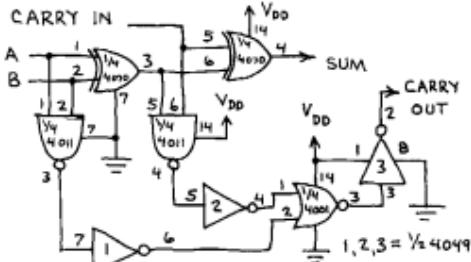


PHASE DETECTOR

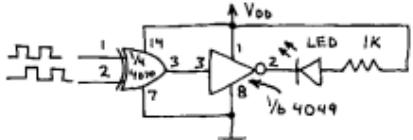


LED STOPS GLOWING WHEN THE INPUT FREQUENCIES ARE EQUAL.

8-BIT DIGITAL-TO-ANALOG CONVERTER DAC 801 (CONTINUED)

256-STEP STAIRCASE GENERATOR

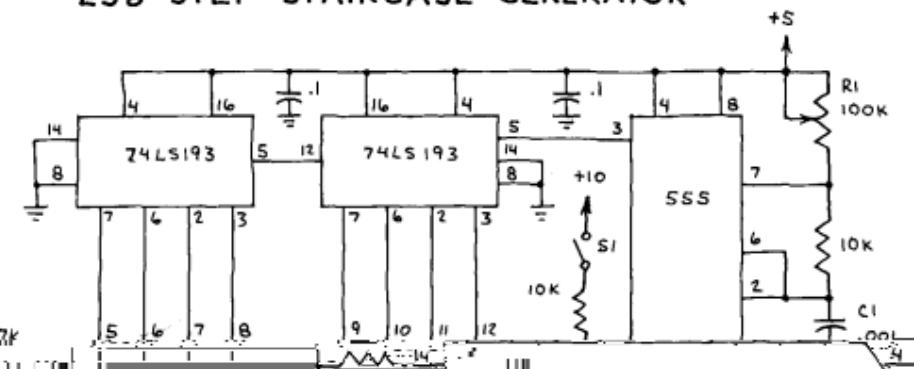



E GENERATOR

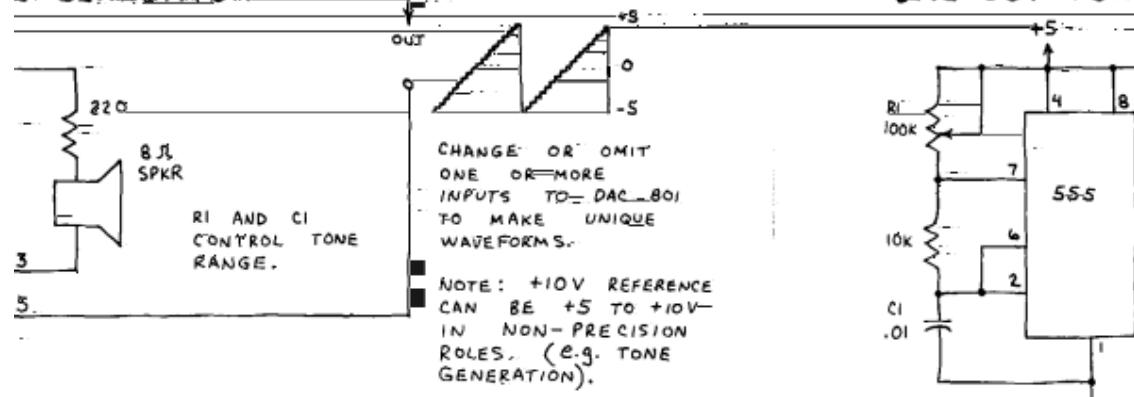

8-BIT DIGITAL-TO-ANALOG CONVERTER DAC 801


PROVIDES VERY FAST 8-BIT DIGITAL-TO-ANALOG CONVERSION. WILL ACCEPT TTL LEVELS AT INPUTS B1 TO B8. CAN PROVIDE \pm OUTPUT. USE TO INTERFACE MICROCOMPUTER TO ANALOG DEVICES.

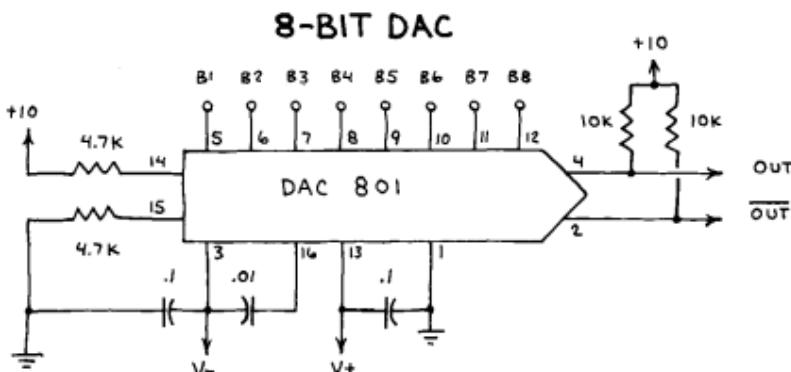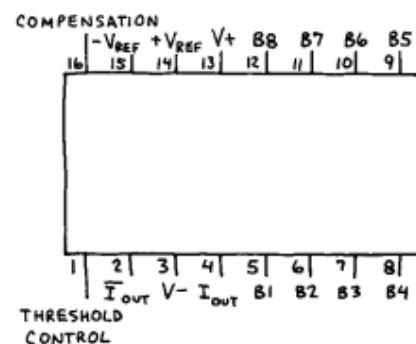B1 - MOST SIGNIFICANT BIT.
B8 - LEAST SIGNIFICANT BIT.
 $V \pm$ - ± 4.5 TO 18 V.




DAC 801 POWER SUPPLY

TI: 120VAC / 25.2 VAC CT

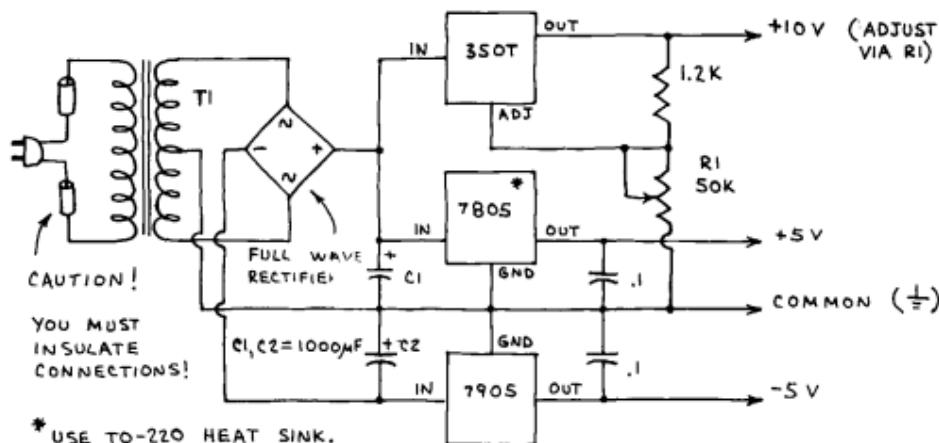

QUAD EXCLUSIVE-OR GATE (CONTINUED) 4070


EXCLUSIVE-NOR

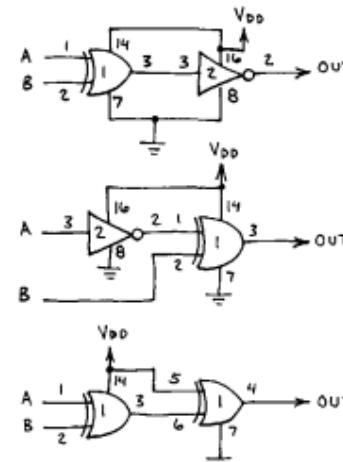

IC1 = 1/4 4070
IC2 = 1/4 4049


A	B	OUT
L	L	H
L	H	L
H	L	L
H	H	H

8-INPUT EX-OR

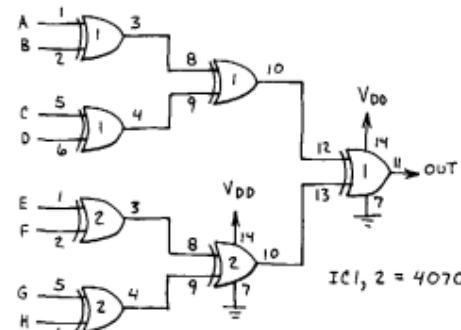


IC1, 2 = 4070

3-INPUT EX-OR

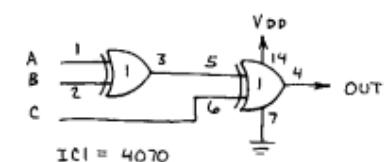

10 MHz OSCILLATOR

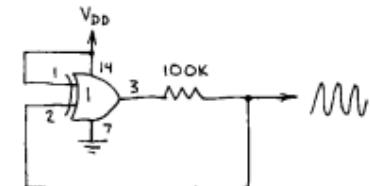


V_{DD} = 3 TO 15 VOLTS

FREQUENCY VARIES WITH V_{DD}:

V _{DD}	FREQUENCY	AMPLITUDE
5	2.4 MHz	3.5 V
10	9.4 MHz	8.0 V
15	11.0 MHz	12.0 V

SQUARE WAVE GENERATOR

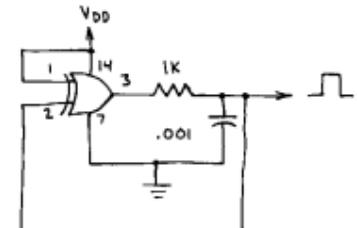



V_{DD} = 3 TO 15 VOLTS

RISETIME = 50 NANOSECONDS
FREQUENCY = 2 MHz WHEN
V_{DD} = 10 VOLTS

HEX INVERTING BUFFER 4049


IN ADDITION TO STANDARD LOGIC AND CMOS TO TTL INTERFACING, OFTEN USED IN OSCILLATORS AND PULSE GENERATORS. FOR LOW CURRENT APPLICATIONS, USE 4011 CONNECTED AS INVERTER. (OK TO USE 4011 FOR CIRCUITS ON THIS PAGE.)

CLOCK PULSE GENERATOR

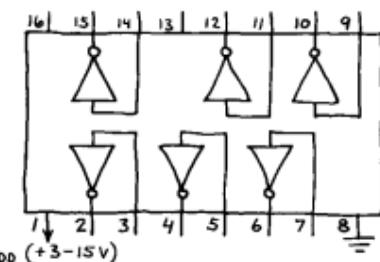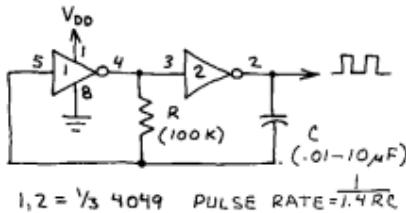


NOTE UNUSUAL LOCATION OF POWER SUPPLY PINS.


PHASE SHIFT OSCILLATOR

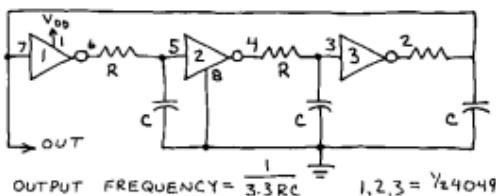


BOUNCELESS SWITCH

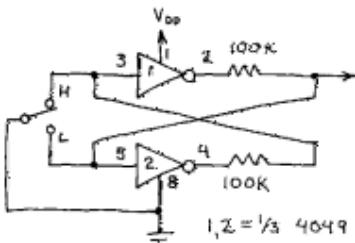


TRIANGLE WAVE SOURCE

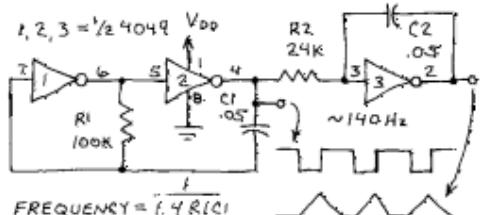

SQUARE WAVE GENERATOR

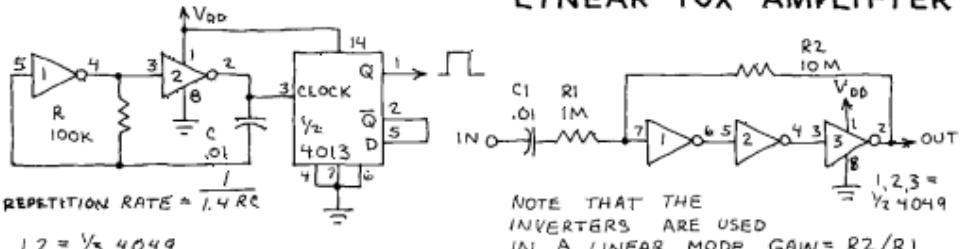


LINEAR 10X AMPLIFIER

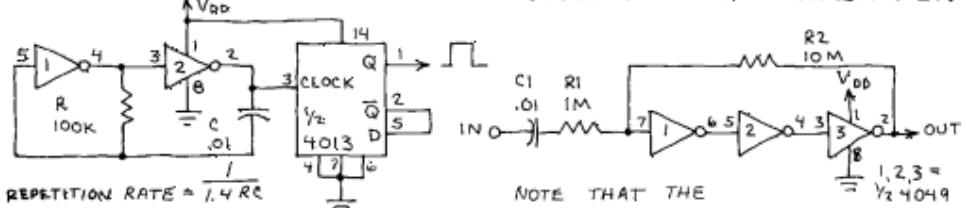


ANALOG-TO-DIGITAL CONVERTER TL507

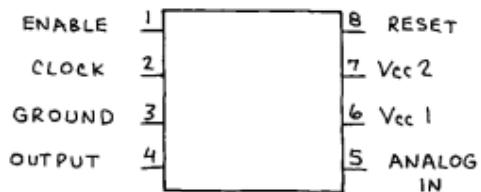PROVIDES ANALOG-TO-DIGITAL CONVERSION FOR MICROPROCESSORS. CAN PROVIDE 4-BIT OR 8-BIT OUTPUT WITH EXTERNAL COUNTER PLUS STEERING LOGIC. MAKES GOOD PULSE WIDTH MODULATOR. NOTE: USE V_{CC1} OR V_{CC2} .




V_{CC1} = 3.5 TO 6 VOLTS
 V_{CC2} = 8 TO 18 VOLTS

PULSE WIDTH MODULATOR

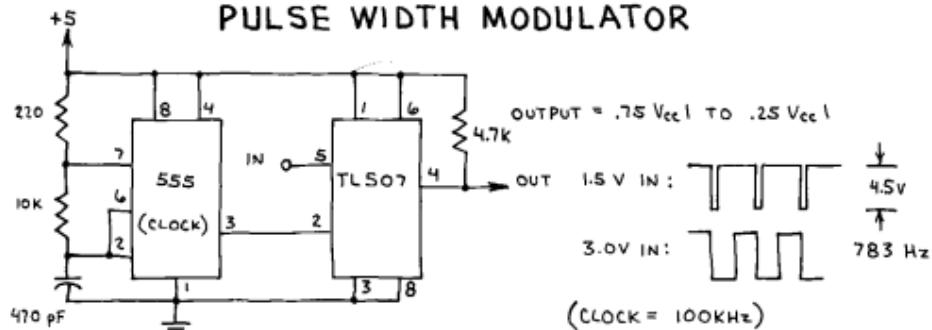


8-BIT ANALOG-TO-DIGITAL CONVERTER

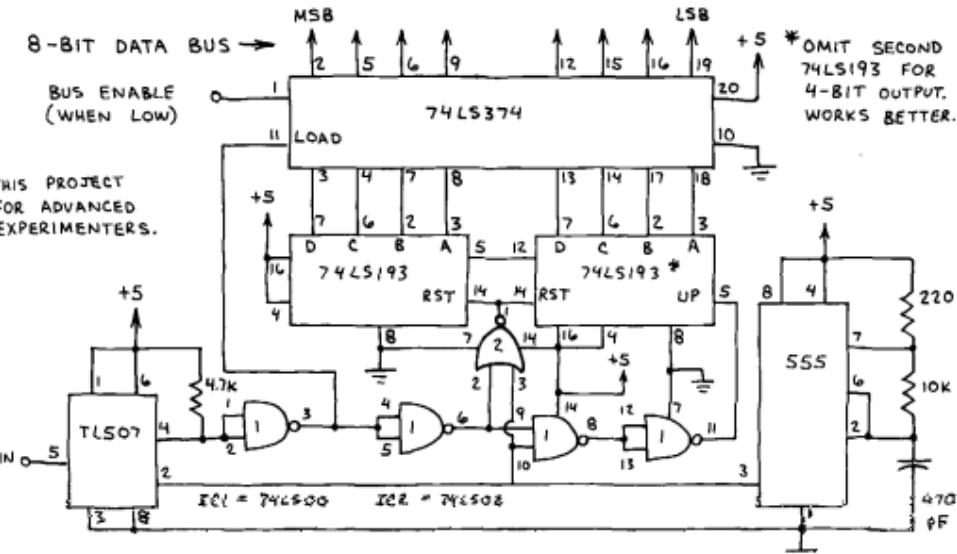


VOLTAGE CONTROLLED OSCILLATOR (VCO) 566

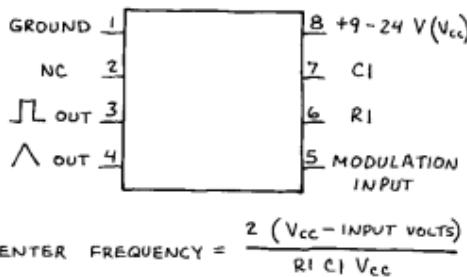
VERY STABLE, EASY TO USE TRIANGLE AND SQUARE WAVE OUTPUTS. ν_{RI} AND C_1 CONTROL CENTER FREQUENCY. VOLTAGE AT PIN 5 VARIES FREQUENCY. IMPORTANT: OUTPUT WAVE DOES NOT FALL TO 0 VOLT! AT 12 VOLTS (PIN 8), FOR EXAMPLE, TRIANGLE OUTPUT CYCLES BETWEEN +4 AND +6 VOLTS. SQUARE OUTPUT CYCLES BETWEEN +6 AND +11.5 VOLTS.



FUNCTION GENERATOR

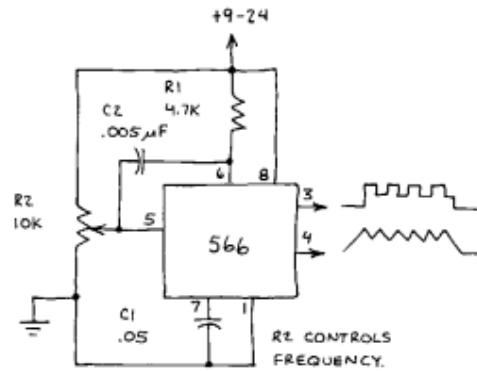


TWO-TONE WARBLER

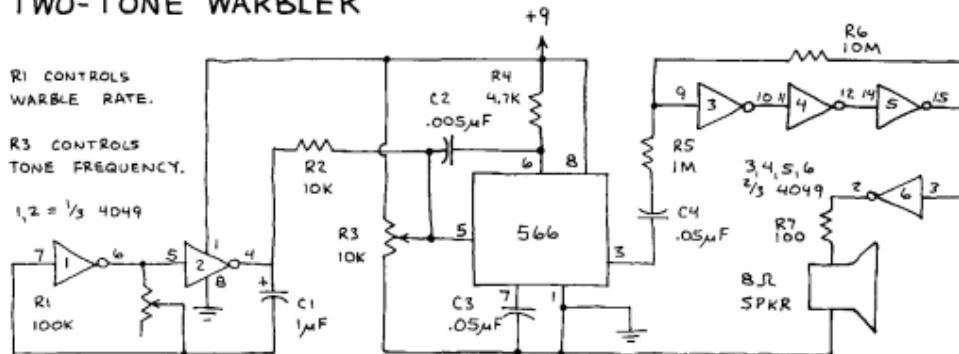

HEX NON-INVERTING BUFFER 4050


PRIMARILY INTENDED FOR INTERFACING CMOS TO TTL. SUPPLIES MORE CURRENT THAN STANDARD CMOS.

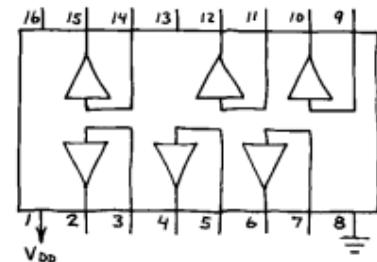IMPORTANT: ALL UNUSED INPUTS MUST GO TO PIN 1 OR 8.



NOTE UNUSUAL LOCATION OF POWER SUPPLY PINS.


FSK GENERATOR *

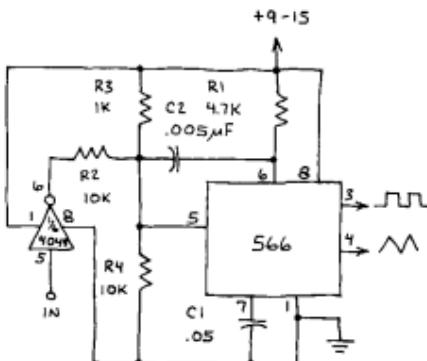


IN	OUTPUT	USE TO TRANSMIT BINARY DATA OVER TELEPHONE LINES OR STORE BINARY DATA ON MAGNETIC TAPE.
L	1.5 KHz	
H	3.0 KHz	

$V_{cc} = 9$ VOLTS.


OUTPUT EXPANDER

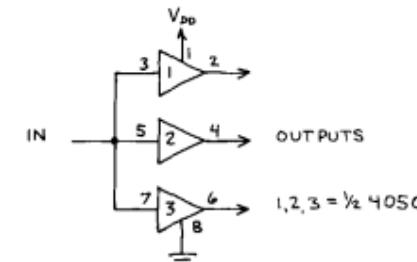


OUTPUT BUFFER

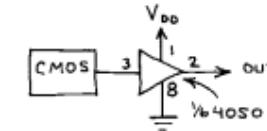


CMOS TO CMOS AT LOWER V_{dd}

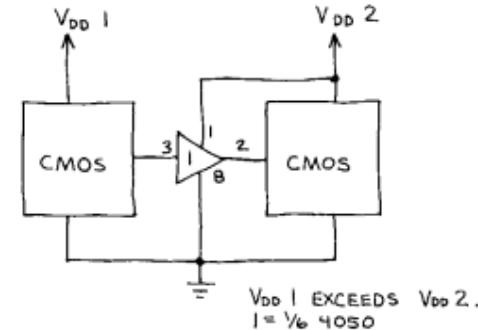


LOGIC PROBE

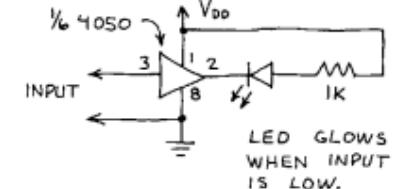

INCREASED OUTPUT DRIVE

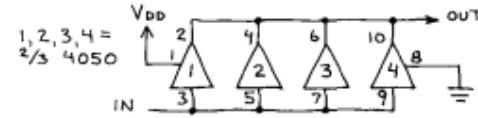


CMOS TO TTL/LS AT LOWER V_{cc}

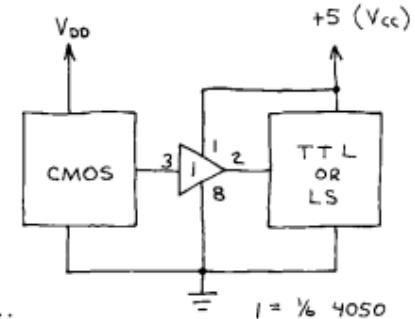



DUAL 4-INPUT NAND GATE 4012

VERY USEFUL IN MAKING DECODERS. ALSO CAN BE USED TO ADD ONE OR MORE ENABLE INPUTS TO VARIOUS CIRCUITS.

ENABLE INPUT

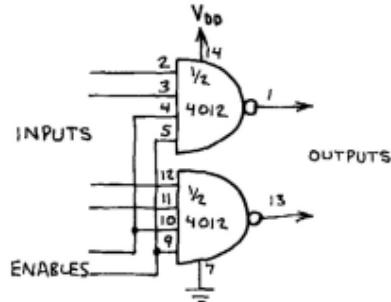


1-OF-4 DECODER

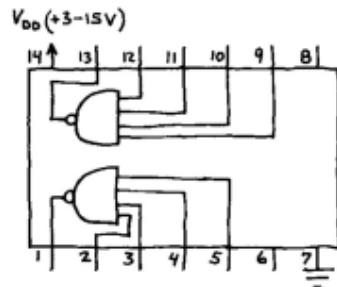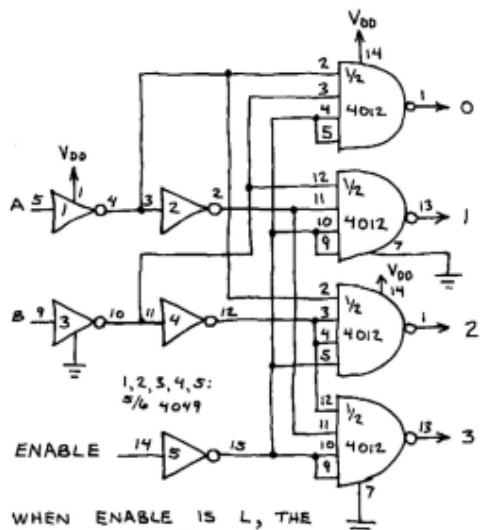


BCD DECODERS


DECIMAL 0

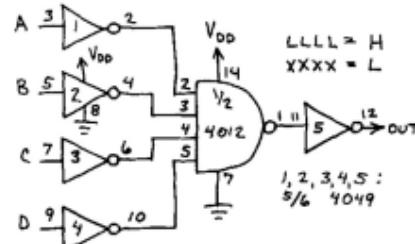

DECIMAL 1

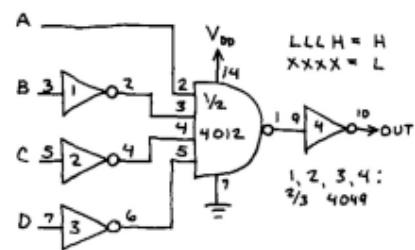

DECIMAL 9

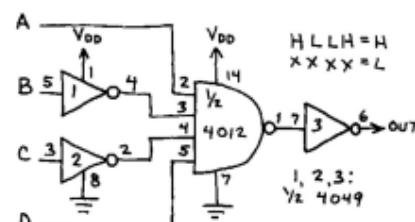


VOLTAGE-TO-FREQUENCY (CONTINUED)

FREQUENCY-TO-VOLTAGE CONVERTER

9400


AUDIO FREQUENCY METER

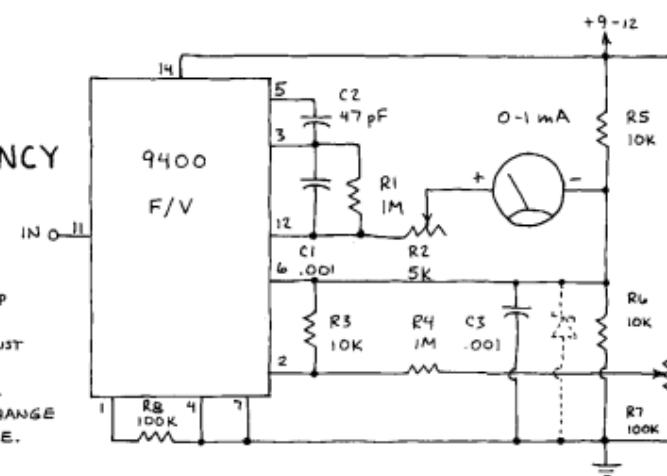INPUT FREQUENCY MUST CROSS 0 VOLT. WORKS UP TO 25 KHz. R2 IS ZERO. ADJUST FOR METER. ADJUST R7 TO GIVE MAXIMUM READING AT 25 KHz IN. FOR MORE STABILITY, CHANGE R6 TO 6-V ZENER DIODE.




ANALOG DATA TRANSMISSION SYSTEM*

TRANSMITTER

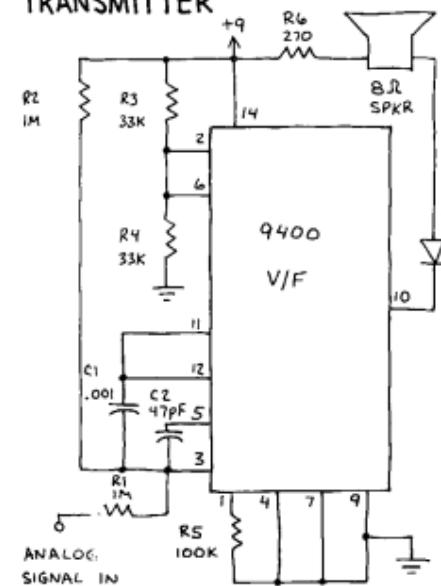

RECEIVER

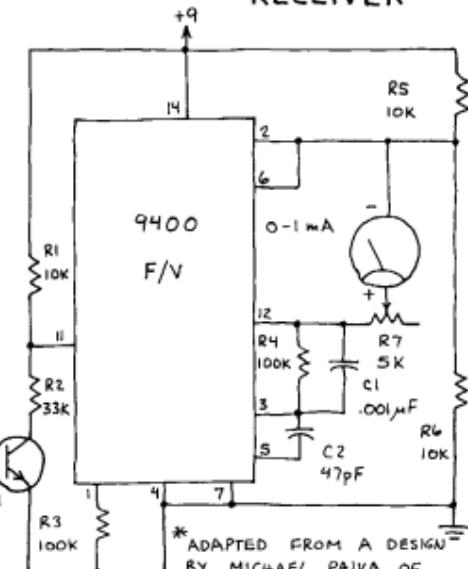


*ADAPTED FROM A DESIGN BY MICHAEL PAIVA OF TELEDRYNE.

THE SPKR IS OPTIONAL BUT MAY PROVE HELPFUL DURING INITIAL TESTING. USE AN IRLED. Q1 CAN BE THE PHOTOTRANSISTOR SUPPLIED WITH R7. IN THE RECEIVER R7 IS ZERO ADJUST.


VOLTAGE-TO-FREQUENCY FREQUENCY-TO-VOLTAGE CONVERTER 9400

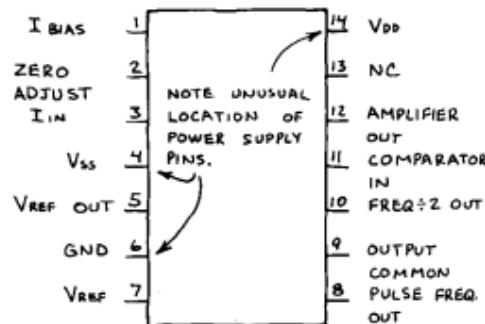IN VOLTAGE-TO-FREQUENCY (V-F) MODE, AN INPUT VOLTAGE WHICH HAS BEEN CONVERTED INTO A CURRENT BY A RESISTOR AT PIN 3 IS TRANSFORMED INTO A PROPORTIONAL FREQUENCY. IN FREQUENCY-TO-VOLTAGE MODE A FREQUENCY AT PIN 11 IS CONVERTED INTO A PROPORTIONAL VOLTAGE. THIS CHIP CAN BE OPERATED FROM A SINGLE OR DUAL POLARITY POWER SUPPLY.




CAUTION: THIS CHIP INCORPORATES BOTH BIPOLAR AND CMOS CIRCUITRY. THEREFORE CMOS HANDLING PRECAUTIONS MUST BE FOLLOWED TO AVOID PERMANENT DAMAGE.

BASIC V/F CONVERTER

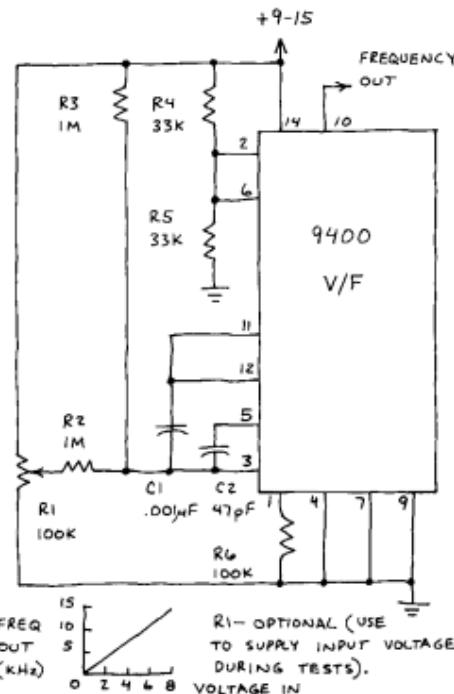


FSK* DATA TRANSMITTER

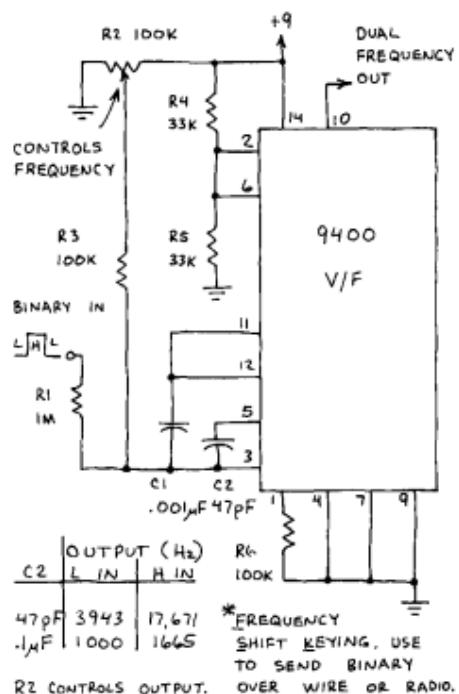


TRIPLE 3-INPUT NAND GATE 4023

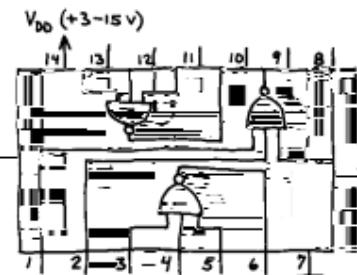
HANDY FOR MAKING CUSTOM DECODERS, CONVERTERS, AND MULTIPLE INPUT GATES.



6-INPUT OR-GATE

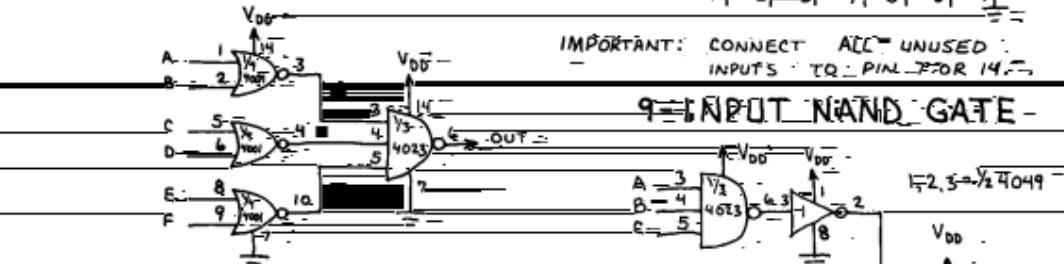


9-INPUT NAND GATE

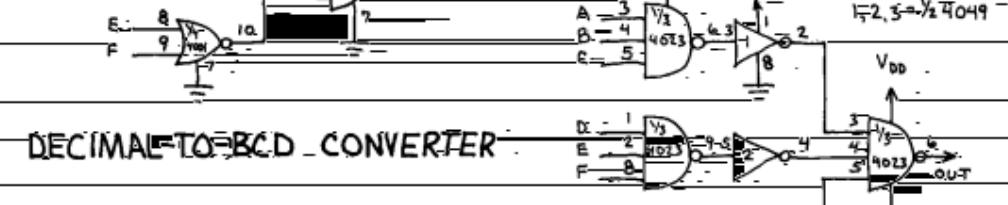


DECIMAL-TO-BCD CONVERTER

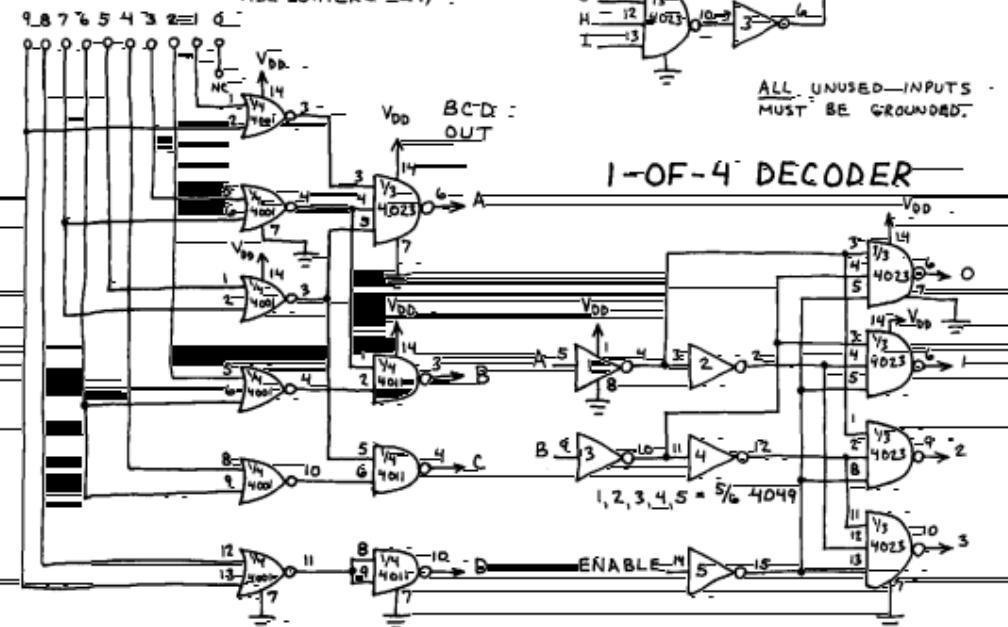DECIMAL IN (SELECTED DIGIT HIGH, ALL OTHERS LOW).




1-OF-4 DECODER

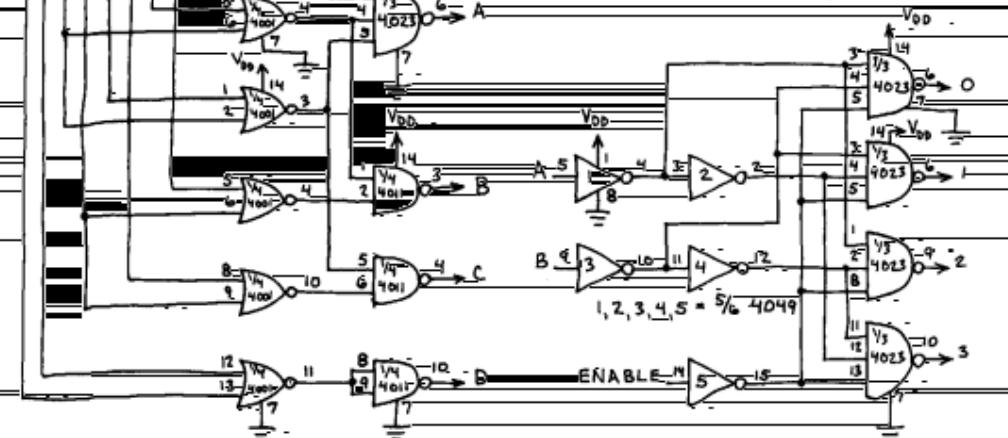


QUAD BILATERAL SWITCH

4066

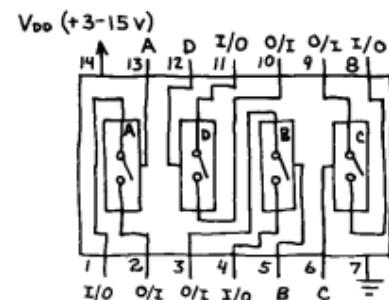
ONE OF THE MOST VERSATILE CMOS CHIPS. PINS A, B, C AND D CONTROL FOUR ANALOG SWITCHES. CLOSE A SWITCH BY CONNECTING ITS CONTROL PIN TO V_{DD} . ON RESISTANCE = 80-250 OHMS. OPEN A SWITCH BY CONNECTING ITS CONTROL PIN TO GROUND (PIN 7). OFF RESISTANCE = 10^9 OHMS. I/O (INPUT/OUTPUT) AND O/I PINS ARE REVERSIBLE.




DATA BUS CONTROL

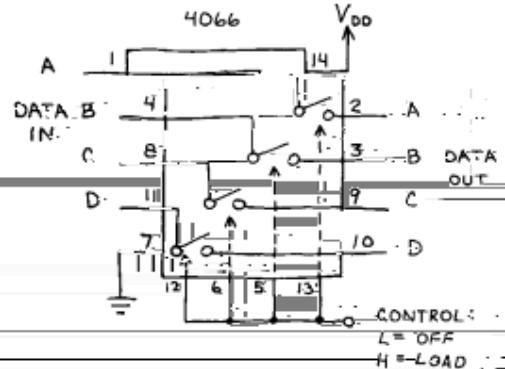

DATA SELECTOR

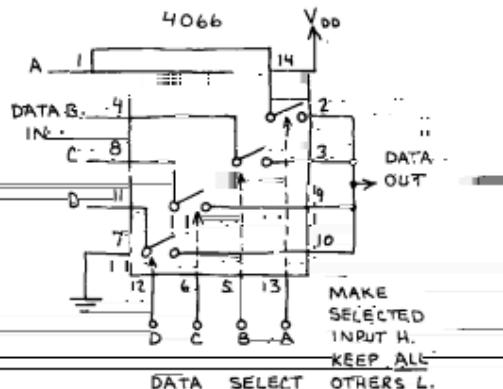

DIGITAL TO ANALOG (D/A) CONVERTER

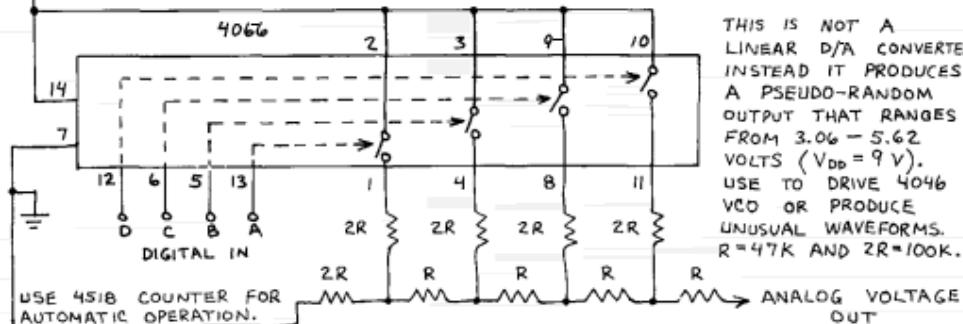

12-KEY PUSHBUTTON TONE MODULE


CEX-4000

GENERATES THE 12 STANDARD TELEPHONE TONE DIALING FREQUENCY PAIRS. V_t SHOULD NOT EXCEED 6 VOLTS. REQUIRES 3.58 MHZ CRYSTAL. OK TO USE FROM 1 TO 12 KEYS FOR REMOTE CONTROL.


TOUCH-TONE® IS A REGISTERED TRADEMARK OF AT&T.

O (FREQUENCIES IN Hz) O		
1	2	3
699.1	699.1	699.1
1215.9	1331.7	1471.9
4	5	6
766.2	766.2	766.2
1215.9	1331.7	1471.9
7	8	9
847.4	847.4	847.4
1215.9	1331.7	1471.9
*	0	#
948	948	948
1215.9	1331.7	1471.9

PORTABLE TOUCH-TONE® GENERATOR

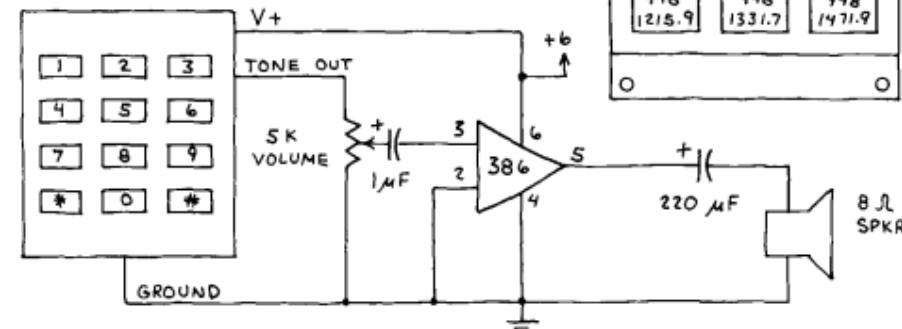


REMOTE CONTROL

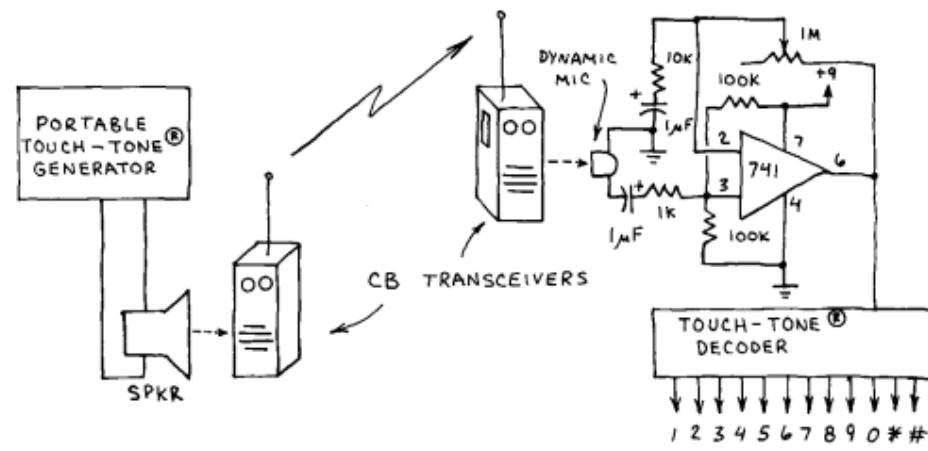

TONE DECODER (CONTINUED)

567


TOUCH-TONE® DECODER

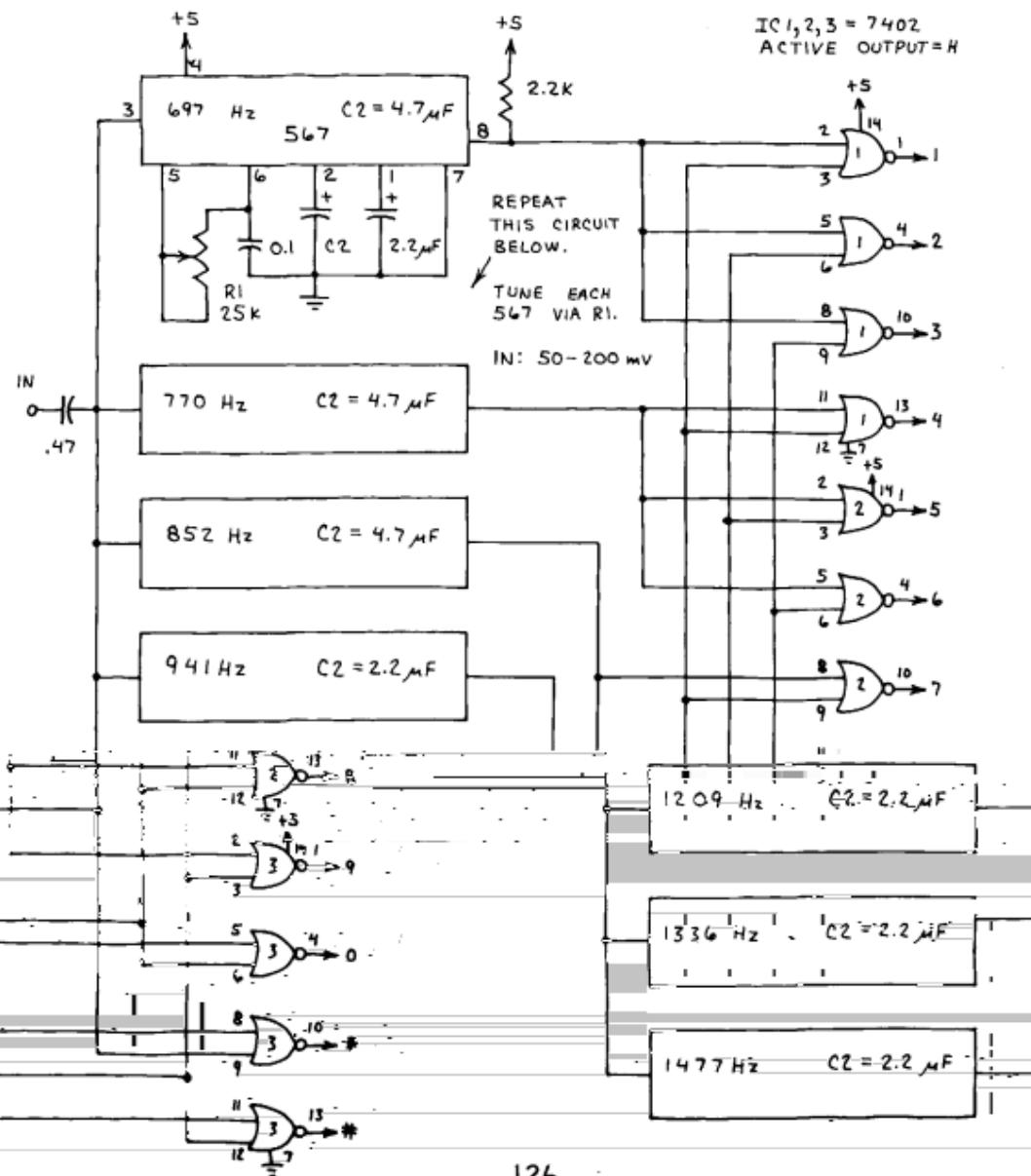


QUAD BILATERAL SWITCH (CONTINUED)

4066

PROGRAMMABLE GAIN AMPLIFIER

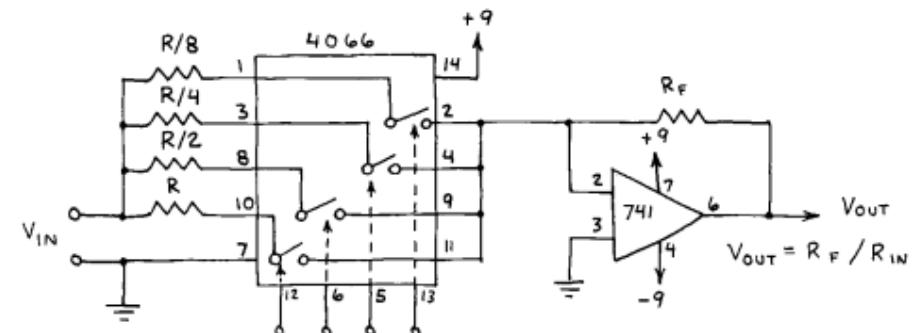

PROGRAMMABLE FUNCTION GENERATOR

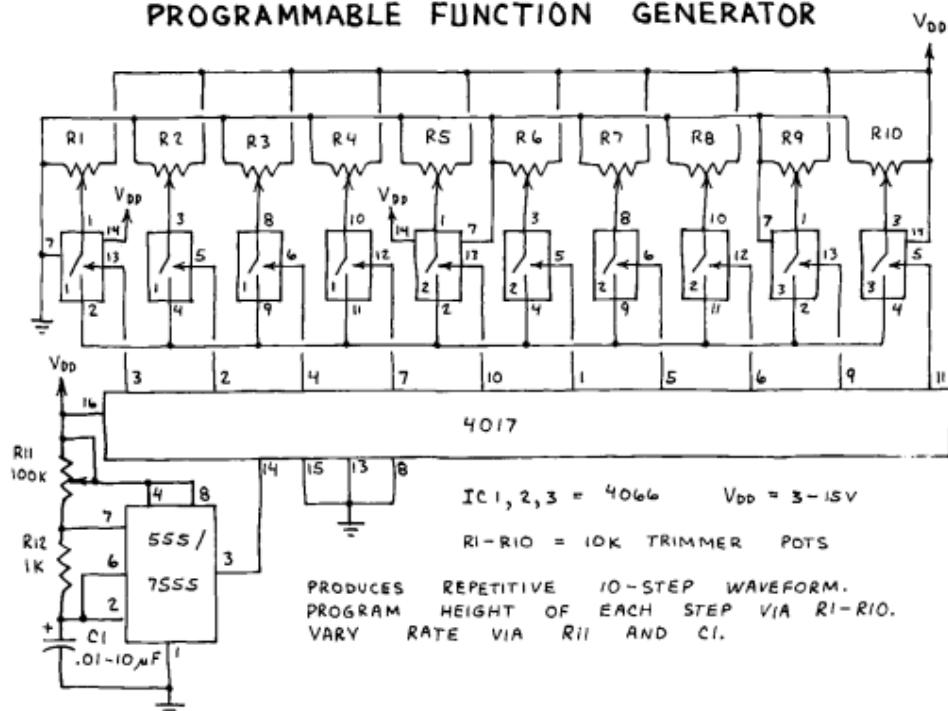


1024-BIT STATIC RAM

2102L


1024 1-BIT STORAGE LOCATIONS ADDRESSED BY PINS A0-A9. TTL/LS COMPATIBLE. CE (CHIP ENABLE) INPUT CONTROLS R/W (READ/WRITE) OPERATIONS. 3-STATE OUTPUTS.

CE	R/W	OPERATION
L	L	WRITE (LOADS BIT AT PIN 11)
L	H	READ (OUTPUTS BIT AT PIN 12)
H	X	HIZ (OUTPUT ENTERS THIRD STATE)

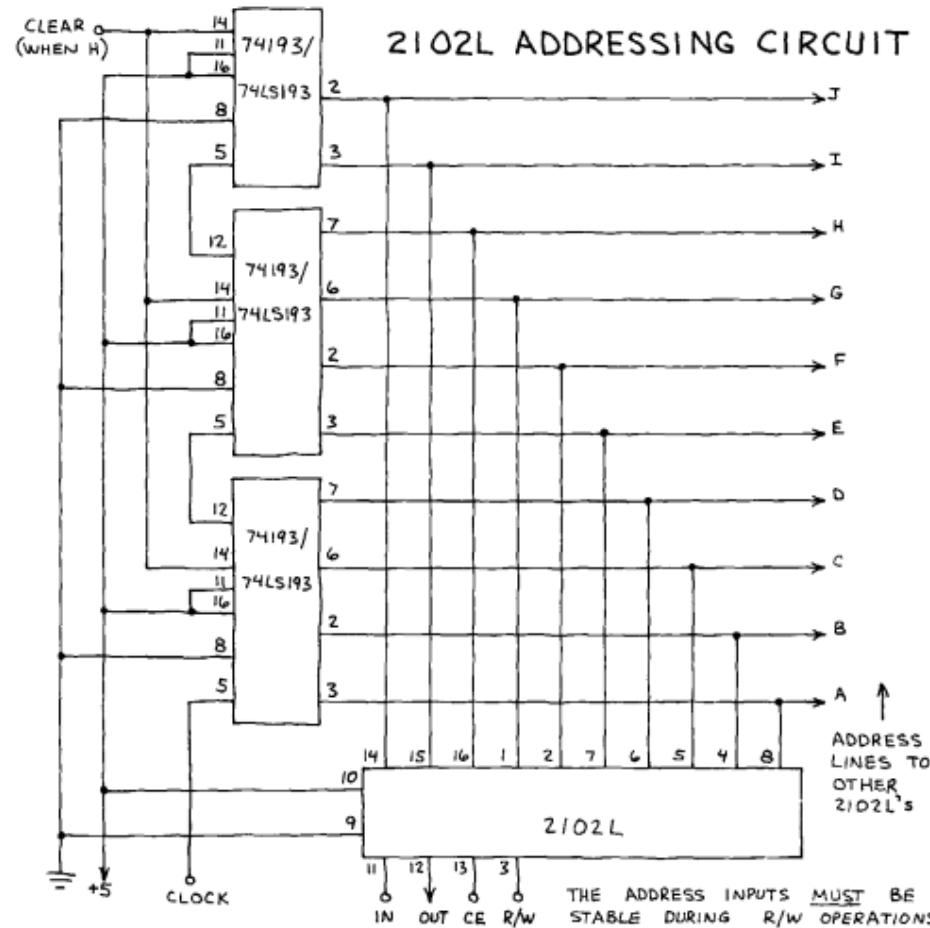


TONE DECODER (CONTINUED)


567

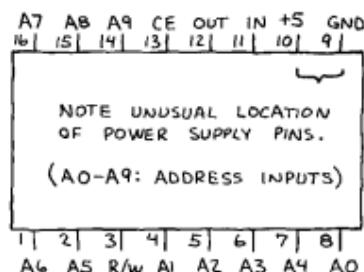



2-FREQUENCY OSCILLATOR

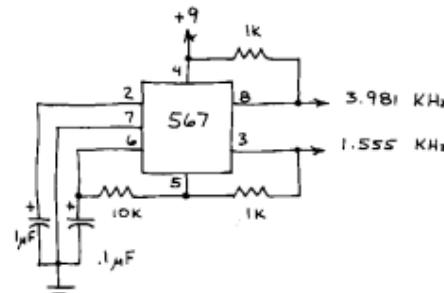


2-PHASE OSCILLATOR

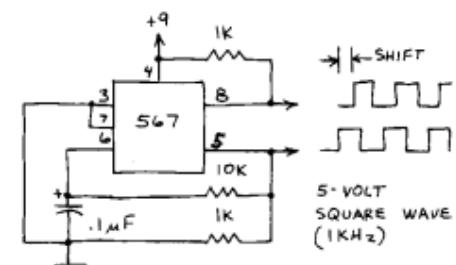

LATCHING THE 567 OUTPUT *

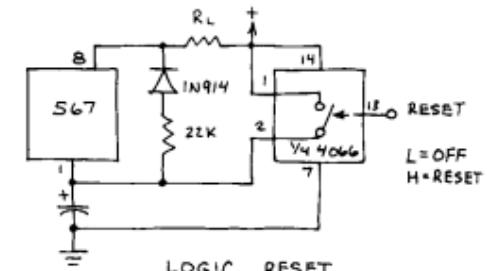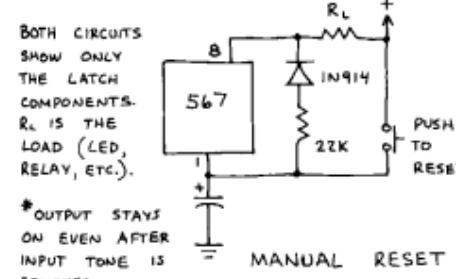


NARROW BAND FREQUENCY DETECTOR

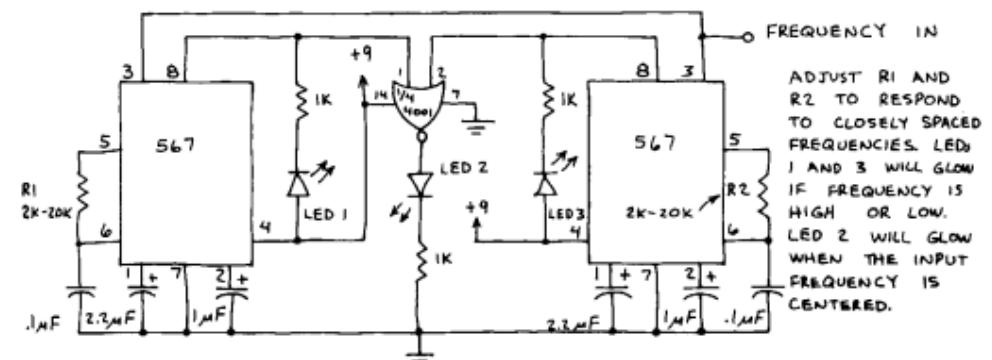

TONE DECODER


567

CONTAINS A PHASE-LOCKED LOOP. PIN 8 GOES LOW WHEN THE INPUT FREQUENCY MATCHES THE CHIP'S CENTER FREQUENCY (f_0). THE LATTER FREQUENCY IS SET BY THE TIMING RESISTOR AND CAPACITOR (R AND C) AND IS $(1/f_0) \div (RC)$. R SHOULD BE BETWEEN 2K-20K. THE 567 CAN BE ADJUSTED TO DETECT ANY INPUT BETWEEN 0.01 Hz TO 500kHz. NOTE: 1 SECOND OR MORE MAY BE REQUIRED FOR THE 567 TO LOCK ON TO LOW FREQUENCY INPUTS! SEE THIS CHIP'S SPECIFICATIONS FOR MORE INFORMATION.

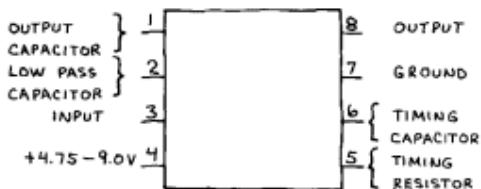


THE VALUE IN MICROFARADS OF THE LOW PASS CAPACITOR SHOULD BE n/f_0 WHERE n RANGES BETWEEN 1300 (FOR UP TO 14 % f_0 DETECTION BANDWIDTH) TO 62,000 (UP TO 2 % f_0 DETECTION BANDWIDTH). THE OUTPUT CAPACITOR SHOULD HAVE ABOUT TWICE THE CAPACITANCE OF THE LOW PASS FILTER CAPACITOR.


BASIC TONE DETECTOR CIRCUIT

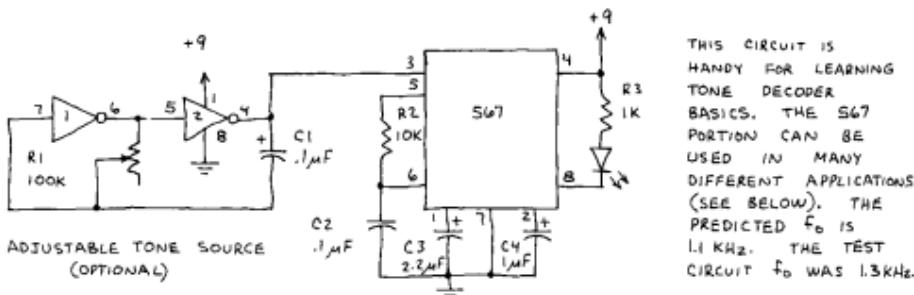

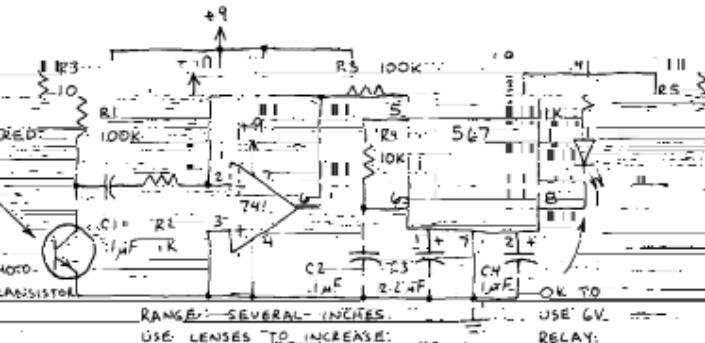INFRARED REMOTE CONTROL SYSTEM TRANSMITTER



RECEIVER

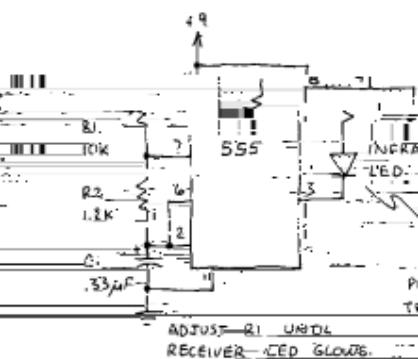

124


1024-BIT STATIC RAM (CONTINUED)

2102L

ADDING PROGRAMMED OR MANUAL JUMP


ADD THESE CONNECTIONS TO THE ADDRESSING CIRCUIT ON FACING PAGE.

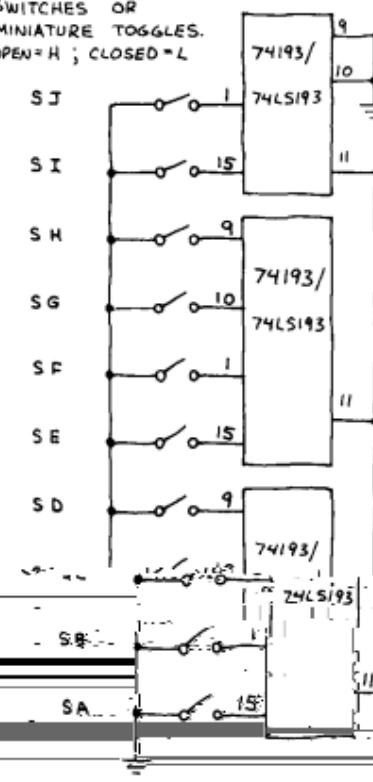SA-SJ: USE
8-POSITION DIP
SWITCHES OR
MINIATURE TOGGLES.
OPEN=H ; CLOSED=L




NORMALLY THE LOAD INPUT IS HIGH, MAKING LOAD LOW LOADS THE ADDRESS PROGRAMMED IN SWITCHES. SA-SJ INTO THE 74193'S. THIS PERMITS A PROGRAMMED JUMP OR A MANUAL JUMP TO ANY ADDRESS.

SINGLE I/O PORT

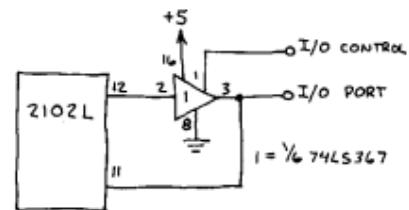

ADD THIS CIRCUIT TO THE ADDRESSING CIRCUIT ON FACING PAGE. WHEN I/O (INPUT/OUTPUT) CONTROL IS H, PIN 3 OF THE 74LS367 ENTERS THIRD STATE (HI-Z) AND I/O PORT ACCEPTS INPUT DATA. WHEN PIN 3 OF THE 74LS367 IS L, I/O PORT OUTPUTS DATA. BOTH THESE OPERATIONS ARE DEPENDENT UPON THE STATUS OF THE 2102L CONTROL INPUTS.

CASCADING 2102L'S

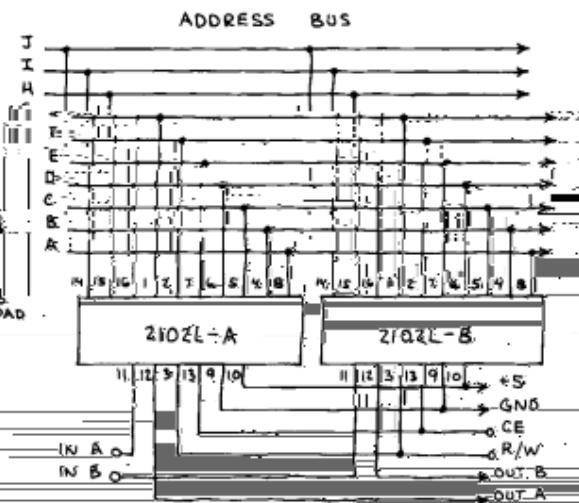


21

1024 x 4-BIT RAM

2114L /4045

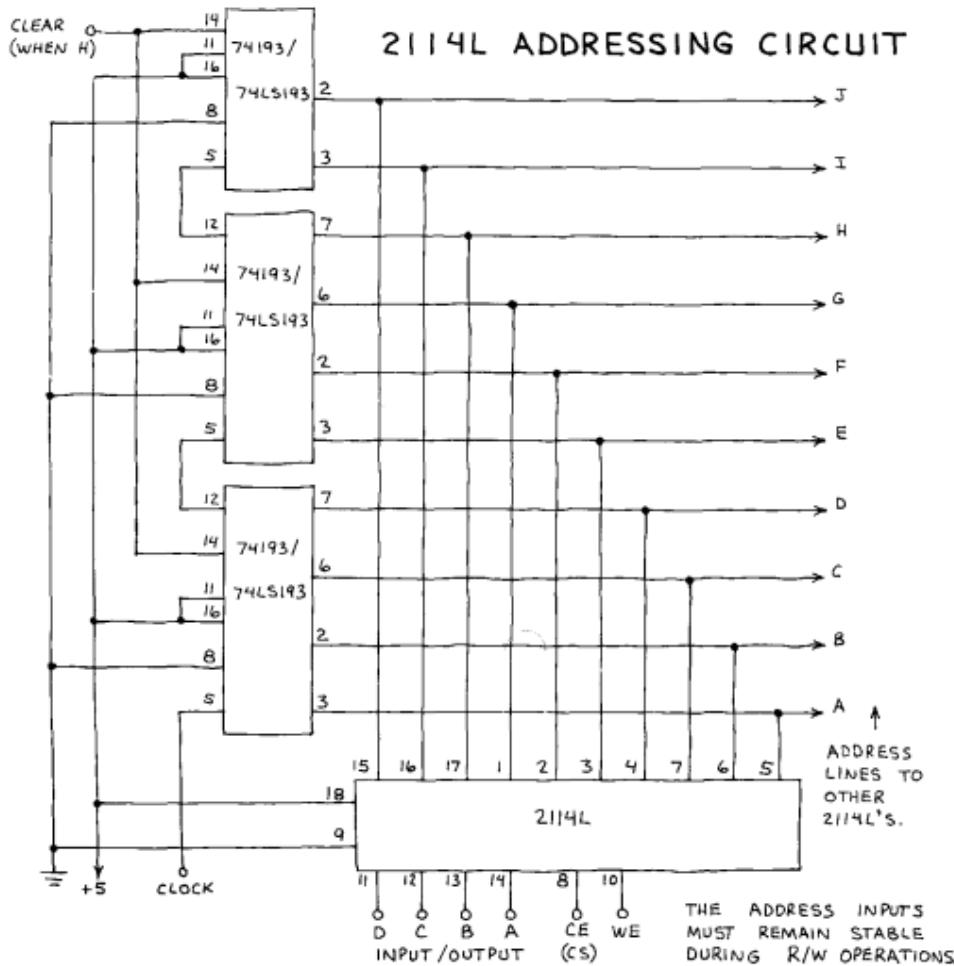1024-4-BIT STORAGE LOCATIONS ADDRESSED BY PINS A0-A9. TTL/LS COMPATIBLE. FOR READ/WRITE OPERATIONS, CE (CHIP ENABLE, ALSO CALLED CHIP SELECT) MUST BE LOW. WE INPUT MUST BE LOW TO WRITE (LOAD) DATA INTO CHIP. WHEN WE IS HIGH, DATA IN ADDRESSED LOCATION APPEARS AT INPUT/OUTPUT PINS. IDEAL CHIP FOR DO-IT-YOURSELF MICROCOMPUTERS AND CONTROLLERS.





PHASE LOCKED LOOP (CONTINUED)

4046

FREQUENCY SYNTHESIZER


SOUND EFFECTS GENERATOR

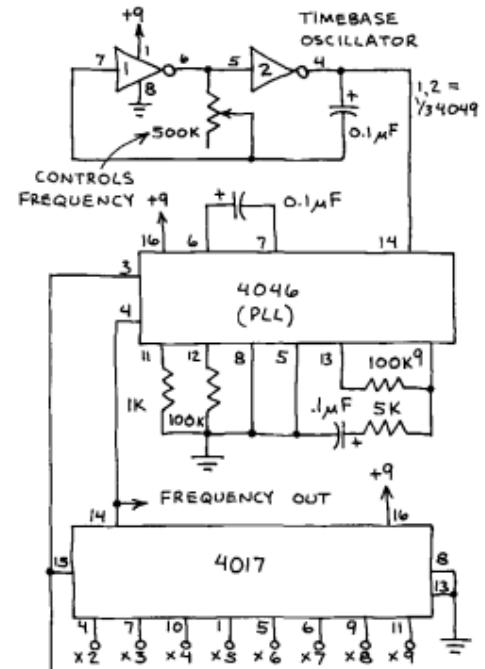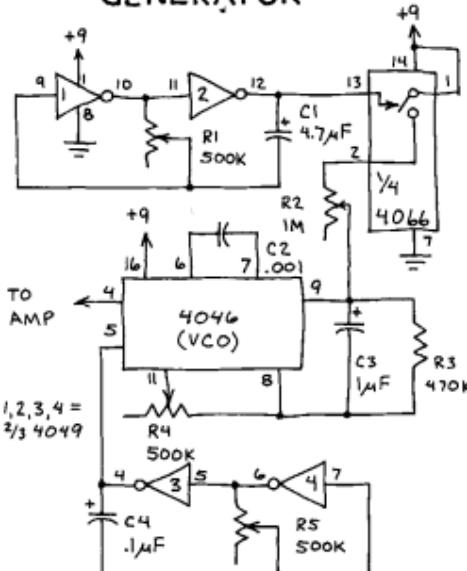

PRODUCES FASCINATING VARIETIES OF UNDULATING AND CHOPPED TONES.
R1 CONTROLS CYCLE TIME. R2 CONTROLS DELAY TIME. R4 CONTROLS FREQUENCY RANGE. R5 CONTROLS CHOPPING RATE. CHANGING R5'S SETTING GIVES MOST DRAMATIC RESULTS.


TONE BURST GENERATOR

LOCK INDICATOR *

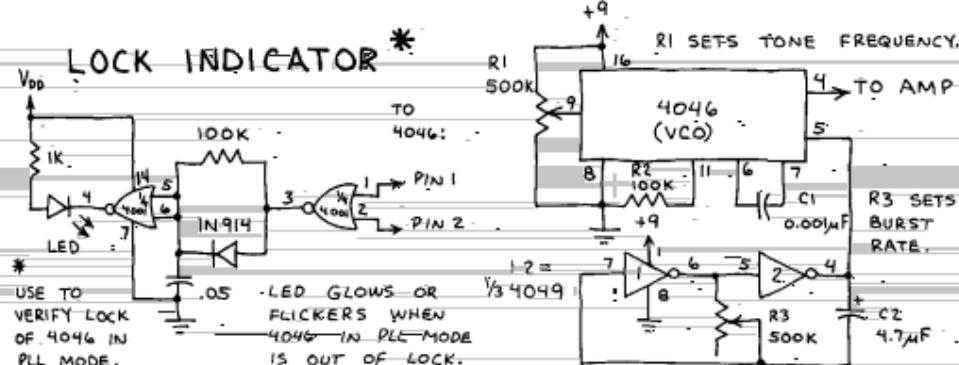

PHASE-LOCKED LOOP (PLL) 4046

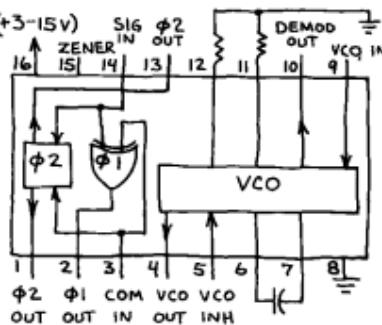
EXCEPTIONALLY VERSATILE CHIP. CONTAINS TWO PHASE COMPARATORS AND VOLTAGE CONTROLLED OSCILLATOR (VCO). USE VCO AND ONE PHASE COMPARATOR TO MAKE PLL. CIRCUITS ON THIS PAGE USE VCO ONLY.



SPEAKER AMPLIFIER*




CHIRP BURST SEQUENCER

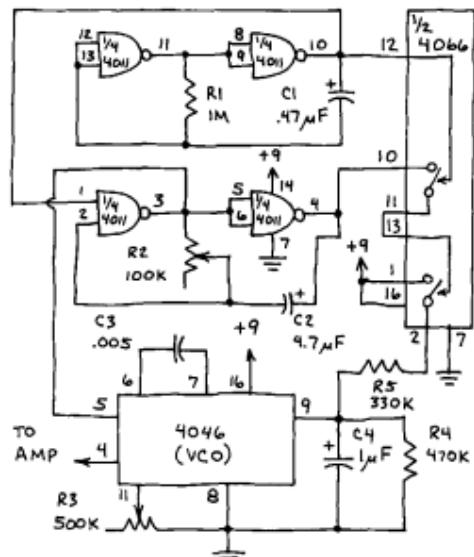


R2: ADJUST FOR 1-4 CHIRPS PER CYCLE.
CHIRPS WILL HAVE DIFFERENT FREQUENCIES.

R3: CONTROLS PITCH OF CHIRPS.
FOR TONES INSTEAD OF CHIRPS,
CONNECT TO PIN 12 INSTEAD OF PIN 11.

TUNABLE OSCILLATOR

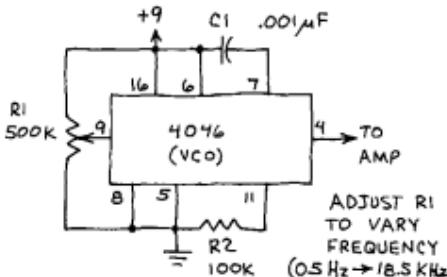

SIREN

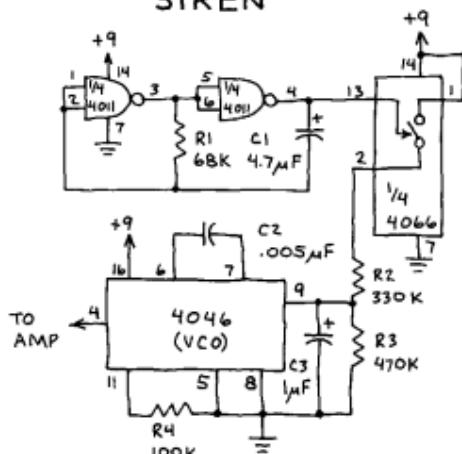

CHANGE R1 OR C1 TO ALTER CYCLE TIME.
CHANGE R4 OR C2 TO ALTER FREQUENCY.
CHANGE R3 OR C3 TO ALTER WAIL.


1024 × 4-BIT RAM (CONTINUED)

2114L / 4045

1024-NIBBLE

DATA LOADING CIRCUIT

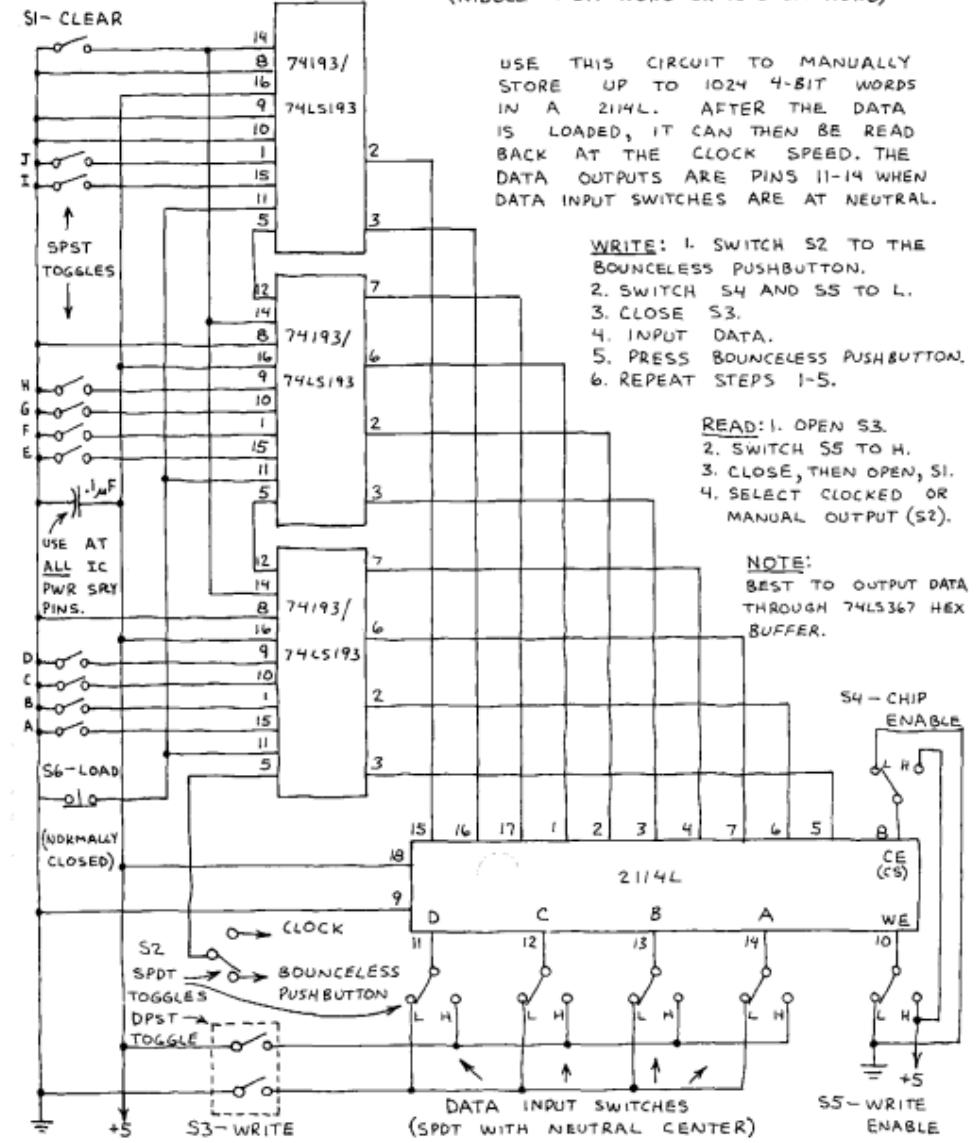
(NIBBLE = 4-BIT WORD OR $\frac{1}{2}$ 8-BIT WORD)




DUAL D FLIP-FLOP

4013

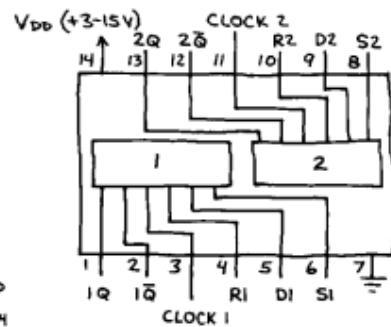
VERY VERSATILE PAIR OF D-TYPE FLIP-FLOPS. GROUND UNUSED INPUTS.




1-OF-4 SEQUENCER

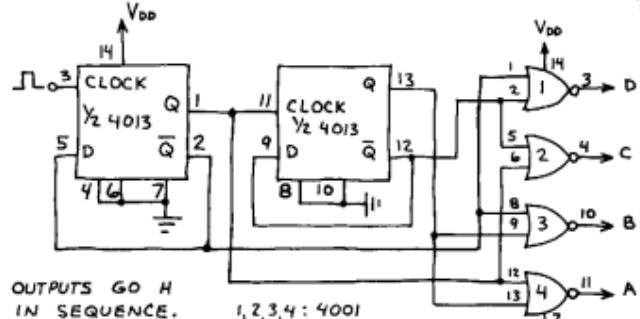


DIVIDE-BY-2

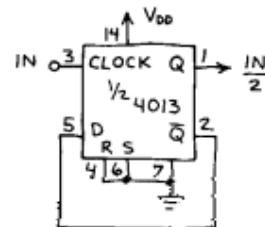

MODULO-8 COUNTER

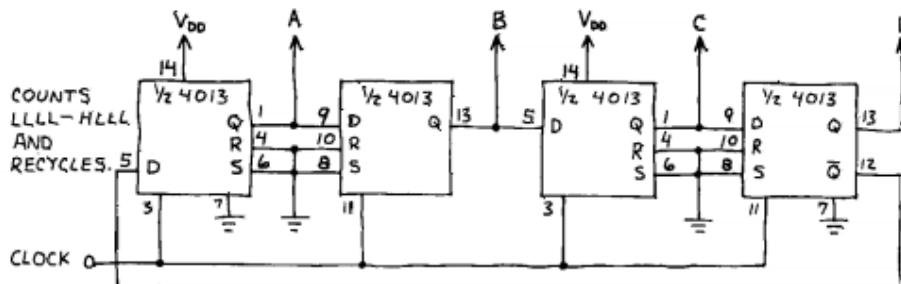

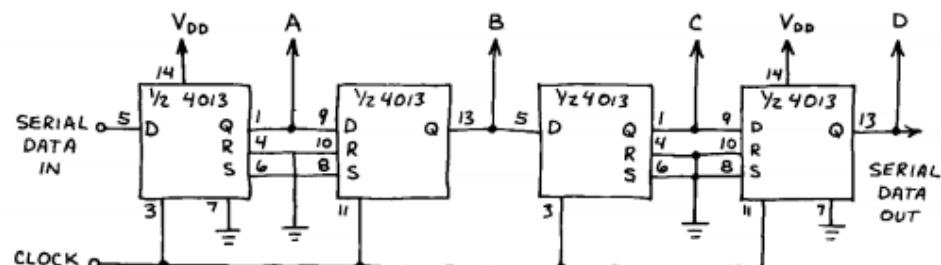
SERIAL IN/OUT, PARALLEL OUT SHIFT REGISTER



PHASE-LOCKED LOOP


565

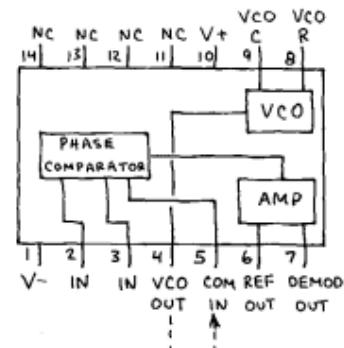SOPHISTICATED ANALOG SYSTEM THAT AUTOMATICALLY TRACKS A FLUCTUATING INPUT SIGNAL. VOLTAGE CONTROLLED OSCILLATOR (VCO) FREQUENCY IS CONTROLLED BY OUTPUT VOLTAGE FROM PHASE COMPARATOR. THIS CAUSES VCO FREQUENCY TO MOVE TOWARD INPUT SIGNAL. THE COMPARATOR VOLTAGE OUTPUT IS AMPLIFIED AND AVAILABLE FOR COMMUNICATIONS APPLICATIONS... AS SHOWN BELOW.




PULSE-FREQUENCY-MODULATED INFRARED COMMUNICATOR

TRANSMITTER

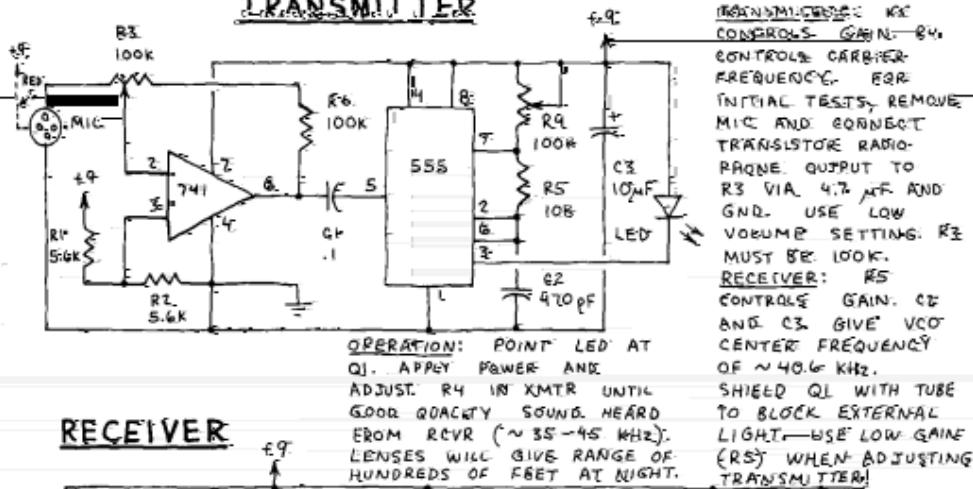


RECEIVER

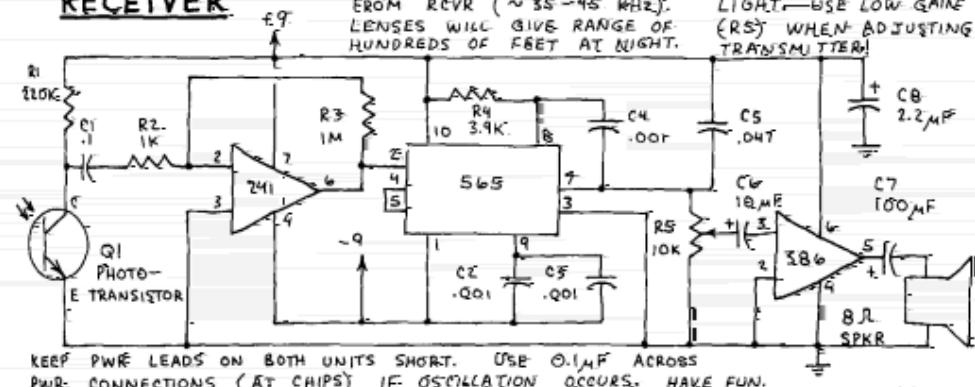


TIMER 7555

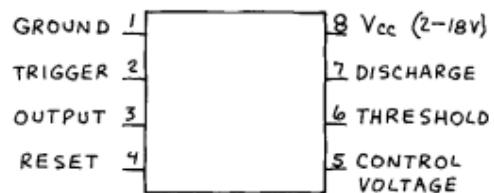CMOS VERSION OF THE 555. VERY LOW POWER CONSUMPTION. WIDER SUPPLY VOLTAGE RANGE. LONGER TIMING CYCLES. CAUTION: APPLY POWER TO 7555 BEFORE CONNECTING EXTERNAL CIRCUIT.




FREQUENCY METER

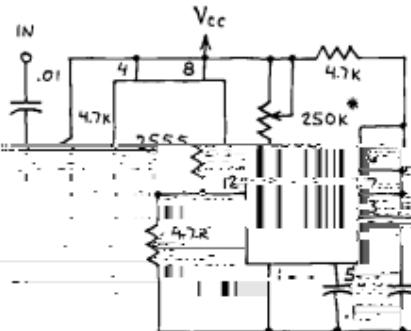


*CALIBRATE
INPUT MUST BE
SQUARE-WAVE.

LIGHT PROBE FOR BLIND

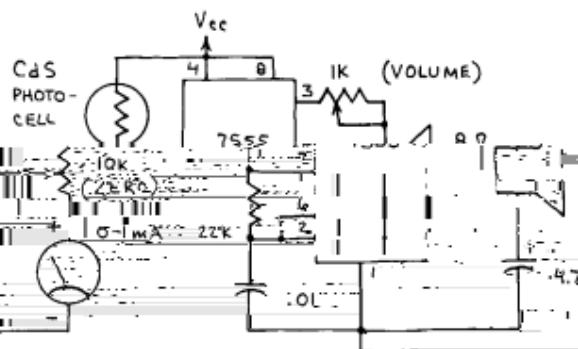


EVENT FAILURE ALARM

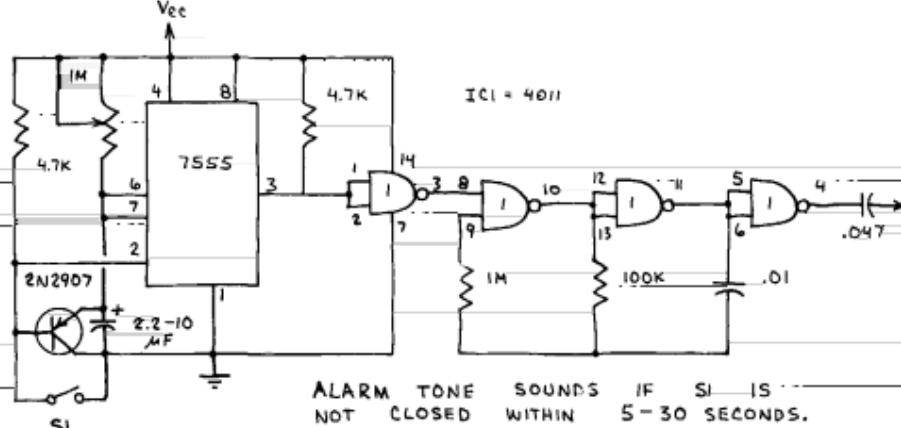


DUAL JK FLIP FLOP 4027

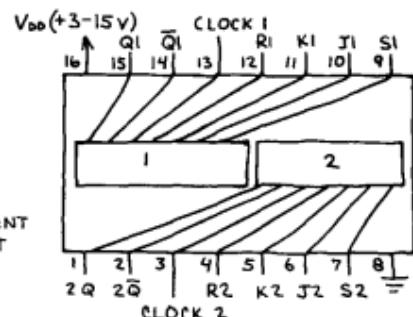
USE FOR DIVIDERS, COUNTERS AND REGISTERS. S (SET) AND R (RESET) INPUTS MUST BE LOW FOR CLOCKING TO OCCUR. MAKING S OR R HIGH SETS OR RESETS FLIP-FLOP INDEPENDENT OF CLOCK. IMPORTANT: ALL INPUTS MUST GO SOMEWHERE!




DIVIDE-BY-2 COUNTER

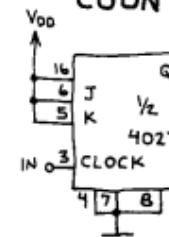


DIVIDE-BY-5 COUNTER

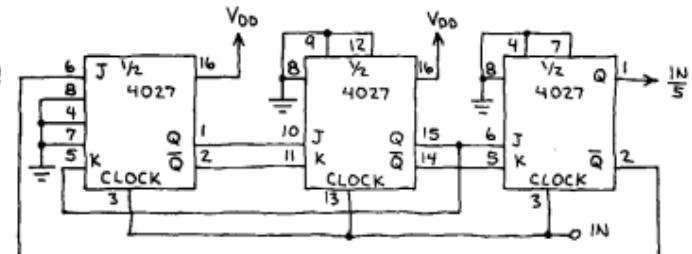


DIVIDE-BY-3 COUNTER

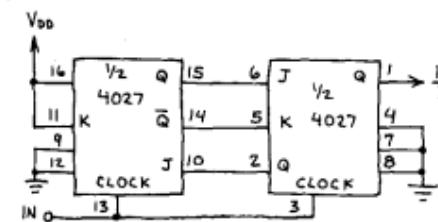

DIVIDE-BY-4 COUNTER

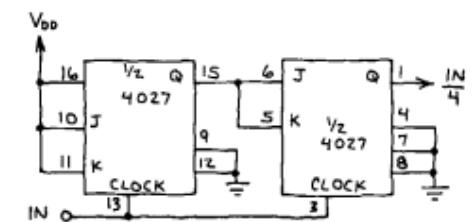



4-BIT SERIAL SHIFT REGISTER

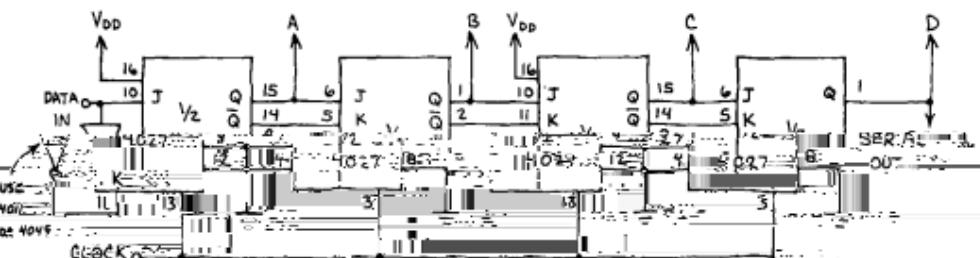

QUAD LATCH 4042

FOUR BISTABLE LATCHES.
CAN BE USED AS A
4-BIT DATA REGISTER.
ALL FOUR LATCHES ARE
CLOCKED SIMULTANEOUSLY.
POLARITY PIN PROVIDES
CLOCKING FLEXIBILITY.


4-BIT DATA LATCH

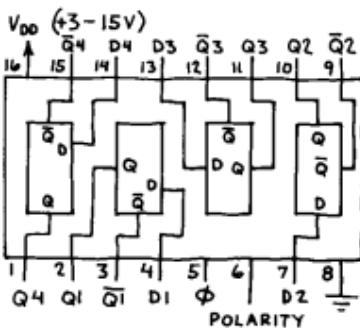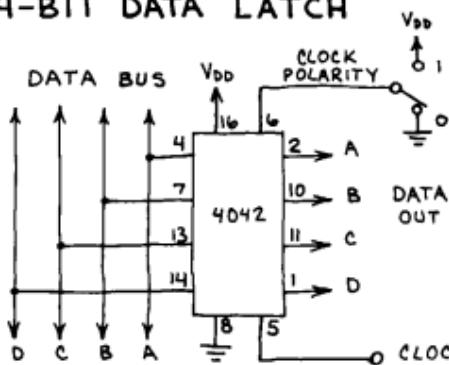

CLOCK	POLARITY	Q
0	0	LATCH
0	1	D
1	0	D
1	1	LATCH

DATA ON BUS AT OUTPUTS. DATA IS LATCHED (SAVED) WHEN CLOCK SWITCHES.


STEPPED WAVE GENERATOR

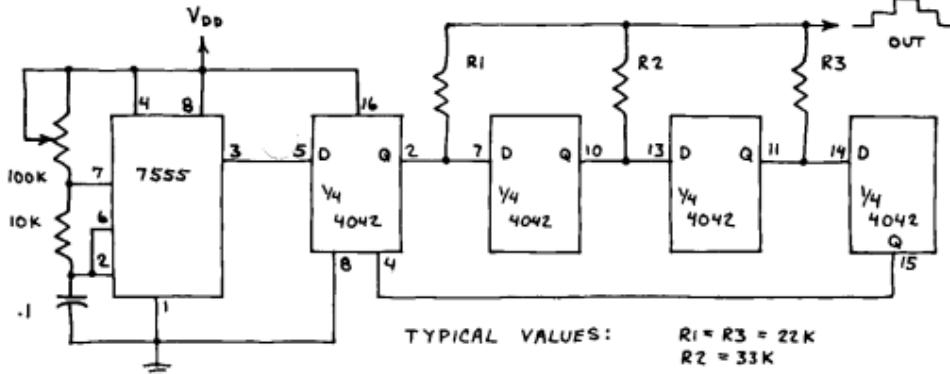

TYPICAL VALUES:
 $R_1 = R_3 = 22\text{k}$
 $R_2 = 33\text{k}$


QUAD TIMER (CONTINUED) 558

FULLY ADJUSTABLE PULSE GENERATOR

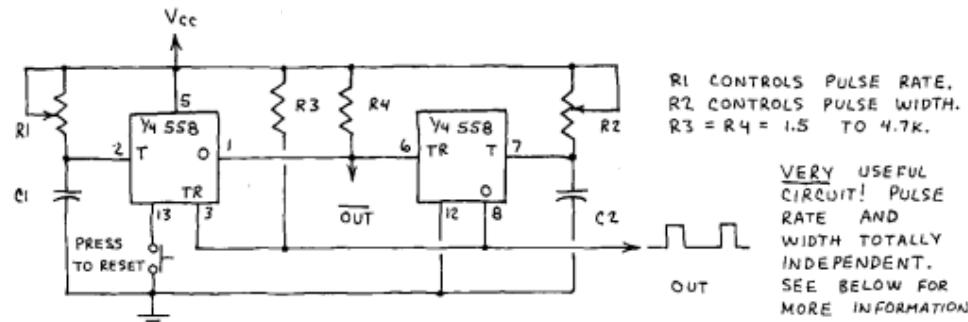


VERY USEFUL CIRCUIT! PULSE RATE AND WIDTH TOTALLY INDEPENDENT. SEE BELOW FOR MORE INFORMATION

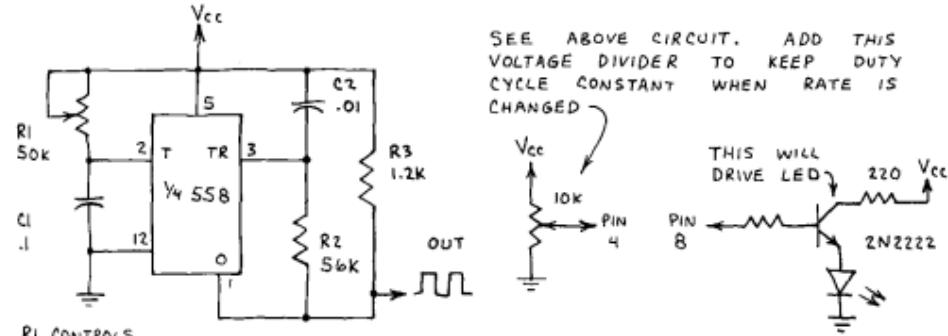SIMPLE OSCILLATOR FIXED DUTY CYCLE PULSER



LONG DURATION TIMER

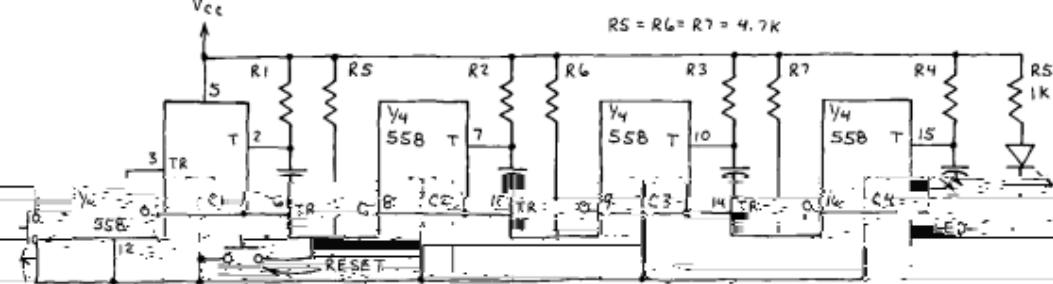


PUSH TO START
SELECT $R_1, R_2, R_3, R_4, C_1, C_2, C_3, C_4$ TO GIVE DESIRED DELAY PER STAGE. DELAY = $R \times C$. TOTAL DELAY = SUM OF ALL STAGES. LED TURNS ON AFTER TIME DELAY AND TURNS ON AGAIN.


QUAD TIMER

558

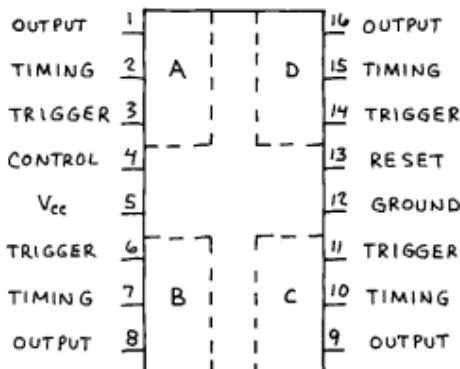
CONTAINS FOUR INDEPENDENT MONOSTABLE TIMERS. EACH TIMER IS SIMILAR TO PART OF A 555 TIMER. ASTABLE OPERATION POSSIBLE WITH ONE TIMER. $V_{cc} = +4.5$ TO 18 VOLTS! CONTROL AND RESET PINS ARE COMMON.




BASIC TIMER

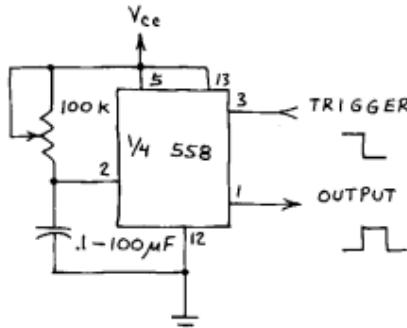

ONE-SHOT

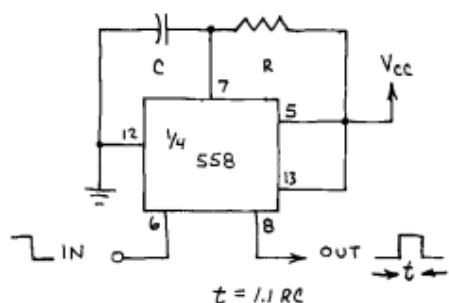

PROGRAMMABLE SEQUENCER

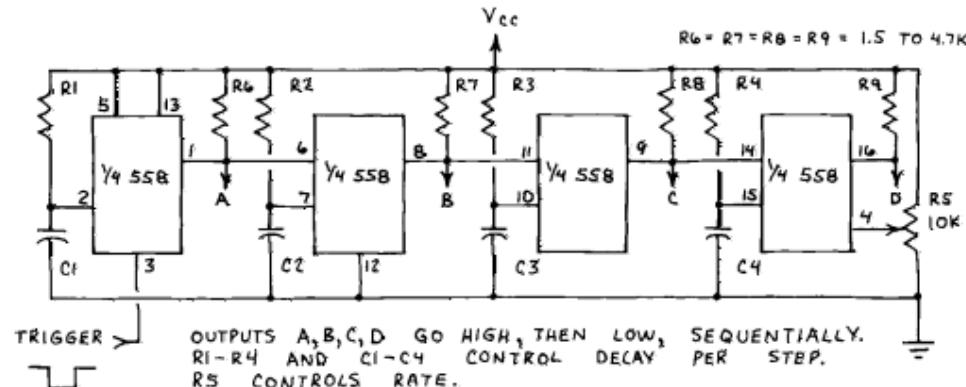


118


DUAL ONE-SHOT

4528

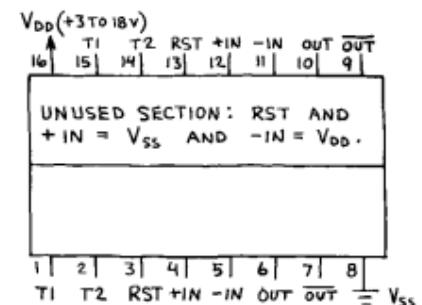
TWO FULLY INDEPENDENT MONOSTABLE MULTIVIBRATORS. BOTH CAN BE RETRIGGERED. TRIGGER CAN BE RISING OR FALLING EDGE OF PULSE. T1 AND T2 ARE TIMING INPUTS. RST IS RESET AND ±IN ARE TRIGGER INPUTS.




POSITIVE ONE-SHOT

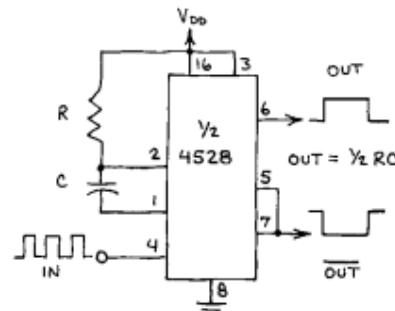

PULSE DELAYER

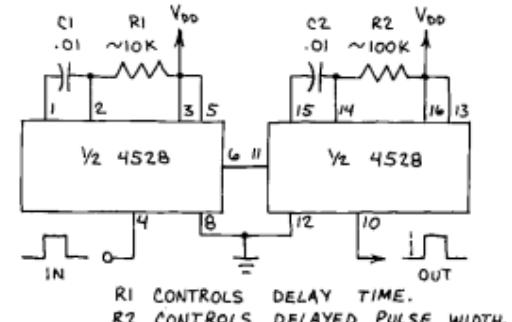


STEPPED TONE GENERATOR

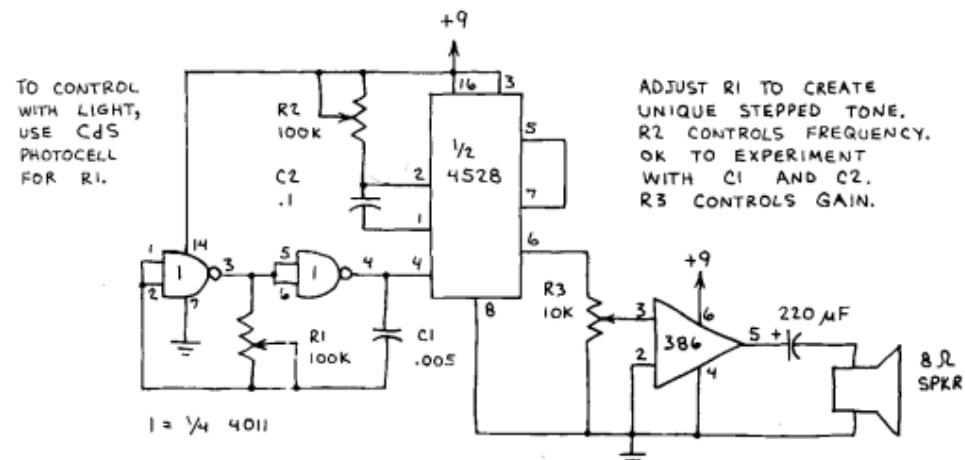

27



14-STAGE BINARY COUNTER 4020

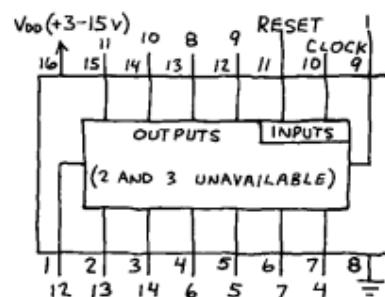A RIPPLE COUNTER WITH CARRY OUTPUT. THE 14-STAGE BINARY COUNT IS COMPLETED IN 16,384 CLOCK PULSES. THIS MAKES POSSIBLE VERY LONG DURATION TIMERS, ASSUMING THE OUTPUTS ARE DECODED. THE OUTPUTS REQUIRE A BRIEF SETTLING TIME AFTER EACH CLOCK PULSE.



14-BIT BINARY COUNTER

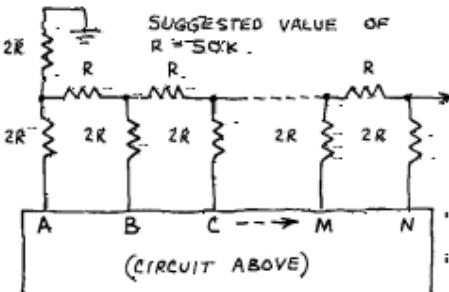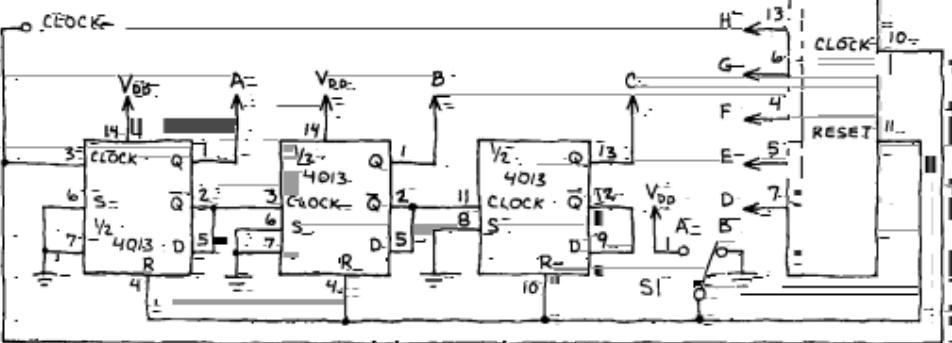THE SECOND AND THIRD OUTPUTS OF STANDARD 8-BIT DECADE 4020'S ARE NOT AVAILABLE. THIS CIRCUIT INCORPORATES A 3-BIT COUNTER TO SUPPLY THE MISSING OUTPUTS. #15 IS THE LOWEST ORDER OUTPUT.



STAIRCASE GENERATOR


ANALOG
OUTPUT

OUTPUT IS A STEPPED VOLTAGE. APPLICATIONS INCLUDE ANALOG-TO-DIGITAL CONVERSION AND WAVEFORM SYNTHESIS.


DUAL TIMER (CONTINUED) 556

TWO-STAGE TIMER

SOUND SYNTHESIZER

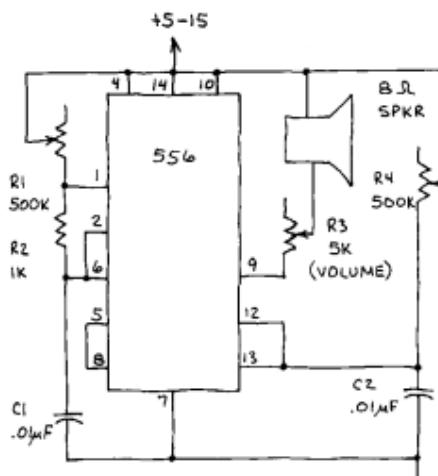


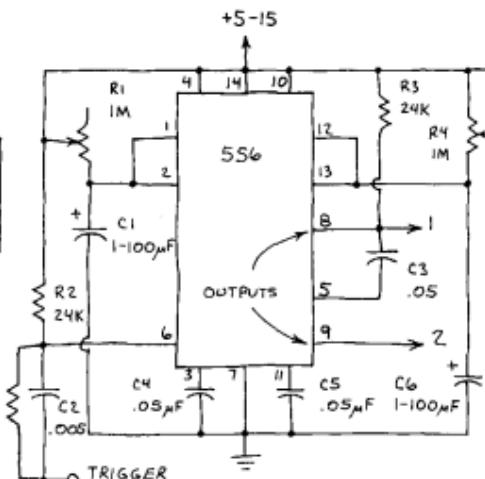THIS CIRCUIT IS AN OSCILLATOR FOLLOWED BY A FREQUENCY DIVIDER. ADJUST R1 AND R4 FOR VERY UNUSUAL SOUND EFFECTS.



BOTH TIMERS ARE IN ONE-SHOT MODE. GROUNDING THE TRIGGER INPUT INITIATES THE FIRST TIMER'S CYCLE TIME. THE SECOND TIMER'S CYCLE BEGINS AFTER THE FIRST IS COMPLETE.

PROGRAMMABLE 4-STATE TONE GENERATOR

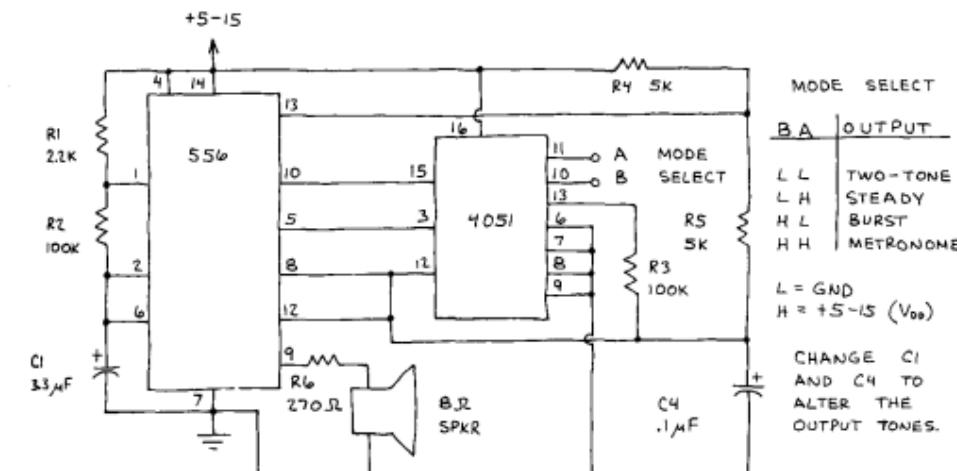

MODE SELECT

BA | OUTPUT

L L TWO-TONE

L H STEADY

H L BURST

H H METRONOME

L = GND


H = +5-15 (Vdd)

CHANGE C1
AND C4 TO
ALTER THE
OUTPUT TONES.

DUAL TIMER


556

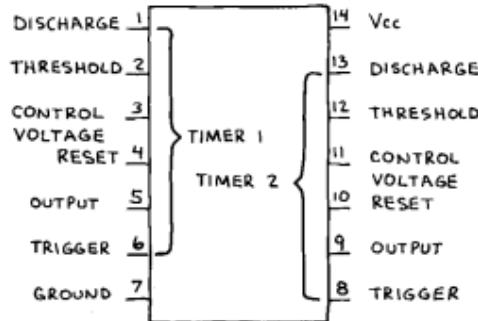CONTAINS TWO INDEPENDENT TIMERS ON A SINGLE CHIP. BOTH TIMERS ARE IDENTICAL TO THE 555. ALL THE APPLICATION CIRCUITS CAN ALSO BE BUILT WITH TWO 555'S. THIS PIN CROSS REFERENCE WILL SIMPLIFY SUBSTITUTING TWO 555'S FOR A 556 OR HALF A 556 FOR A 555:




FUNCTION	555	556(1)	556(2)
GROUND	1	7	7
TRIGGER	2	6	8
OUTPUT	3	5	9
RESET	4	4	10
CONTROL V	5	3	11
THRESHOLD	6	2	12
DISCHARGE	7	1	13
Vcc	8	14	14

INTERVAL TIMER

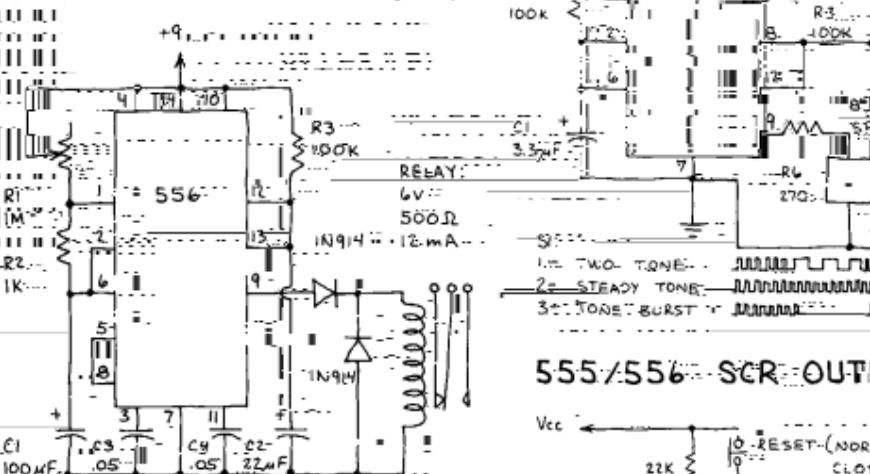

TIMER 1 IS CONNECTED AS ASTABLE OSCILLATOR. TIMER 2 IS A ONE-SHOT RELAY DRIVER. 1 FIRES 2 ONCE EACH CYCLE. 2 PULLS RELAY IN FOR 3-5 SECONDS.


555/556 SCR OUT

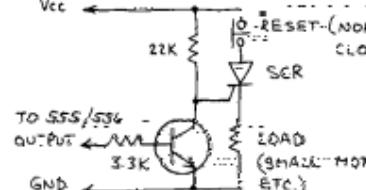


DUAL BCD COUNTER

4518

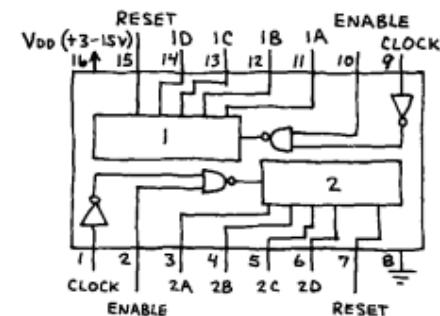TWO SYNCHRONOUS DECADE COUNTERS IN ONE PACKAGE. WHEN ENABLE IS HIGH AND RESET IS LOW, EACH COUNTER ADVANCES ONE COUNT PER CLOCK PULSE.




CASCADED BCD COUNTERS

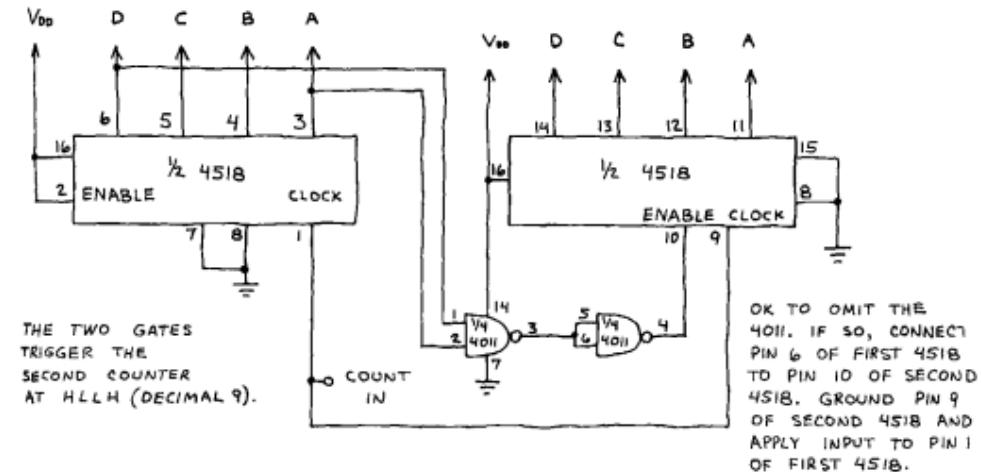

BCD KEYBOARD ENCODER

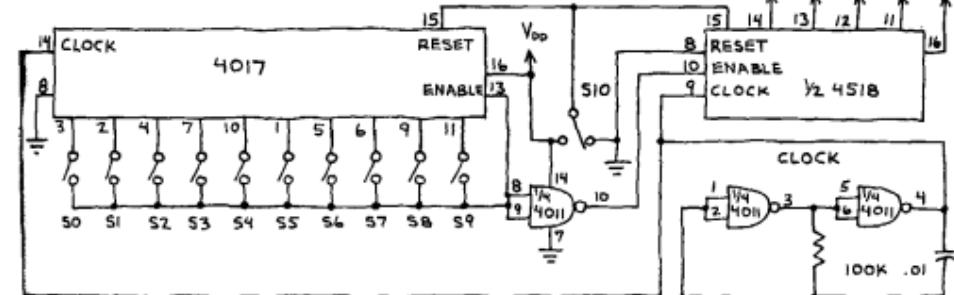
PRESS S0-S9, THEN TOGGLE RESET SWITCH S0 TO Vdd AND BACK TO GROUND. BCD EQUIVALENT OF SELECTED KEY (S0-S9) APPEARS → D C B A Vdd




DECADE COUNTER/DIVIDER 4017

SEQUENTIALLY MAKES 1-OF-10 OUTPUTS HIGH (OTHERS STAY LOW) IN RESPONSE TO CLOCK PULSES. MANY APPLICATIONS. COUNT TAKES PLACE WHEN PINS 13 AND 15 ARE LOW.



RANDOM NUMBER GENERATOR

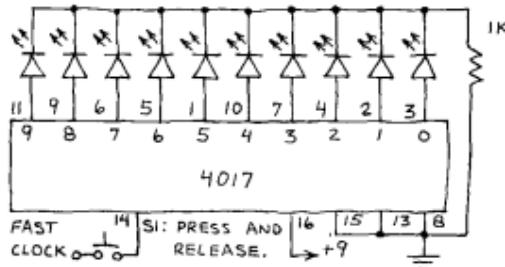


COUNT TO N AND HALT

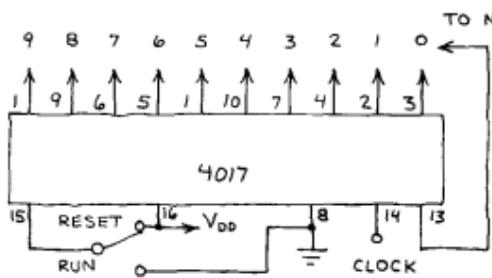

COUNT TO N AND RECYCLE

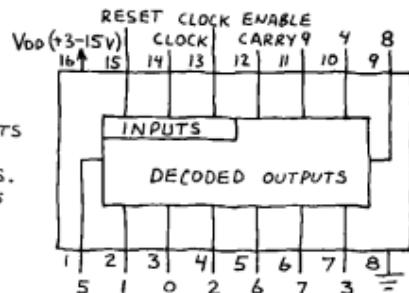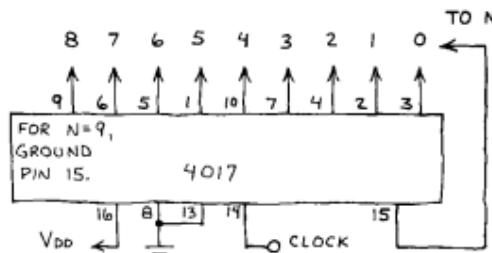


0-99 COUNTER

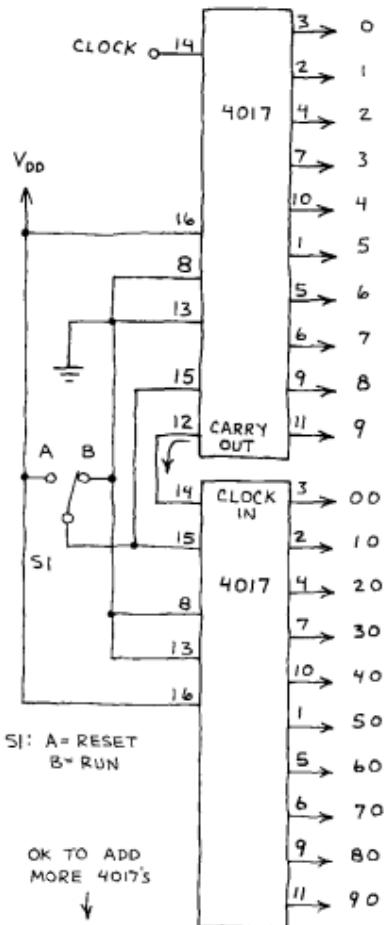


TIMER (CONTINUED) 555


NEON LAMP POWER SOURCE

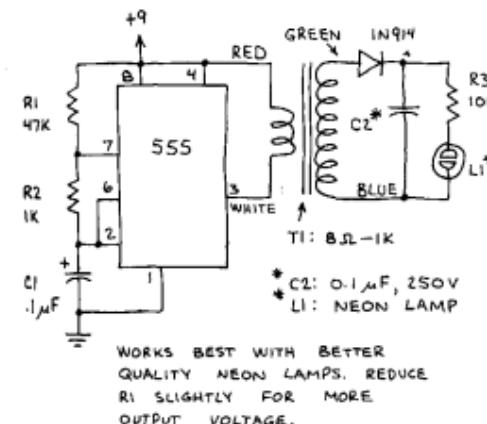

FREQUENCY DIVIDER

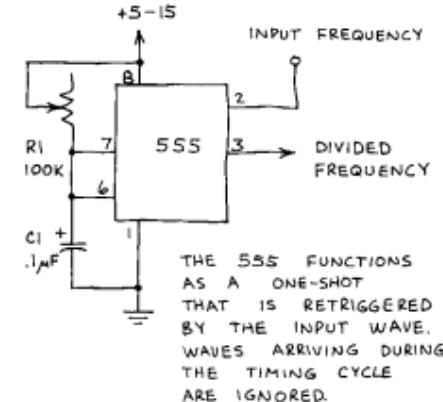

ONE-SHOT TONE BURST

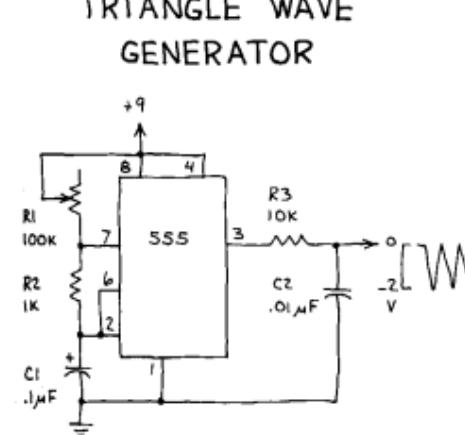


ADJUST R1 TO PROVIDE UP TO 10 KHz. OUTPUT FREQUENCY THIS HIGH PRODUCES CLOSELY SPACED TRIANGLE WAVES. THE WAVES ARE SEPARATED AT SLOWER FREQUENCIES (VVVV).

PRESS SI AND STEADY OUTPUT FREQUENCY APPEARS AT PIN 3. RELEASE SI AND OUTPUT FREQUENCY CONTINUES UNTIL C2 IS DISCHARGED BY R4. INCREASE C2 (OR R4) TO INCREASE LENGTH OF THE BURST. CHANGE FREQUENCY OF TONE BURST VIA R2 OR C1.


TIMER (CONTINUED)

555

ULTRA-LONG TIME DELAY

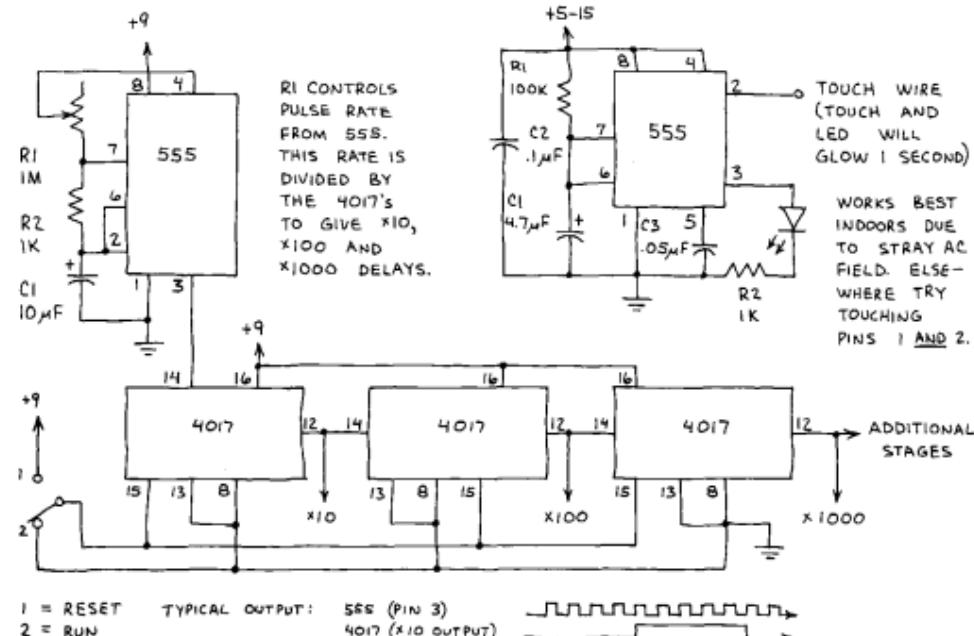


LIGHT DETECTOR

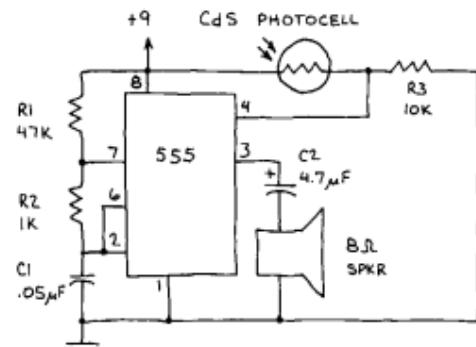

PRODUCES WARNING TONE WHEN LIGHT STRIKES PHOTOCELL. MAKES A GOOD OPEN DOOR ALARM FOR REFRIGERATOR OR FREEZER.


TOUCH SWITCH

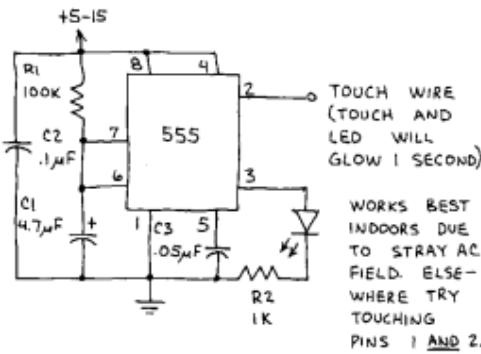


DECADE COUNTER/DIVIDER (CONTINUED)

4017

BCD KEYBOARD ENCODER

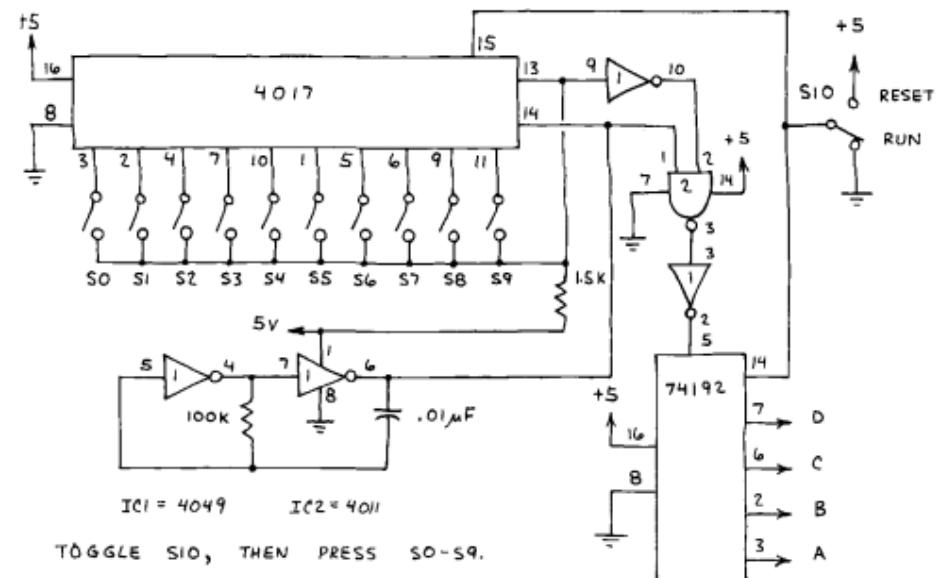

FREQUENCY DIVIDER

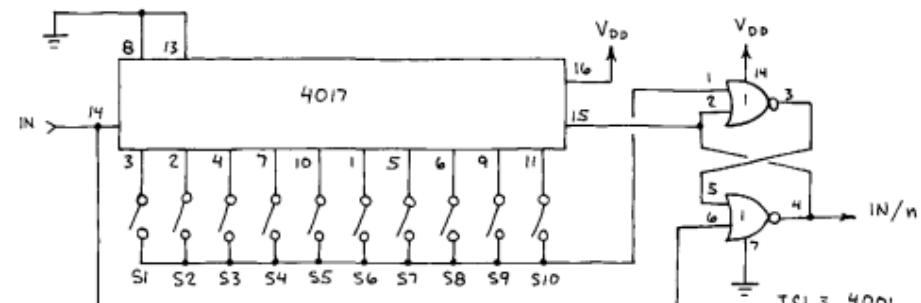


CLOSE S1-S10 TO DIVIDE FREQUENCY BY FROM 1 TO 10.


3-DIGIT BCD COUNTER

MC14553

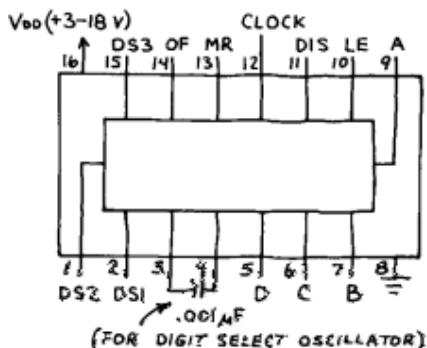
COMPLETE 3-DIGIT COUNTER. USE FOR DO-IT-YOURSELF EVENT AND FREQUENCY COUNTERS. BEGINNERS: GET SOME PRACTICAL CIRCUIT EXPERIENCE BEFORE USING THIS CHIP. PIN EXPLANATIONS: DS (DIGIT SELECT) 1, 2, 3 - SEQUENTIALLY STROBES READOUTS. LE - LATCH ENABLE (WHEN H). DIS - INHIBITS INPUT WHEN H. CLOCK - INPUT. MR - MASTER RESET (WHEN H). OF - OVERFLOW. A, B, C, D - BCD OUTPUTS.



3-DIGIT EVENT COUNTER

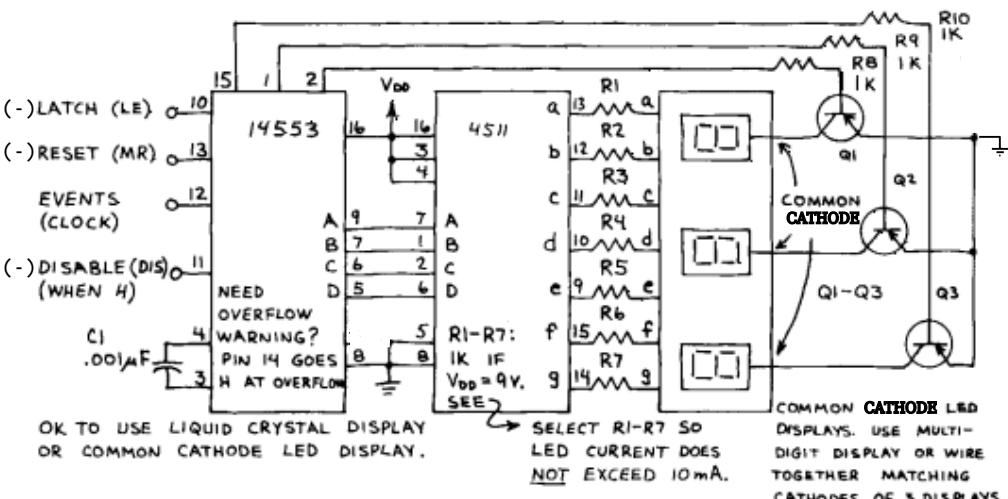


6-DIGIT FREQUENCY COUNTER

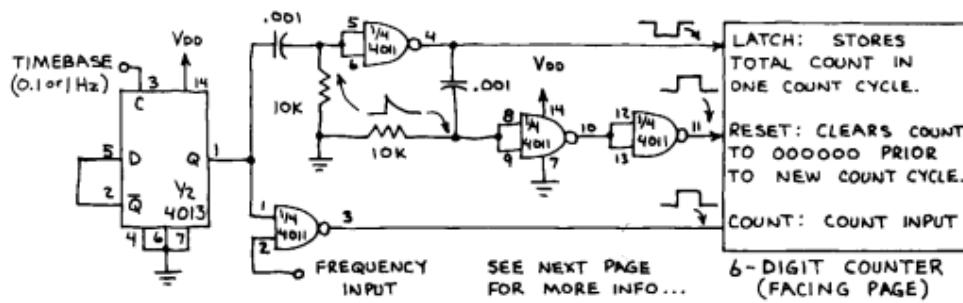


TIMER (CONTINUED)

555

LED TRANSMITTER

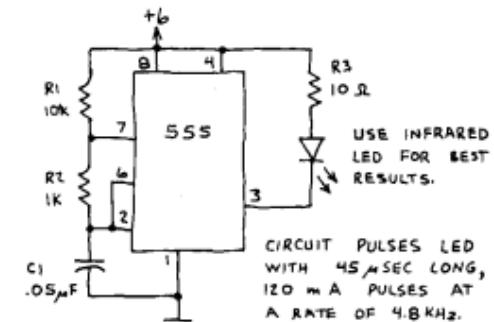

TOY ORGAN

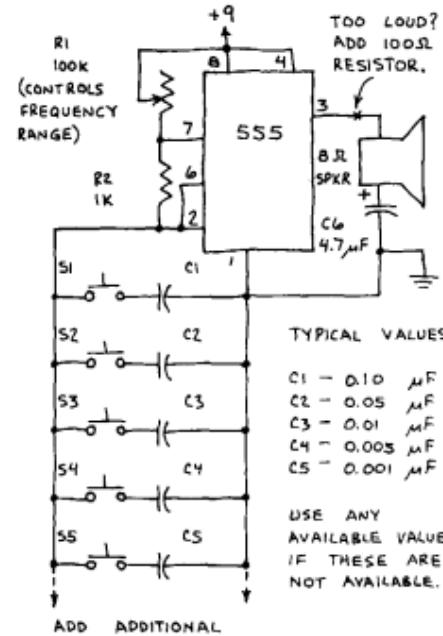

TYPICAL VALUES:


C1 = 0.10 μF
C2 = 0.05 μF
C3 = 0.01 μF
C4 = 0.005 μF
C5 = 0.001 μF

USE ANY AVAILABLE VALUES IF THESE ARE NOT AVAILABLE.

ADD ADDITIONAL STAGES IF DESIRED.
SWITCHES ARE NORMALLY OPEN PUSHBUTTONS.

USE TO SUPPLY CLOCK PULSES TO TTL AND LS LOGIC CIRCUITS. RI CONTROLS PULSE REPETITION RATE.

MISSING PULSE DETECTOR

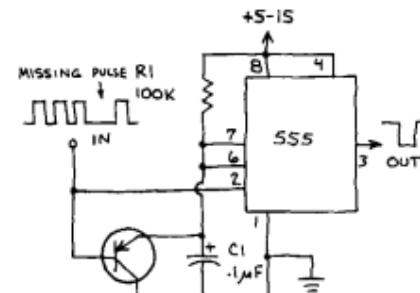


THIS CIRCUIT IS A ONE-SHOT THAT IS CONTINUALLY RETRIGGERED BY INCOMING PULSES. A MISSING OR DELAYED PULSE THAT PREVENTS RETRIGGERING BEFORE A TIMING CYCLE IS COMPLETE CAUSES PIN 3 TO GO LOW UNTIL A NEW INPUT PULSE ARRIVES. RI AND CI CONTROL RESPONSE TIME. USE IN SECURITY ALARMS, CONTINUITY TESTERS, ETC.

TIMER 555


THE FIRST AND STILL THE MOST POPULAR IC TIMER CHIP. OPERATES AS A ONE-SHOT TIMER OR AN ASTABLE MULTIVIBRATOR. THE 555 IS TWO 555 CIRCUITS ON ONE CHIP.

555 EQUIVALENT CIRCUIT

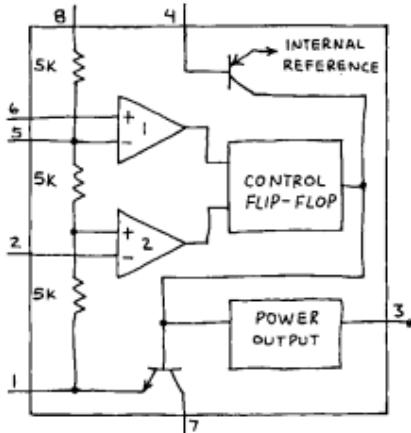


1 AND 2 ARE COMPARATORS. CIRCUIT CAN BE MADE FROM INDIVIDUAL PARTS AS SHOWN... BUT 555 IS MUCH SIMPLER.


ONE-SHOT TIMER

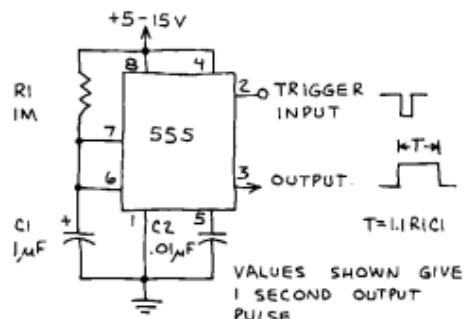


VALUES SHOWN GIVE 1 SECOND OUTPUT PULSE.

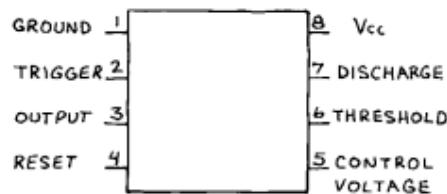

BOUNCELESS SWITCH

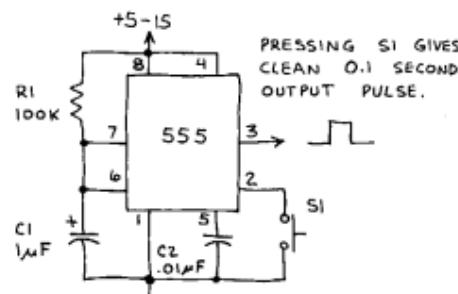


TIMER PLUS RELAY

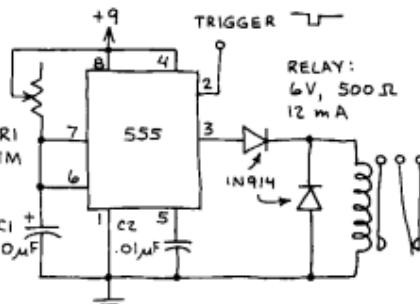

VALUES OF R₁ AND C₁ SHOWN WILL PULL RELAY IN FOR UP TO ABOUT 1.1 SECONDS. USE POINTER KNOB AND PAPER SCALE TO HELP CALIBRATE CIRCUIT. USES INCLUDE DARKROOM TIMING. CIRCUIT CAN BE TRIGGERED BY A NEGATIVE PULSE OR WITH A PUSHBUTTON SWITCH ACROSS PINS 1 AND 2.

3-DIGIT BCD COUNTER (CONTINUED) MC14553

6-DIGIT COUNTER

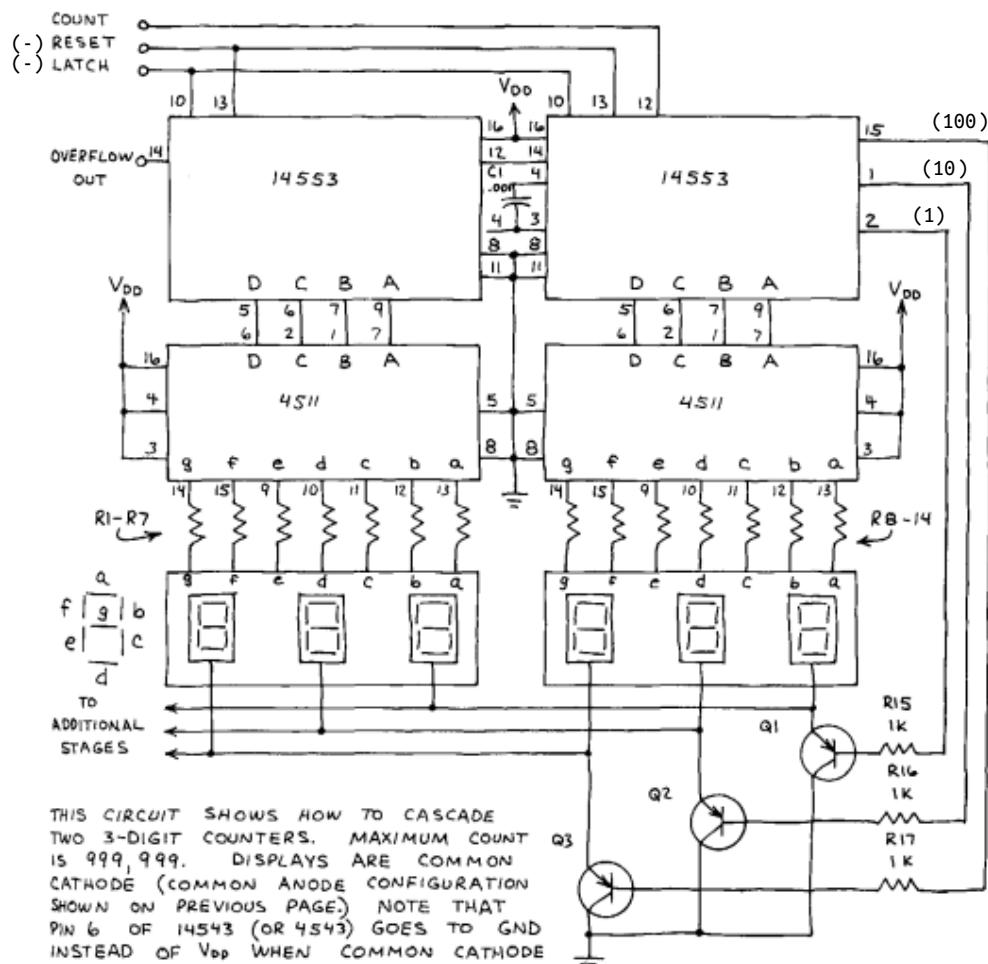


THIS CIRCUIT SHOWS HOW TO CASCADE TWO 3-DIGIT COUNTERS. MAXIMUM COUNT IS 999,999. DISPLAYS ARE COMMON CATHODE (COMMON ANODE CONFIGURATION SHOWN ON PREVIOUS PAGE). NOTE THAT PIN 6 OF 14553 (OR 4543) GOES TO GND INSTEAD OF V_{dd} WHEN COMMON CATHODE DISPLAY IS USED.

FREQUENCY COUNTER:

USE INPUT AND CONTROL CIRCUIT ON PREVIOUS PAGE. INPUT FREQUENCY SHOULD NOT EXCEED V_{dd}. NON-SQUARE WAVE INPUTS MAY REQUIRE INPUT TAILORING. USE COMPARATOR TO SHARPEN SLOW RISING AUDIO SIGNALS.


INPUT BUFFER

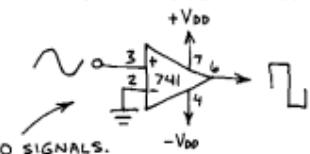


BCD-TO-DECIMAL DECODER

4028

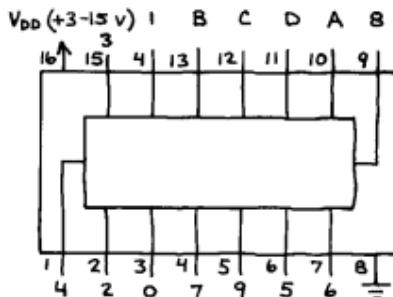DECODES 4-BIT BCD INPUT INTO 1-OF-10 OUTPUTS. SELECTED OUTPUT GOES HIGH; ALL OTHERS STAY LOW. USE FOR DECIMAL READOUTS, SEQUENCERS, PROGRAMMABLE COUNTERS, ETC.



0-9 SECOND TIMER

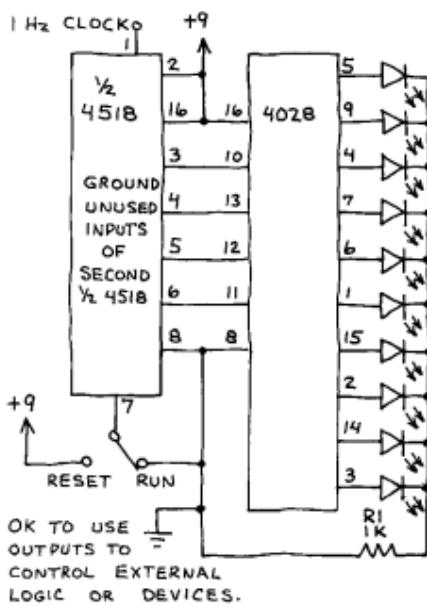


COUNT TO N AND RECYCLE

USE THE ADJACENT CIRCUITS WITH THESE CHANGES:

V_{DD}:

- 1. OMIT 4049
- 2. MAKE PIN 2 HIGH
- 3. USE PIN 7 AS CONTROL INPUT


(4028)

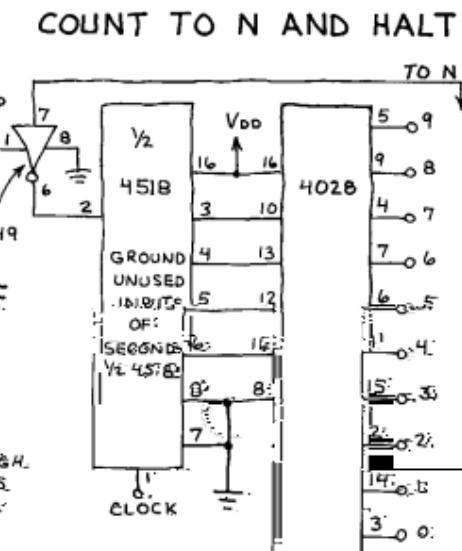


LCD CLOCK MODULE

PCIM-161

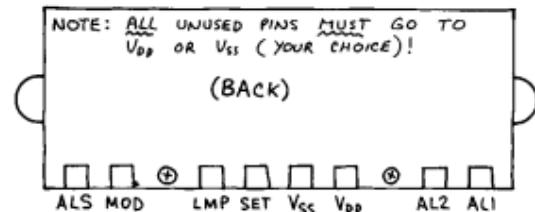COMPLETE CLOCK MODULE.
REQUIRES ONLY 1.5 VOLT
CELL AND SWITCHES.
FOR COMPLETE INFORMATION
SEE DATA SUPPLIED WITH
MODULE. V_{DD} MUST NOT
EXCEED 1.6 VOLTS!




1-OF-8 DECODER

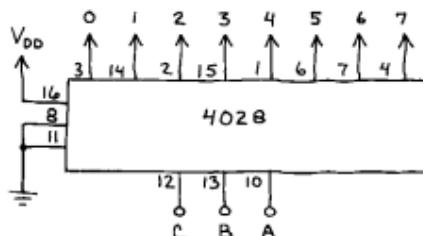


ADDRESS INPUTS

COUNT TO N AND HALT

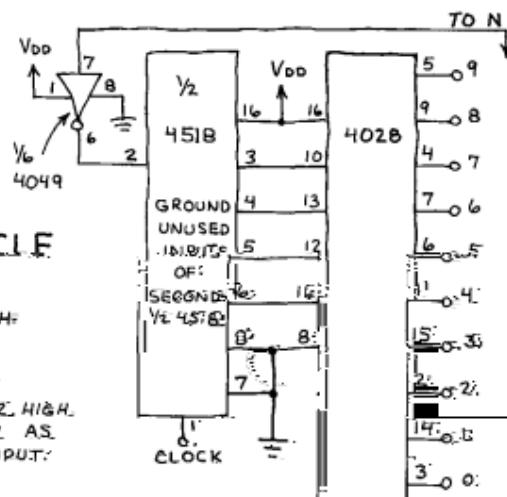



ALARM CLOCK

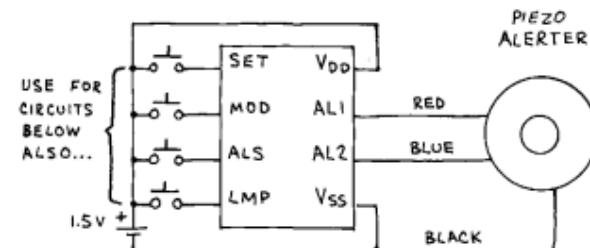


TO SET ALARM:

1. PRESS ALS TWICE; PRESS SET UNTIL HOUR APPEARS.
2. PRESS ALS; PRESS SET UNTIL MINUTES APPEAR.
3. PRESS ALS.

ALARM CLOCK RADIO

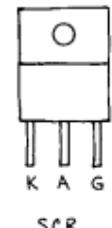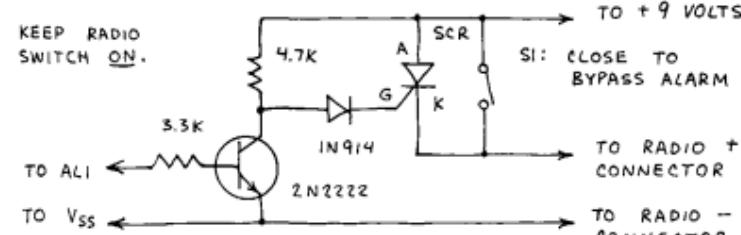

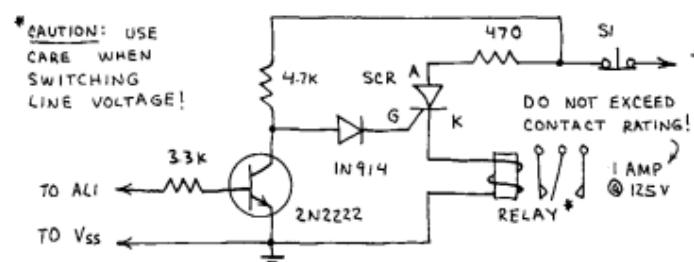CURRENT DRAIN:
RELAY ON = 14.8 mA
RELAY OFF = 1.8 mA




SI: NORMALLY CLOSED PUSHBUTTON,
OPEN (PRESS) TO RESET. MUST WAIT FOR 1/2 SECOND ALARM CYCLE BEFORE RESETTING.

LED VU METER MODULE


NSM3916

INCLUDES LED BARGRAPH DRIVER AND LEDs ON SAME SUBSTRATE. MAKE MODE PIN HIGH FOR BARGRAPH MODE. LEAVE OPEN FOR DOT MODE. SEE DATA SUPPLIED WITH MODULE FOR MORE INFORMATION. ALSO, SEE LM3914 AND LM3915.

VU BAR GRAPH DISPLAY

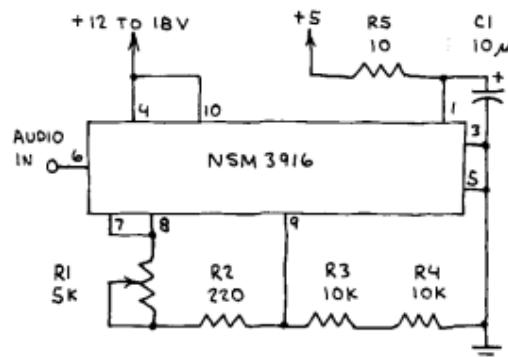


BACK AND FORTH FLASHER

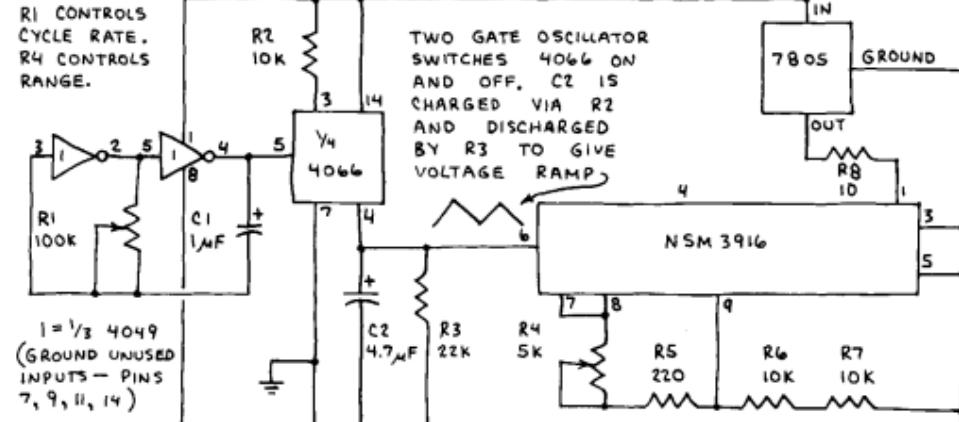


BCD-TO-7-SEGMENT LATCH/DECODER/DRIVER 4511

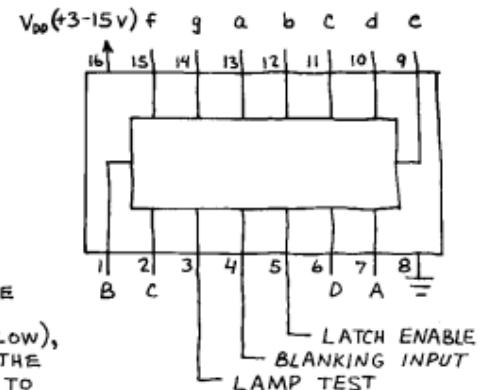CONVERTS BCD DATA INTO FORMAT SUITABLE FOR PRODUCING DECIMAL DIGITS ON 7-SEGMENT LED DISPLAY. INCLUDES BUILT-IN 4-BIT LATCH TO STORE DATA TO BE DISPLAYED (WHEN PIN 5 IS HIGH). WHEN LATCH IS NOT USED (PINS LOW), THE 7-SEGMENT OUTPUTS FOLLOW THE BCD INPUTS. MAKE PIN 4 LOW TO EXTINGUISH THE DISPLAY AND HIGH FOR NORMAL OPERATION. MAKE PIN 3 LOW TO TEST THE DISPLAY AND HIGH FOR NORMAL OPERATION.




DISPLAY FLASHER

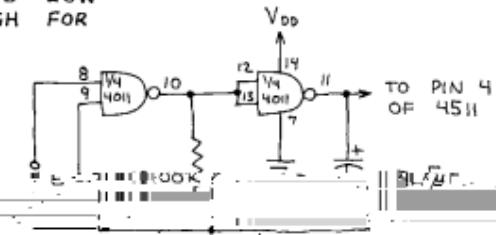DISPLAY FLASHES ONE PER SECOND WHEN E IS HIGH. E FLASHES OFF



DECIMAL COUNTING UNIT (DCU)


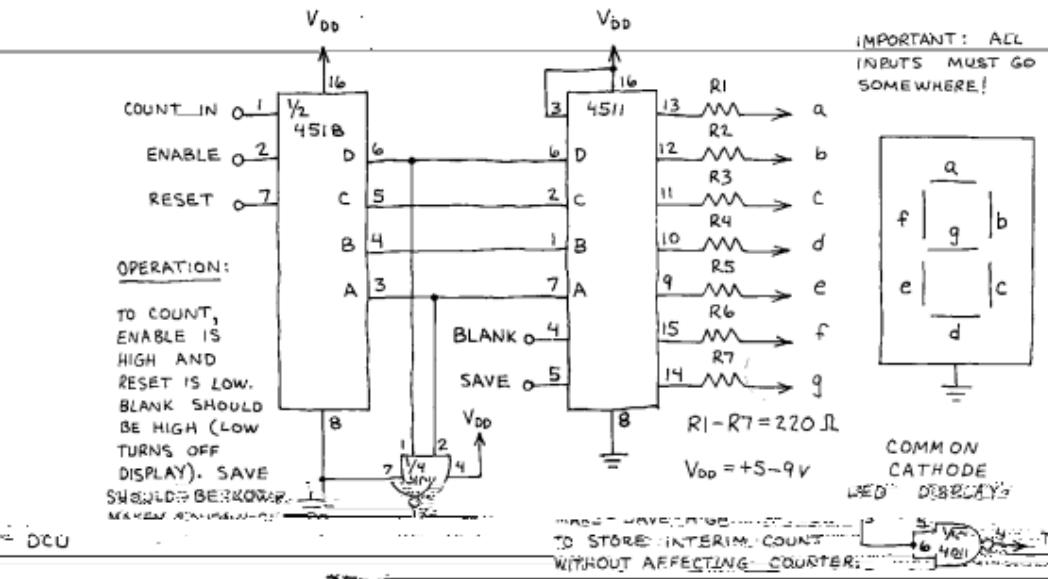


8-STAGE SHIFT REGISTER


4021

PARALLEL INPUT / SERIAL OUTPUT SHIFT REGISTER. ALSO SERIAL INPUT. DATA AT PARALLEL INPUTS IS FORCED INTO THE REGISTER IRRESPECTIVE OF THE CLOCK STATUS WHEN PIN 9 IS MADE HIGH. KEEP PIN 9 LOW FOR NORMAL OPERATION.

PARALLEL-TO-SERIAL DATA CONVERTER

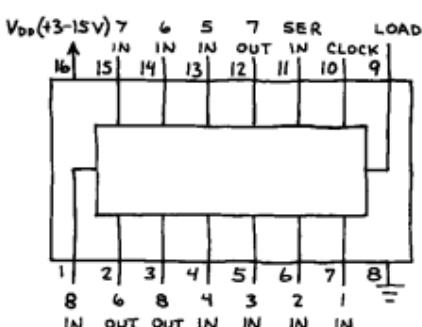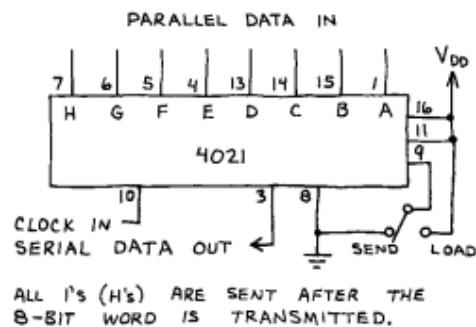


8-STAGE DELAY LINE

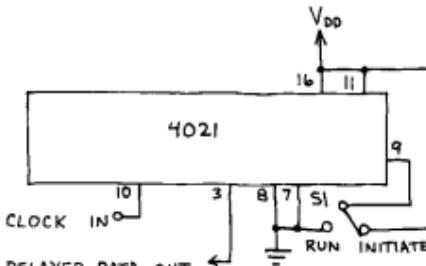

THE FIRST PARALLEL INPUT (PIN 7) IS GROUNDED. THIS LOADS A SINGLE L WHEN SI IS SWITCHED TO INITIATE. THE SINGLE L BIT REACHES THE OUTPUT AFTER 8 CLOCK PULSES.


PSEUDO-RANDOM SEQUENCER

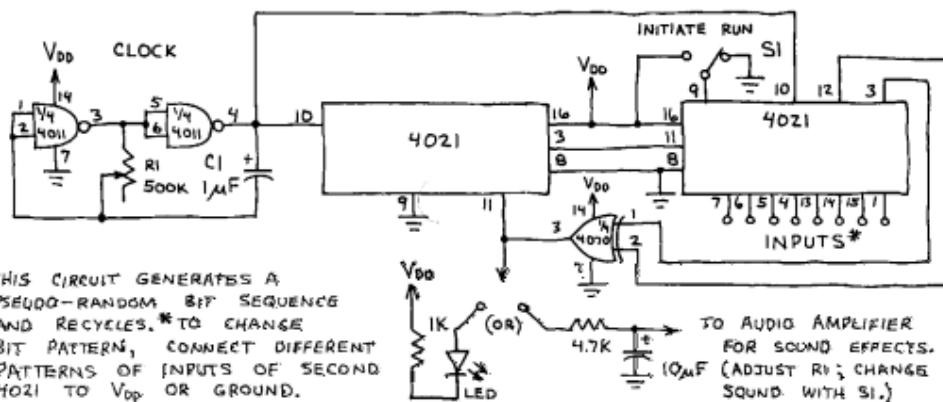

DOT/BAR DISPLAY DRIVER


LM3915N

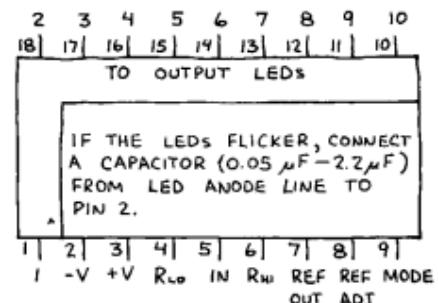LOGARITHMIC VERSION OF THE LM3914N. THE LM3914N USES A STRING OF 1K RESISTORS AS A VOLTAGE DIVIDER WITH LINEARLY SCALED DIVISIONS. THE VOLTAGE DIVIDER RESISTORS OF THE LM3915N ARE SCALED TO GIVE A -3dB INTERVAL FOR EACH OUTPUT. THIS CHIP IS IDEAL FOR VISUALLY MONITORING THE AMPLITUDE OF AUDIO SIGNALS.



SEE LM3914N FOR EXPLANATION OF PIN FUNCTIONS.

0 TO -27 dB DOT/BAR DISPLAY

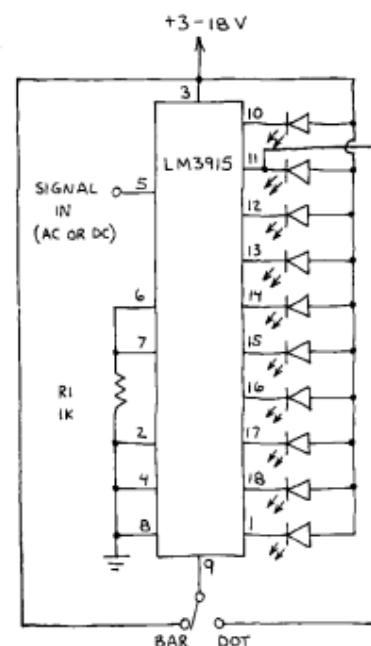

LED DISPLAY

BAR MODE *	
0 dB (FULLSCALE OR FS)	● ● ● ● ● ● ● ●
-3 dB (.707 FS)	● ● ● ● ● ● ● ○
-6 dB (.500 FS)	● ● ● ● ● ● ○ ○ ○
-9 dB (.354 FS)	● ● ● ● ● ○ ○ ○ ○ ○
-12 dB (.250 FS)	● ● ● ● ○ ○ ○ ○ ○ ○ ○
-15 dB (.177 FS)	● ● ● ○ ○ ○ ○ ○ ○ ○ ○ ○
-18 dB (.125 FS)	● ● ○ ○ ○ ○ ○ ○ ○ ○ ○ ○ ○
-21 dB (.088 FS)	● ○ ○ ○ ○ ○ ○ ○ ○ ○ ○ ○ ○ ○
-24 dB (.062 FS)	○ ○ ○ ○ ○ ○ ○ ○ ○ ○ ○ ○ ○ ○ ○
-27 dB (.044 FS)	○ ○ ○ ○ ○ ○ ○ ○ ○ ○ ○ ○ ○ ○ ○ ○


* OK TO USE DOT MODE.

THE INPUT SIGNAL CAN BE CONNECTED DIRECTLY TO PIN 5 WITHOUT RECTIFICATION, LIMITING OR AC COUPLING. SEE THE LM3914N FOR MORE IDEAS AND TIPS.

DOT/BAR DISPLAY DRIVER (CONTINUED)


LM3914N

SOLID-STATE OSCILLOSCOPE

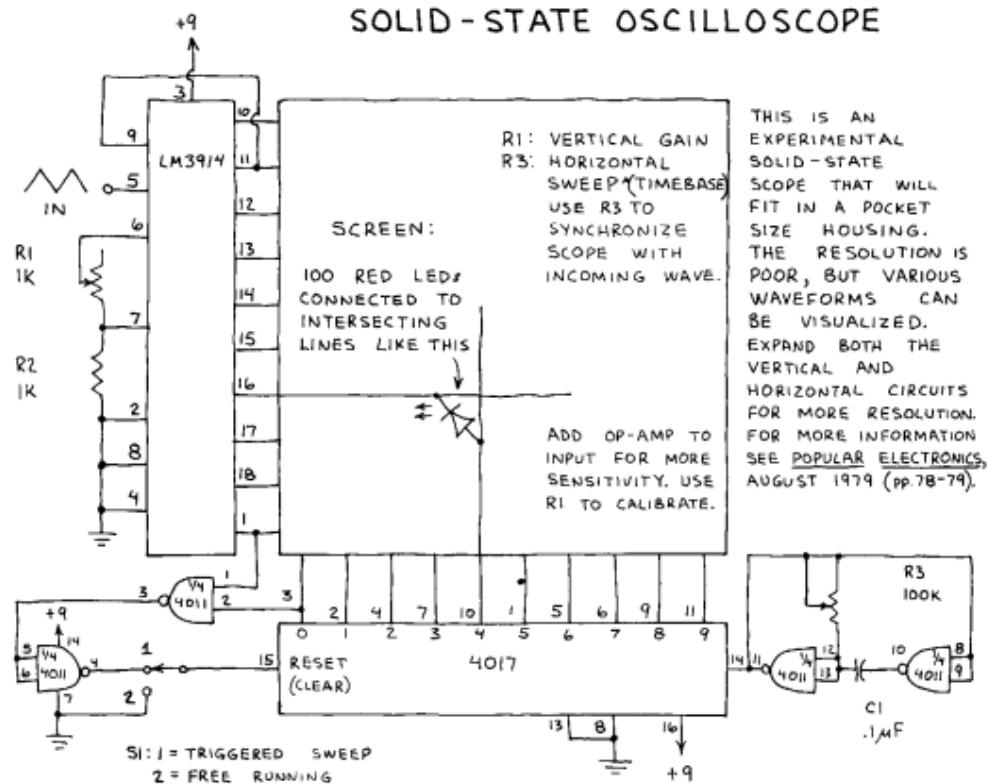


USING THE LM3914 AS A CONTROLLER:

RELAY

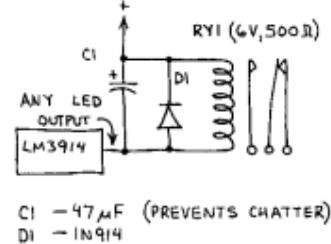


OPTICAL COUPLING

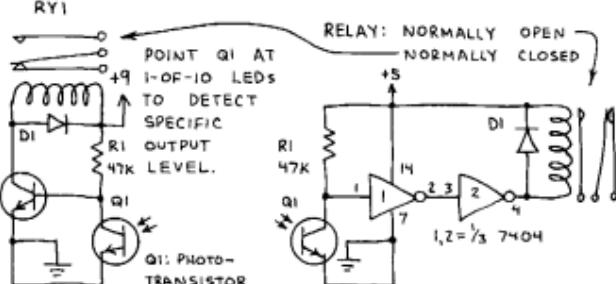


ANALOG MULTIPLEXER

4051

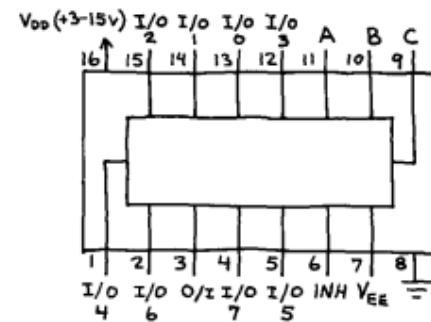


INPUT ADDRESS AT CBA SELLECTS 1-OF-8 ANALOG SWITCHES. SIGNAL AT SELECTED SWITCH I/O (INPUT/OUTPUT) IS THEN APPLIED TO COMMON O/I (OUTPUT/INPUT). THE INPUT SIGNAL MUST NOT EXCEED V_{DD}. THE INHIBIT (INH) INPUT SHOULD BE GROUNDED FOR NORMAL OPERATION. ALL SWITCHES ARE OPEN WHEN INH IS HIGH.

1-OF-8 MULTIPLEXER

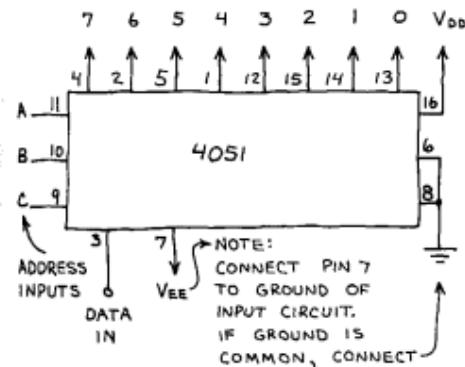


1-OF-8 DATA SELECTOR (DEMULTI/PLEXER)

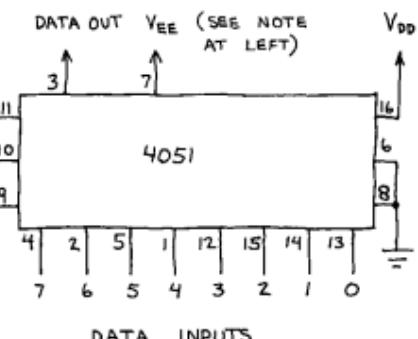

TONE SEQUENCER

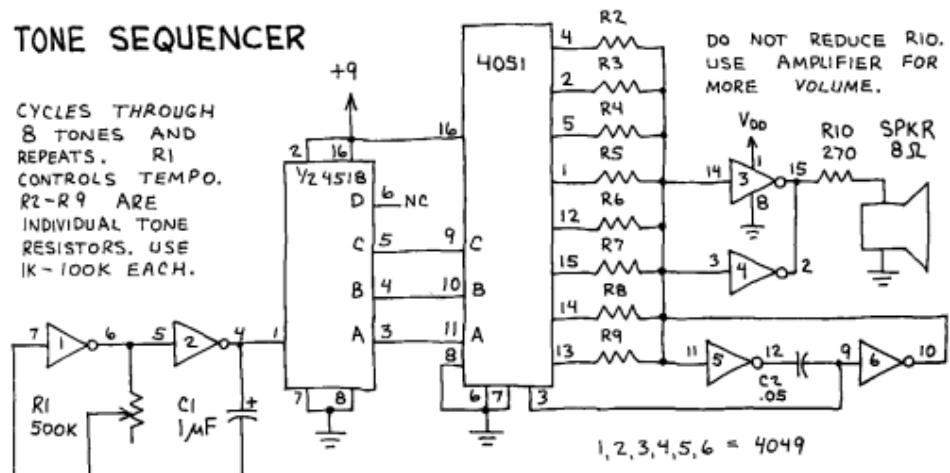
CYCLES THROUGH 8 TONES AND REPEATS. R1 CONTROLS TEMPO. R2-R9 ARE INDIVIDUAL TONE RESISTORS. USE 1K-100K EACH.




60-Hz TIMEBASE

MM5369

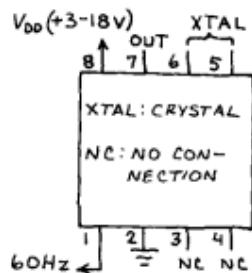PROVIDES PRECISE 60 Hz SQUARE WAVE WHEN USED WITH 3.579545 MHz COLOR TV CRYSTAL. USE FOR MOST DO-IT-YOURSELF TIMERS, CLOCKS, CONTROLLERS, FUNCTION GENERATORS. INSTALL IN SMALL CABINET FOR WORKBENCH PRECISION CLOCK.




60-Hz TIMEBASE

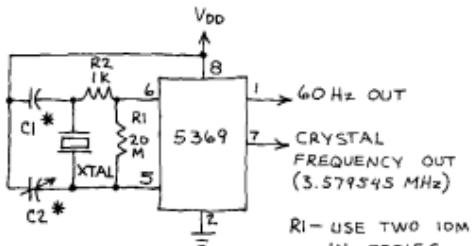


*
MOTOROLA SPECIFIES THAT $C_1 = 30\text{pF}$ AND $C_2 = 6.36\text{ pF}$. OK TO USE SIX 4.7pF CAPACITORS IN PARALLEL OR 47pF CAPACITOR FOR C_1 . TRY TUNABLE CAPACITOR (e.g. 5-50pF) FOR C_2 . TO TUNE, CONNECT FREQUENCY METER TO PIN 7. TUNE C_2 UNTIL FREQUENCY IS 3,579,545 Hz. ACCURACY FAIRLY GOOD EVEN IF YOU DON'T TUNE C_2 .

10-Hz TIMEBASE

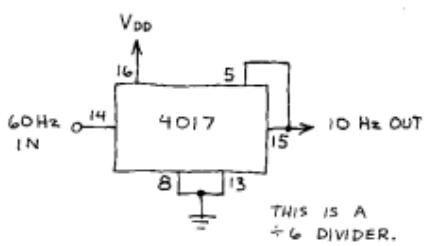


1-Hz TIMEBASE

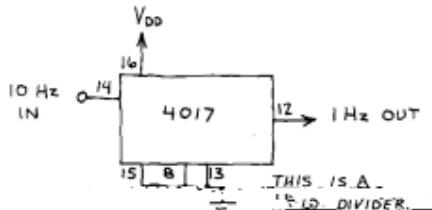

DOT/BAR DISPLAY DRIVER (CONTINUED)

LM3914N

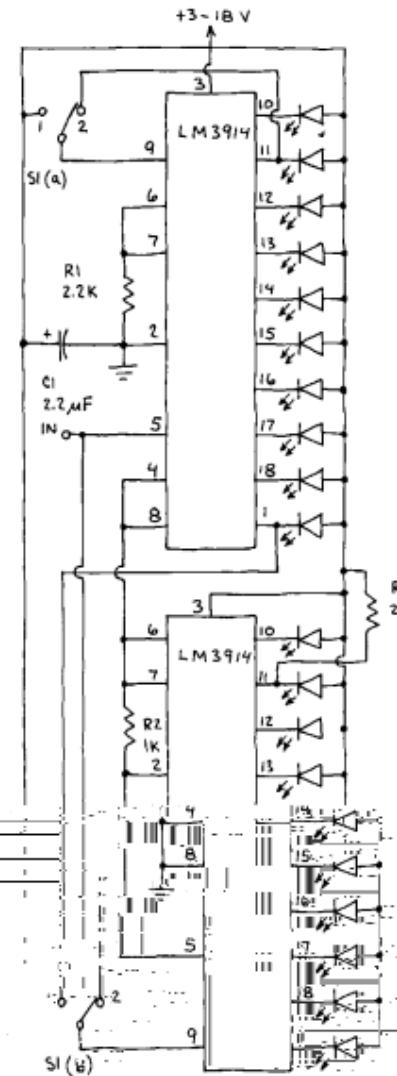


20-ELEMENT READOUT

THIS CIRCUIT SHOWS HOW TO CASCADE 2 OR MORE LM3914'S. WHEN +V = 5 VOLTS, THE READOUT RANGE IS 0.14 V TO 2.7 V. HIGHEST ORDER LED STAYS ON DURING OVERRANGE. AVOID SUBSTITUTIONS FOR R1, R2 AND R3.

SI IS THE MODE SWITCH. USE A DPDT TOGGLE. POSITION 1 SELECTS BAR AND POSITION 2 SELECTS DOT. OMIT SI IF ONLY ONE MODE IS REQUIRED. SIMPLY WIRE IN THE CORRECT CONNECTIONS.

FLASHING BAR READOUT

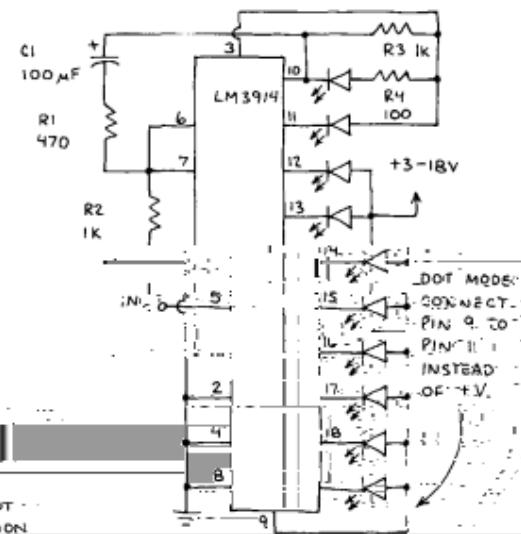


THE CIRCUITS ON THIS PAGE ARE ADAPTED FROM NATIONAL SEMICONDUCTOR'S LM3914 LITERATURE. BOTH WORK WELL.

WHEN ALL 10 LEDs ARE ON THE DISPLAY FLASHES; OTHERWISE THE LEDs DO NOT FLASH. INCREASE C1 TO SLOW FLASH RATE.


DOT/BAR DISPLAY DRIVER LM3914N

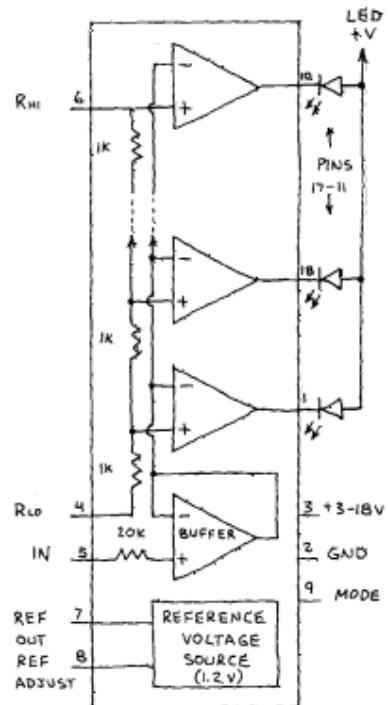ONE OF THE MOST IMPORTANT CHIPS IN THIS NOTEBOOK. LIGHTS UP TO 10 LED's (BAR MODE) OR 1-10 LED's (DOT MODE) IN RESPONSE TO AN INPUT VOLTAGE. CHIP CONTAINS A VOLTAGE DIVIDER AND 10 COMPARATORS THAT TURN ON IN SEQUENCE AS THE INPUT VOLTAGE RISES. HERE'S A SIMPLIFIED VERSION OF THE CIRCUIT:




R_{H1} AND R_{D1} ARE THE ENDS OF THE DIVIDER CHAIN. THE REFERENCE VOLTAGE OUTPUT (REF OUT) IS 1.2-1.3 VOLTS. CONNECT PIN 9 TO PIN 11 FOR DOT MODE OR +V FOR BAR MODE.

106

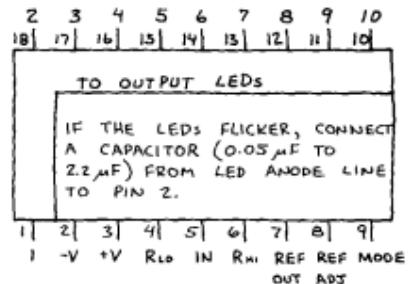


DOT/BAR DISPLAY

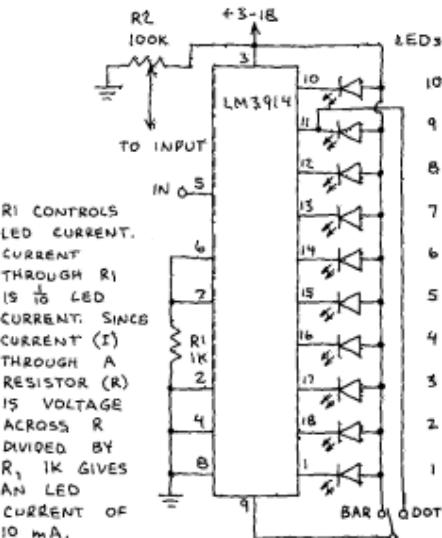


WHEN +V = +3-18 VOLTS, THE READOUT RANGE IS 0.13-1.30 VOLTS. TO CHANGE RANGE TO 0.1-1.0 VOLT (0.1 VOLT PER LED), INSERT A 5K POTENTIOMETER BETWEEN PINS 6 AND 7. CONNECT VOLTmeter ACROSS PINS 5 AND 6 AND ADJUST R₂ FOR 1 VOLT AT PIN 5. THEN JUST 1K POT UNTIL LED 10 GLOWS. REPEAT THIS PROCEDURE FOR 0.1 VOLT AT PIN 5 AND LED 1. OR TO REPLACE THE 1K POT WITH A FIXED RESistor OF THE PROPER VALUE.

NOISE GENERATOR S2688 / MM5837N

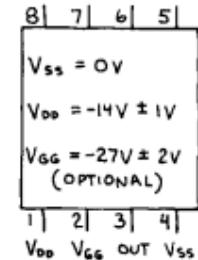PRODUCES BROADBAND WHITE NOISE FOR AUDIO AND OTHER APPLICATIONS. THE NOISE QUALITY IS VERY UNIFORM. IT IS PRODUCED BY A 17-BIT SHIFT REGISTER WHICH IS CLOCKED BY AN INTERNAL OSCILLATOR.




WHITE NOISE SOURCE

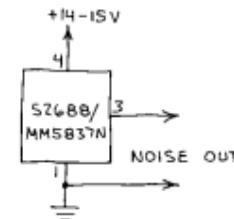


CONNECT OUTPUT TO AUDIO AMPLIFIER TO HEAR NOISE. USE 7815 VOLTAGE REGULATOR TO OBTAIN +15 VOLTS.

PINK NOISE SOURCE

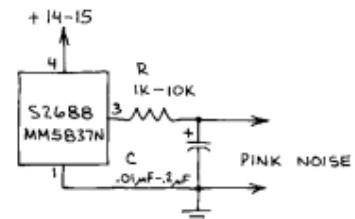


CHANGE R AND C TO ALTER NOISE SPECTRUM. ALSO, TRY LOWER SUPPLY VOLTAGES TO CHANGE SPECTRUM.

COIN TOSSEr

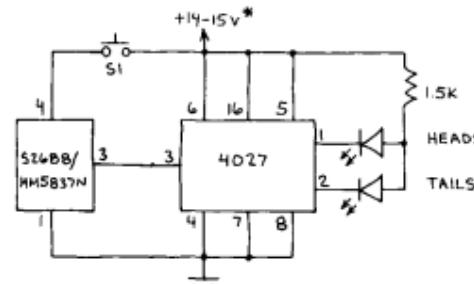

PRESS S1; BOTH LEDS GLOW. RELEASE S1 AND ONLY ONE GLOWS. GROUND INPUTS OF UNUSED HALF OF 4027 (PINS 9,10,11,12 AND 13). * (OK TO USE 9-VOLT BATTERY AS POWER SUPPLY.)

SNARE /BRUSH NOISE

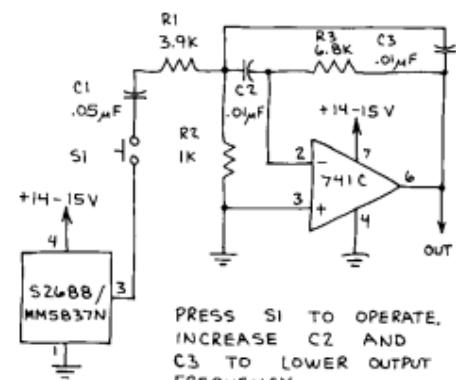

PRESS S1 TO OPERATE. INCREASE C2 AND C3 TO LOWER OUTPUT FREQUENCY.


39

NOTES


LED FLASHER / OSCILLATOR (CONTINUED)

3909


WHOOPER

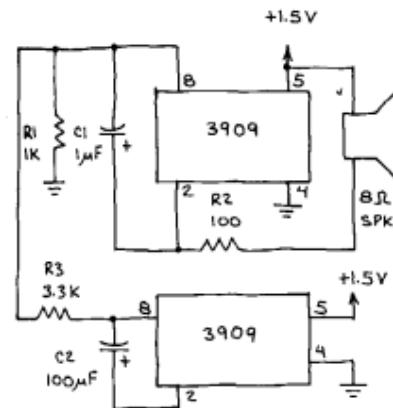


CHIRPER

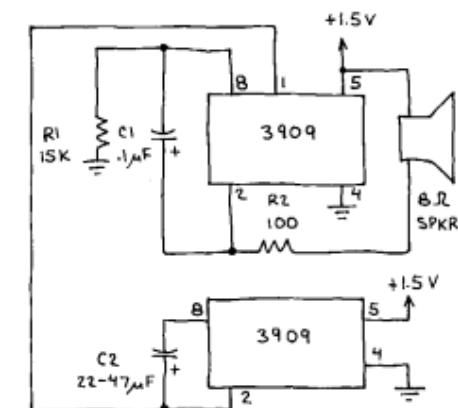



SUN POWERED OSCILLATOR

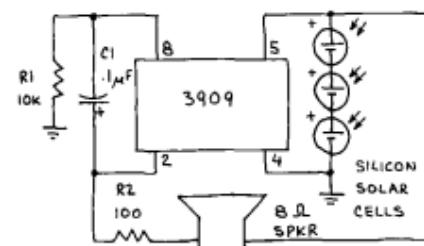

TOY ORGAN

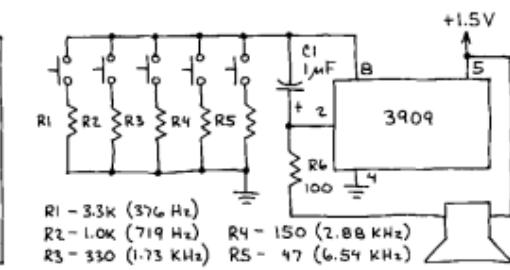


TTL CONTROLLED 3909

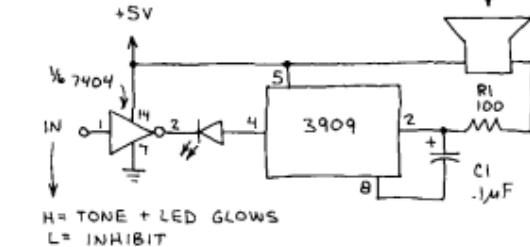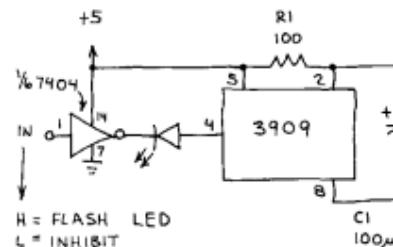


LED FLASHER/OSCILLATOR 3909

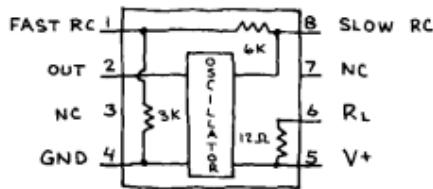
EASIEST TO USE IC IN THIS NOTEBOOK. FLASHES LEDS OR CAN BE USED AS TONE SOURCE. WILL DRIVE SPEAKER DIRECTLY. WILL FLASH A RED LED WHEN V_T IS ONLY 1.3 VOLTS.





LED FLASHER

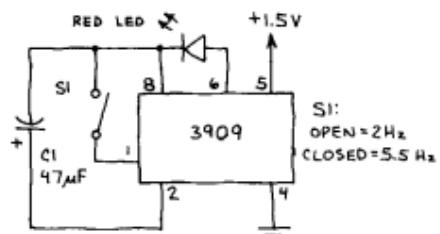


POWER FLASHER

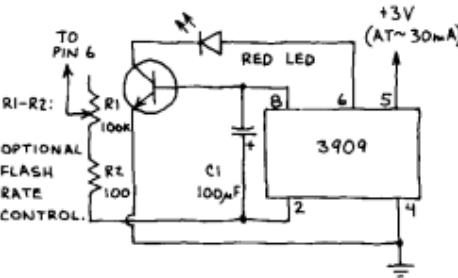

INFRARED TRANSMITTERS

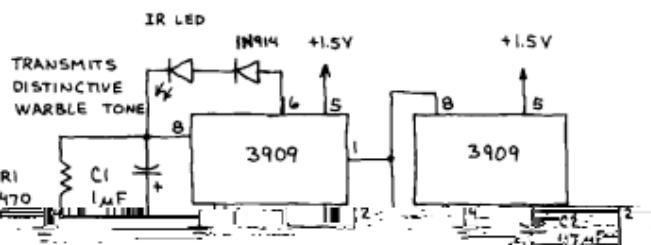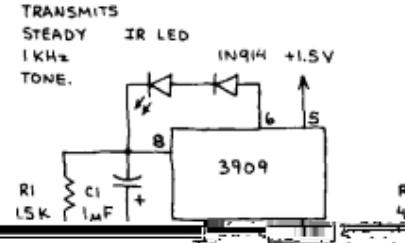


LIGHT-CONTROLLED TONE

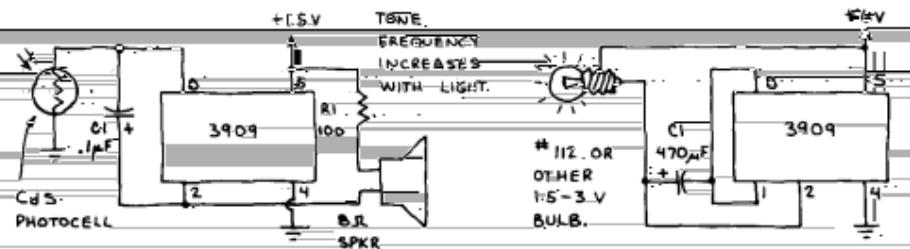

TTL/LS INTEGRATED CIRCUITS

INTRODUCTION

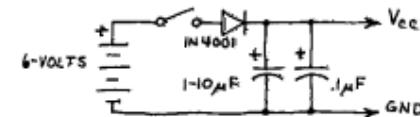TTL IS THE BEST ESTABLISHED AND MOST DIVERSIFIED IC FAMILY. LS IS FUNCTIONALLY IDENTICAL TO TTL BUT IS SLIGHTLY FASTER AND USES 80% LESS POWER. TTL/LS CHIPS REQUIRE A REGULATED 4.75-5.25 VOLT POWER SUPPLY. HERE'S A SIMPLE BATTERY SUPPLY:



THE DIODE DROPS THE BATTERY VOLTAGE TO A SAFE LEVEL. BOTH CAPACITORS SHOULD BE INSTALLED ON THE TTL/LS CIRCUIT BOARD. CIRCUITS WITH LOTS OF TTL/LS CHIPS CAN USE LOTS OF CURRENT. USE A COMMERCIAL 5 VOLT LINE POWERED SUPPLY TO SAVE BATTERIES. OR MAKE YOUR OWN. (SEE THE 7805 ON PAGE 86.)

OPERATING REQUIREMENTS

1. V_{CC} MUST NOT EXCEED 5.25 VOLTS.
2. INPUT SIGNALS MUST NEVER EXCEED V_{CC} AND SHOULD NOT FALL BELOW GND.
3. UNCONNECTED TTL/LS INPUTS USUALLY ASSUME THE H STATE... BUT DON'T COUNT ON IT! IF AN INPUT IS SUPPOSED TO BE FIXED AT H, CONNECT IT TO V_{CC} .
4. IF AN INPUT IS SUPPOSED TO BE FIXED AT L, CONNECT IT TO GND.
5. CONNECT UNUSED AND/NAND/OR INPUTS TO A USED INPUT OF THE SAME CHIP.
6. FORCE OUTPUTS OF UNUSED GATES H TO SAVE CURRENT (NAND—ONE INPUT H; NOR—ALL INPUTS L).

7. USE AT LEAST ONE DECOUPLING CAPACITOR (0.01-0.1 μF) FOR EVERY 5-10 GATE PACKAGES, ONE FOR EVERY 5-2 COUNTERS AND REGISTERS AND ONE FOR EACH ONE-SHOT. DECOUPLING CAPACITORS NEUTRALIZE THE HEFTY POWER SUPPLY SPARS THAT OCCUR WHEN A TTL/LS OUTPUT CHANGES STATES. THEY MUST HAVE SHORT LEADS AND BE CONNECTED FROM V_{CC} TO GND AS NEAR THE TTL/LS IC'S AS POSSIBLE.

8. AVOID LONG WIRES WITHIN CIRCUITS


9. IF THE POWER SUPPLY IS NOT ON THE CIRCUIT BOARD, CONNECT A 1-10μF CAPACITOR ACROSS THE POWER LEADS WHERE THEY ARRIVE AT THE BOARD.

INTERFACING TTL/LS

1. 1 TTL OUTPUT WILL DRIVE UP TO 10 TTL OR 20 LS INPUTS.

2. 1 LS OUTPUT WILL DRIVE UP TO 5 TTL OR 10 LS INPUTS.

3. TTL/LS LED DRIVERS:

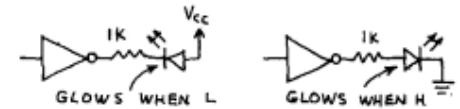


TTL/LS TROUBLESHOOTING

1. DO ALL INPUTS GO SOMEWHERE?
2. ARE ALL IC PINS INSERTED INTO THE BOARD OR SOCKET?
3. DOES THE CIRCUIT OBEY ALL TTL/LS OPERATING REQUIREMENTS?
4. HAVE YOU FORGOTTEN A CONNECTION?
5. HAVE YOU USED ENOUGH DECOUPLING CAPACITORS? ARE THEIR LEADS SHORT?
6. IS V_{CC} AT EACH CHIP WITHIN RANGE?


QUAD NAND GATE 7400/74LS00

THE BASIC BUILDING BLOCK CHIP FOR THE ENTIRE TTL FAMILY. VERY EASY TO USE. HUNDREDS OF APPLICATIONS.



CONTROL GATE

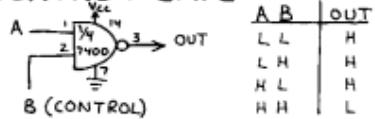


INVERTER

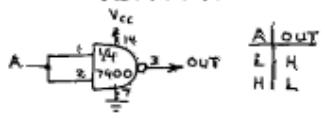


AND GATE

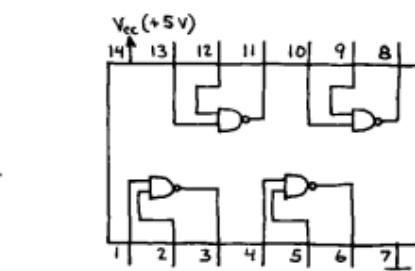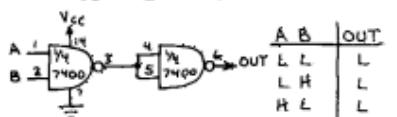


NOR GATE

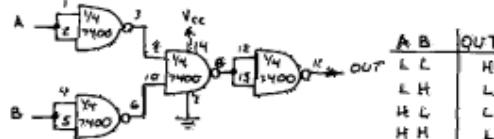


4-INPUT NAND GATE

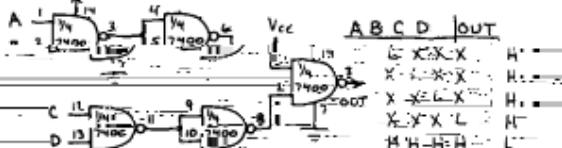


OR GATE

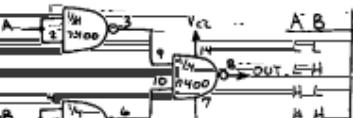


EXCLUSIVE-OR GATE

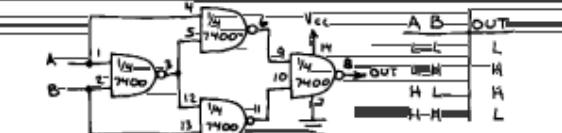

AND-OR GATE

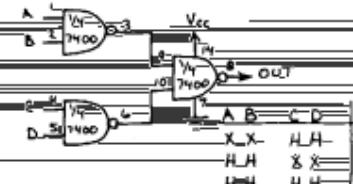


EXCLUSIVE-NOR GATE

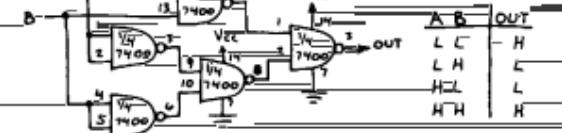


NOTE: PIN NUMBERS CAN BE REARRANGED IF DESIRED.

QUAD COMPARATOR (CONTINUED) LM339

LED BARGRAPH READOUT

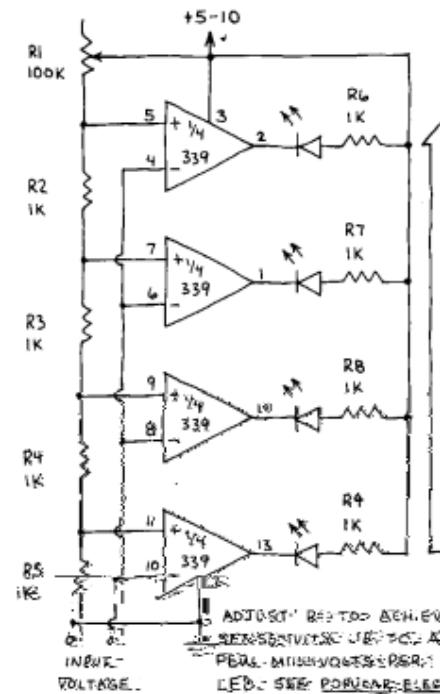


WINDOW COMPARATOR

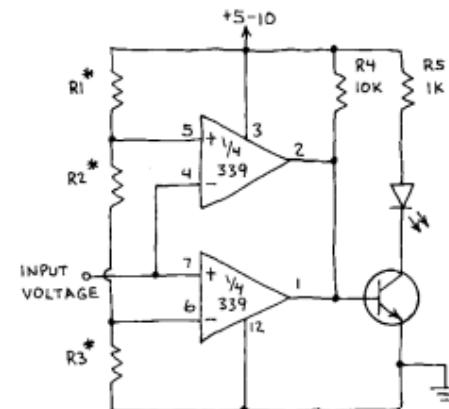


THE LED GLOWS WHEN THE INPUT VOLTAGE IS WITHIN THE WINDOW DETERMINED BY R1-R3. THE WINDOW IS 4-6 MILLIVOLTS WIDE.
* WHEN R1=500 Ω , R2=120 Ω AND R3=1M, IT EXTENDS FROM 1.6-4.2 VOLTS WHEN R1 AND R3=15,000 Ω AND R2=25,000 Ω . USE POTS FOR R1-R3 FOR A FULLY ADJUSTABLE WINDOW.

PROGRAMMABLE LIGHT METER

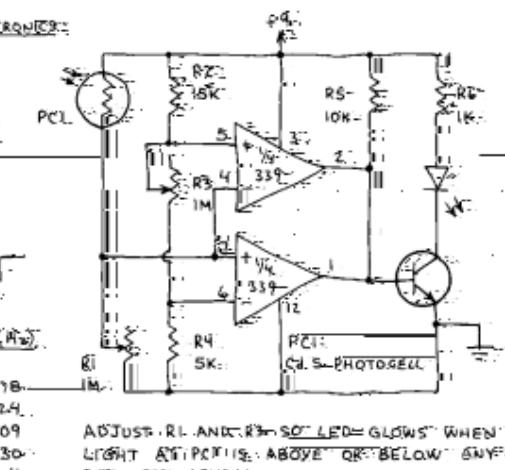


SQUAREWAVE OSCILLATOR

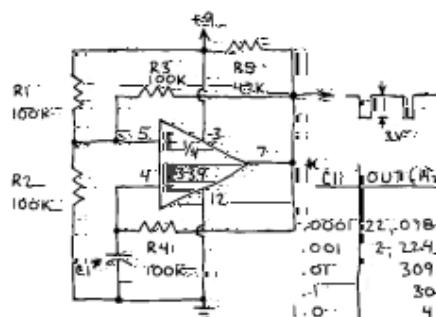



ADJUST R1 AND R3 SO LED GLOWS WHEN LIGHT ATTENUATION ABOVE OR BELOW ANY DESIRED LEVEL.

QUAD COMPARATOR LM339

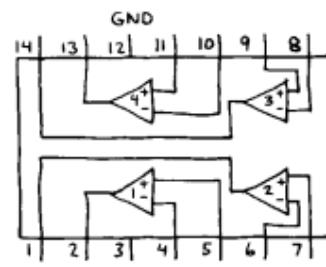FOUR INDEPENDENT VOLTAGE COMPARATORS IN A SINGLE PACKAGE. NOTE THAT A SINGLE POLARITY POWER SUPPLY IS REQUIRED. (MOST COMPARATORS ARE DESIGNED PRIMARILY FOR DUAL SUPPLY OPERATION.) NOTE UNUSUAL LOCATION OF THE SUPPLY PINS. COMPARATORS MAY OSCILLATE IF OUTPUT LEAD IS TOO CLOSE TO INPUT LEADS. GROUND ALL PINS OF UNUSED COMPARATORS.




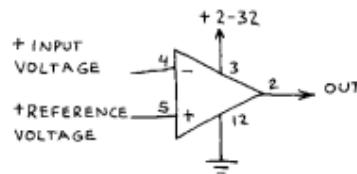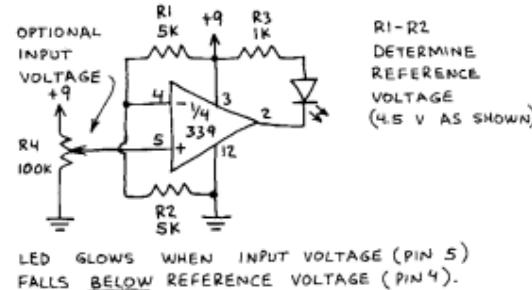NON-INVERTING COMPARATOR INVERTING COMPARATOR




INVERTING COMPARATOR WITH HYSTERESIS


NON-INVERTING COMPARATOR WITH HYSTERESIS

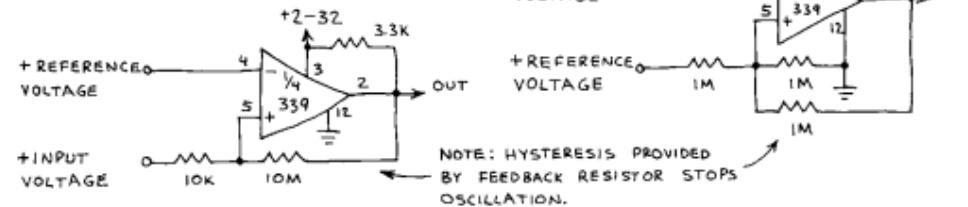


TTL DRIVER

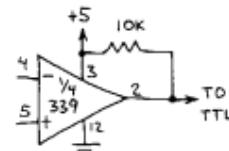

CMOS DRIVER

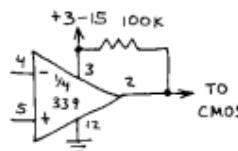


3-STATE OUTPUT

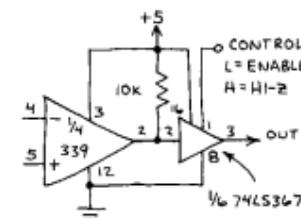


QUAD NAND GATE (CONTINUED) 7400/74LS00

HALF ADDER


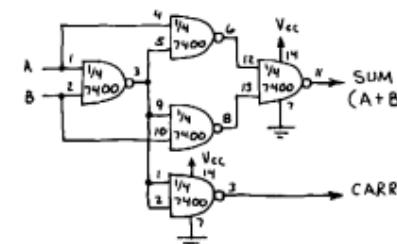


D FLIP-FLOP

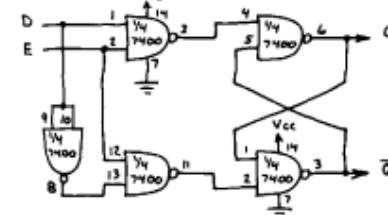


WHEN ENABLE (E) INPUT IS HIGH, Q OUTPUT FOLLOWS D INPUT. NO CHANGE WHEN E IS LOW.


LED DUAL FLASHER

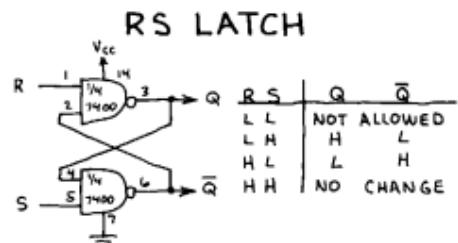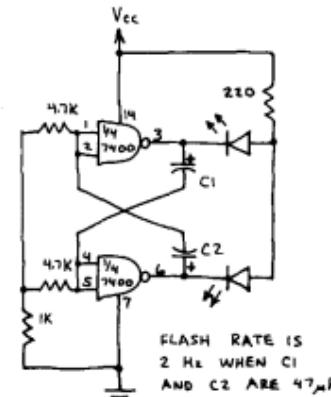

GATED RS LATCH

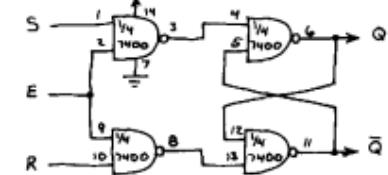


SWITCH DEBOUNCER

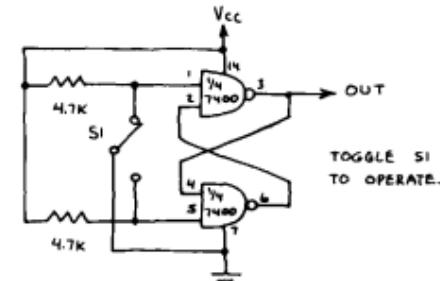


PROVIDES NOISE FREE OUTPUT FROM STANDARD SPDT TOGGLE SWITCH.

QUAD NAND GATE (CONTINUED) 7400/74LS00


8-INPUT NAND GATE

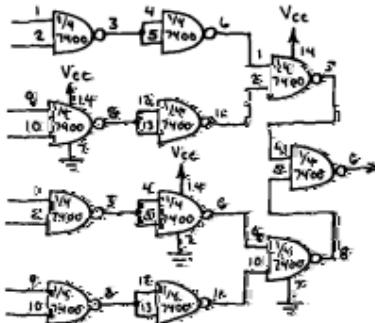

BCD DECODER

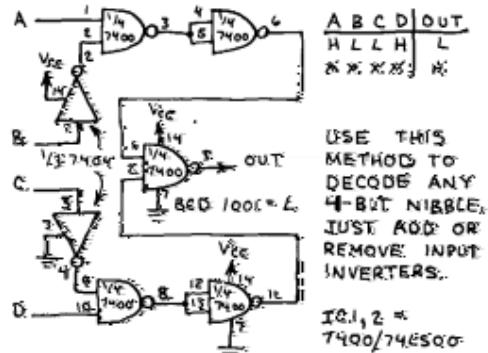


UNANIMOUS VOTE DETECTOR

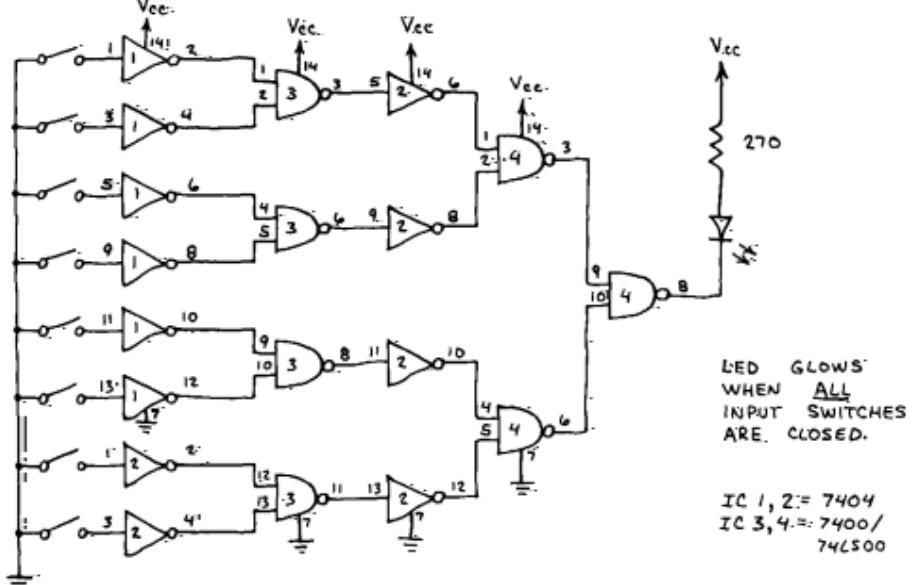


QUAD OPERATIONAL AMPLIFIER LM3900N

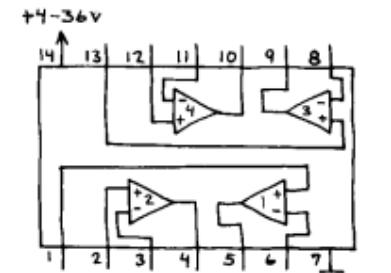OPERATES FROM SINGLE POLARITY POWER SUPPLY. LESS GAIN (70 dB) BUT WIDER BANDWIDTH (25 MHz AT GAIN OF 1) THAN THE LM324 QUAD OP-AMP. NOTE STANDARD POWER SUPPLY PIN LOCATIONS. CAUTION: SHORTING THE OUTPUTS DIRECTLY TO V₊ OR GROUND OR REVERSED POWER CONNECTIONS MAY DAMAGE THIS CHIP.




NOTE: DO NOT SUBSTITUTE LM3900 FOR OTHER OP-AMPS.


ASTABLE MULTIVIBRATOR

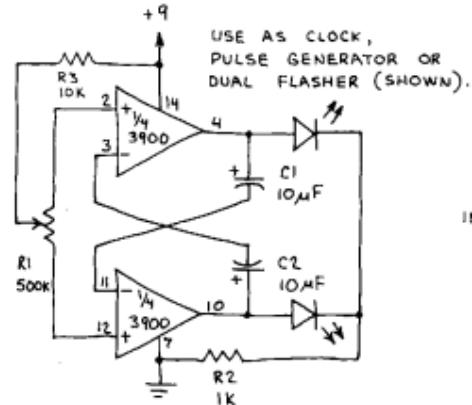


TOGGLE FLIP-FLOP

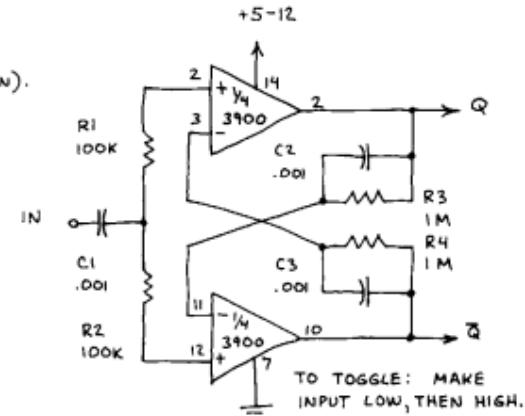

FUNCTION GENERATOR

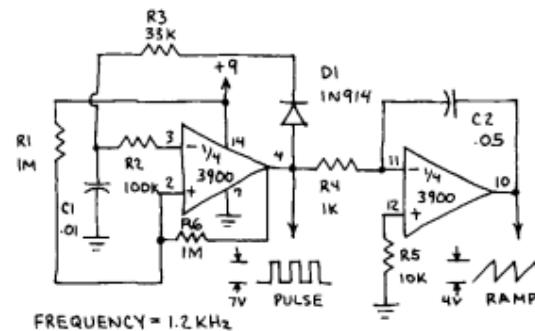


X10 AMPLIFIER

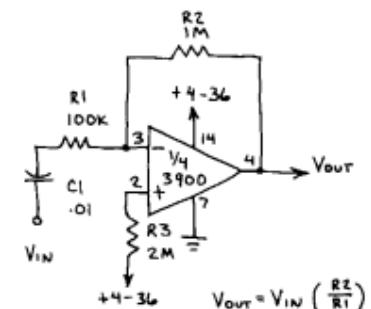


QUAD OPERATIONAL AMPLIFIER LM324N

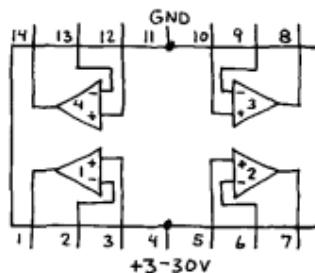OPERATES FROM SINGLE POLARITY POWER SUPPLY. MORE GAIN (100 dB) BUT LESS BANDWIDTH (1 MHz WHEN GAIN IS 1) THAN THE LM3900 QUAD OP-AMP. NOTE UNUSUAL LOCATION OF POWER SUPPLY PINS. CAUTION: SHORTING THE OUTPUTS DIRECTLY TO V₊ OR GND OR REVERSING THE POWER SUPPLY MAY DAMAGE THIS CHIP.




QUAD AND GATE 7408/74LS08

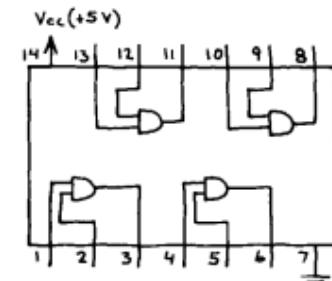ONE OF THE BASIC BUILDING BLOCK CHIPS. NOT AS VERSATILE, HOWEVER, AS THE 7400/74LS00 QUAD NAND GATE.





AND GATE BUFFER

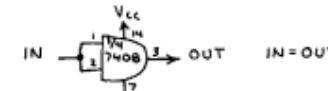


USE FOR INTERFACING WITHOUT CHANGING LOGIC STATES.


NAND GATE

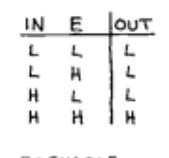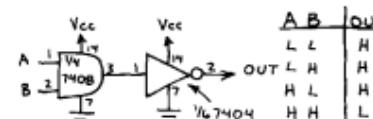



NOR GATE

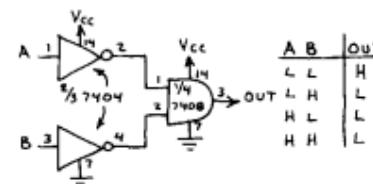


AND-OR-INVERT GATE

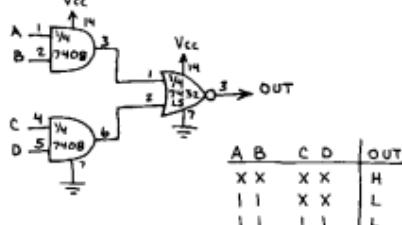


4-INPUT NAND GATE

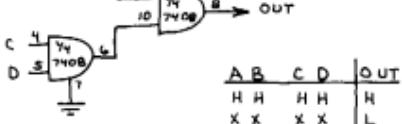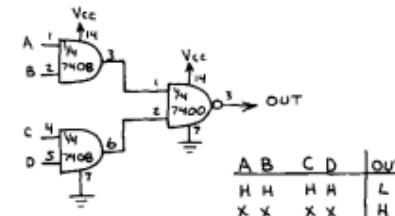



BANDPASS FILTER

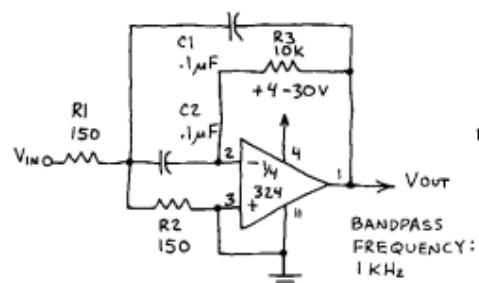

INFRARED TRANSMITTER

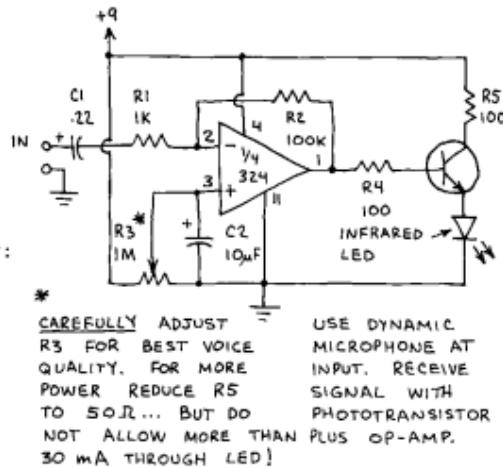


PULSE GENERATOR

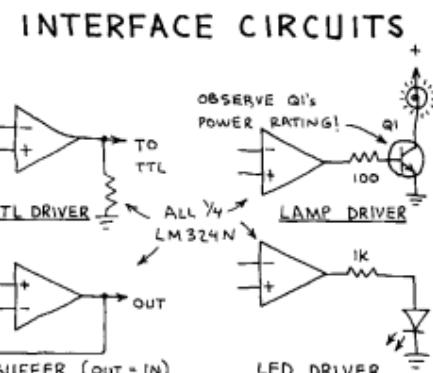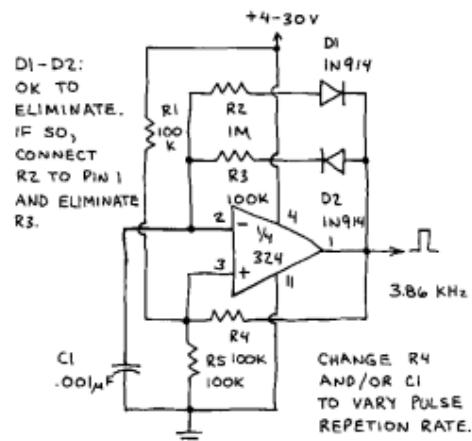

QUAD OR GATE

74LS32

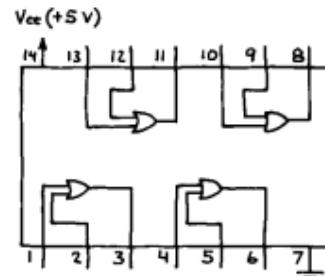
FOUR 2-INPUT OR GATES.
NOT AS VERSATILE AS 7402/
74LS02 QUAD NOR GATE,
BUT VERY USEFUL IN SIMPLE
DATA SELECTORS.




QUAD OPERATIONAL AMPLIFIER

TL084C (JFET INPUT)

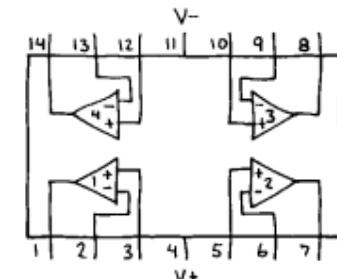HIGH IMPEDANCE (10^{12} OHMS) JUNCTION FET INPUTS. OUTPUT SHORT CIRCUIT PROTECTION. HIGH SLEW RATE (12 V/ μ SEC) PLUS LOW NOISE OPERATION. PERFORMANCE SIMILAR TO LF353N. NOTE THAT PIN CONNECTIONS ARE SAME AS LM324.



AND-OR CIRCUIT

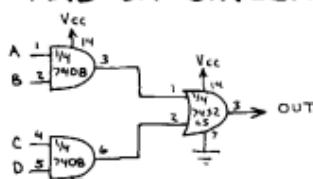

OUTPUT GOES HIGH WHEN BOTH INPUTS OF EITHER OR BOTH AND GATES ARE HIGH; OTHERWISE


THE OUTPUT IS LOW. THIS BASIC CIRCUIT CAN BE USED TO MAKE DATA SELECTORS AS SHOWN BELOW.

SELECTOR




NOTE: FOR 3-INPUT DATA SELECTOR,
USE 74CS27 NOR GATE FOLLOWED
BY INVERTER AND PRECEDED BY
74LS10 3-INPUT AND GATES.

NOR GATE

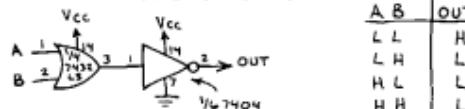


NAND GATE

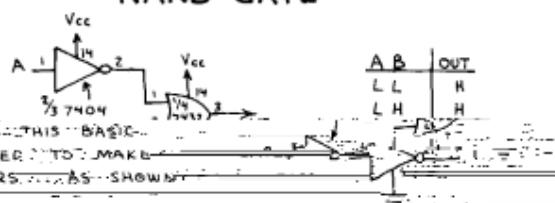


2-INPUT DATA SELECTOR

MICROPHONE PREAMPLIFIER

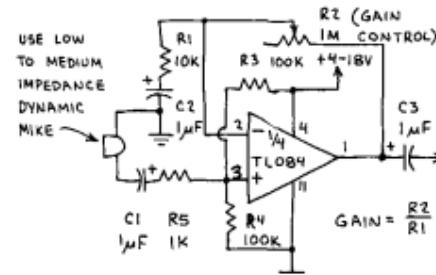


NOTE SINGLE POLARITY POWER SUPPLY (THANKS TO R3 AND R4) AND AC COUPLING.


LOW-Z PREAMPLIFIER

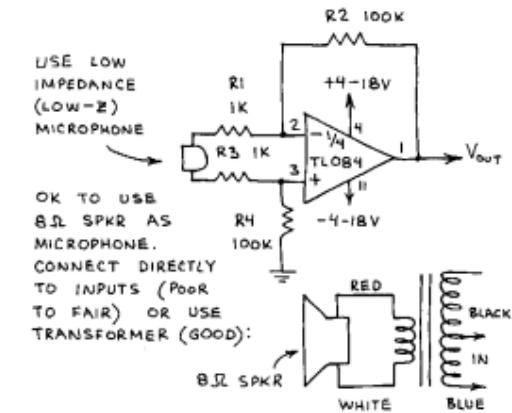

INFRARED VOICE COMMUNICATOR

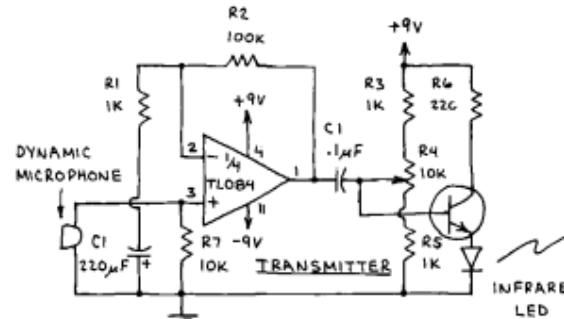

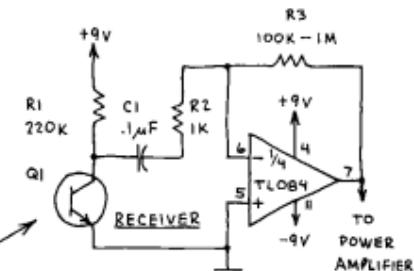
POINT THE LED AT Q1 AND ADJUST R4 UNTIL BEST VOICE QUALITY IS OBTAINED. (R4 APPLIES BIAS TO LED.) R6 LIMITS MAXIMUM LED CURRENT TO A SAFE 40 mA.



MAXIMUM RANGE: HUNDREDS OF FEET AT NIGHT WITH LENSES AT Q1 AND LED. POWER AMP: SEE LM386.


DUAL OPERATIONAL AMPLIFIER LF353N (JFET INPUT)

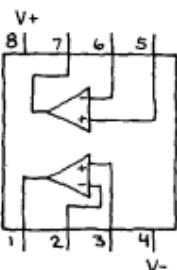HIGH IMPEDANCE (10^{12} OHM) JUNCTION FET INPUTS. OUTPUT SHORT CIRCUIT PROTECTION. HIGH SLEW RATE (13V/ μ SEC), LOW NOISE OPERATION. AMPLIFIERS ARE SIMILAR TO THOSE IN THE TL084C. NOTE THAT PIN CONNECTIONS ARE THE SAME AS 1458. THIS OP-AMP, HOWEVER, OFFERS MUCH BETTER PERFORMANCE.




QUAD NOR GATE 7402/74LS02

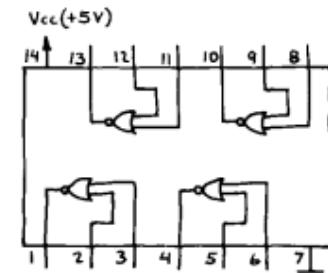JUST AS VERSATILE AS THE 7400/74LS00 QUAD NAND GATE... BUT NOT USED AS OFTEN. ADD INVERTER (7404/74LS04) TO BOTH INPUTS OF A NOR GATE AND AN AND GATE IS FORMED.




EXCLUSIVE-OR GATE

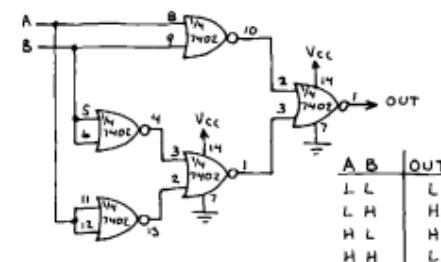


THIS CIRCUIT IS EQUIVALENT TO A BINARY HALF-ADDER.


RS LATCH

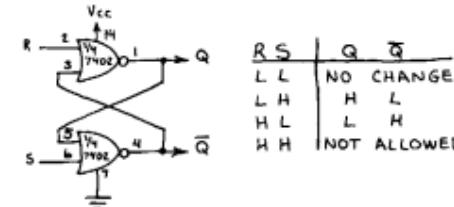

4-INPUT NOR GATE

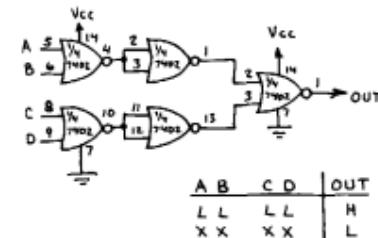


ONE-SHOT

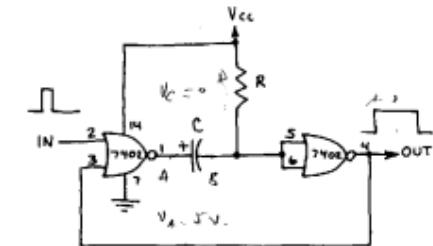


THIS CIRCUIT IS A MONOSTABLE MULTIVIBRATOR OR PULSE STRETCHER. AN INPUT PULSE TRIGGERS AN OUTPUT PULSE WITH A DURATION DETERMINED BY R AND C. OUTPUT PULSE WIDTH IS APPROXIMATELY $0.4RC$.


AND GATE

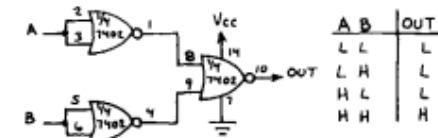


OR GATE

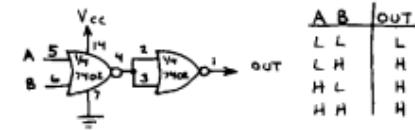


SAMPLE AND HOLD

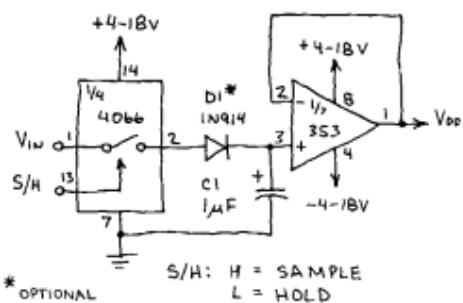

PEAK DETECTOR

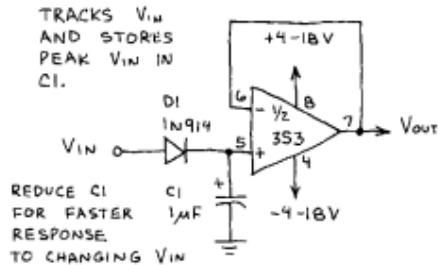


PROGRAMMABLE GAIN OP-AMP

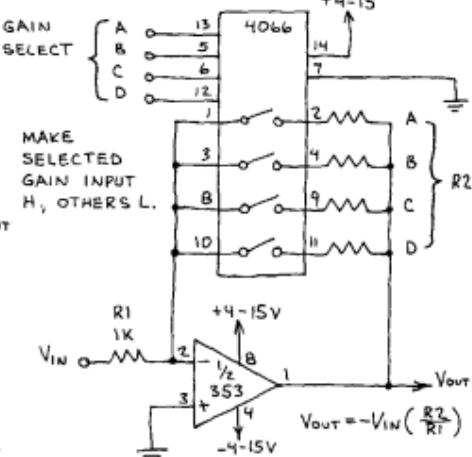


CONNECT OUTPUTS OF PREAMPLIFIERS TO INPUTS 1-3. OK TO ADD MORE CHANNELS. WORKS WELL WITH TL084 MICROPHONE PREAMPLIFIERS.

DUAL 4-INPUT NAND GATE 74LS20

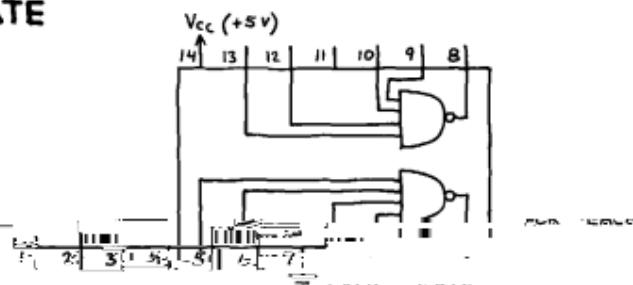MANY DECODER AND ENCODER APPLICATIONS CAN BE USED AS DUAL 3-INPUT NAND GATE WITH ENABLE (CONTROL) INPUT FOR EACH GATE.




BCD DECODERS

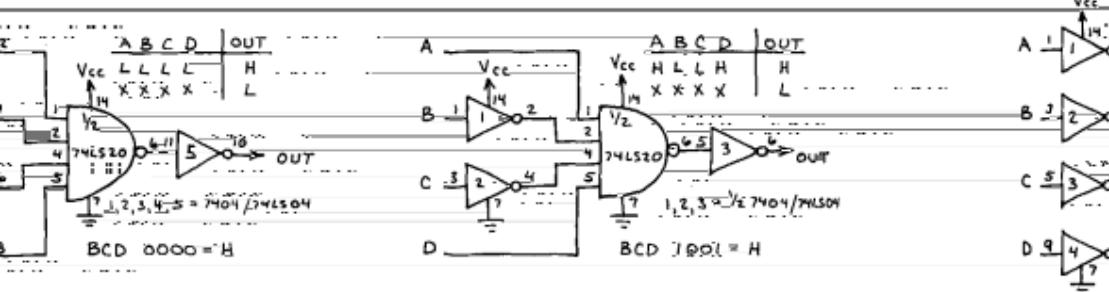

OUTPUTS GO HIGH WHEN APPROPRIATE BCD WORD APPEARS AT INPUTS DCBA. OUTPUTS STAY LOW FOR ALL OTHER INPUTS. (OMIT FINAL INVERTER TO PROVIDE ACTIVE LOW OUTPUT.) USE THIS METHOD TO DECODE ANY 4-BIT NIBBLE.

AL-TO-BINARY CODED DECIMAL (BCD) ENCODER

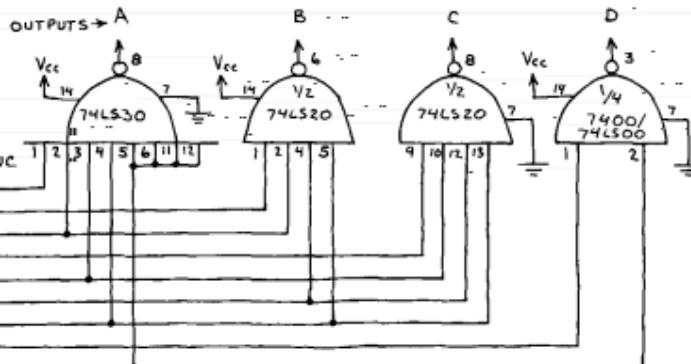


INPUT SHOULD BE LOW AND ALL OTHER INPUTS SHOULD BE HIGH.


SELECTED BCD EQUIVALENT WILL APPEAR AT THE OUTPUTS.

DUAL OPERATIONAL AMPLIFIER 1458

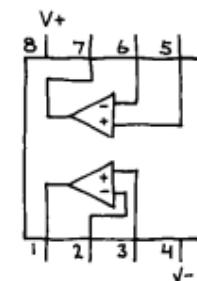TWO 741C OP-AMPS IN A SINGLE 8-PIN MINI-DIP. TRY TO USE THIS CHIP FOR CIRCUITS THAT REQUIRE TWO OR MORE 741'S. YOU'LL SAVE TIME, SPACE AND MONEY.




PEAK DETECTOR

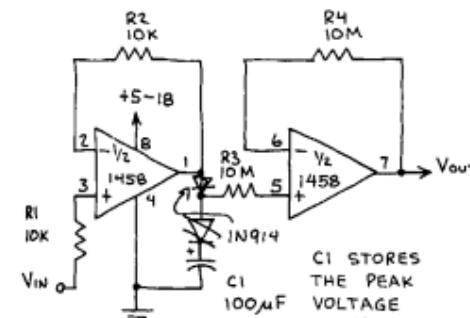

C1 STORES THE PEAK VOLTAGE AT VIN.


APPLICATIONS INCLUDE USE AS ANALOG "MEMORY" THAT STORES PEAK AMPLITUDE OF A FLUCTUATING VOLTAGE.

PULSE GENERATOR

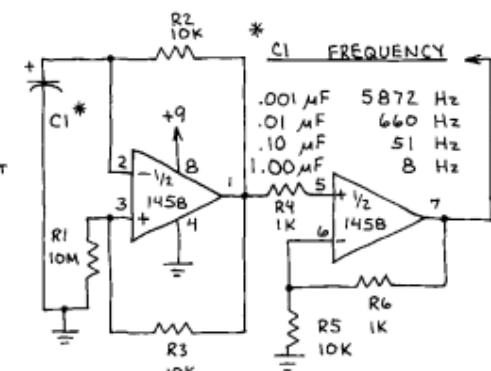


PULSES ARE DC. AMPLITUDE WHEN C1 = 0.1 μF IS 5 VOLTS.

DECIM

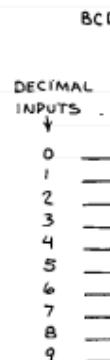


FUNCTION GENERATOR

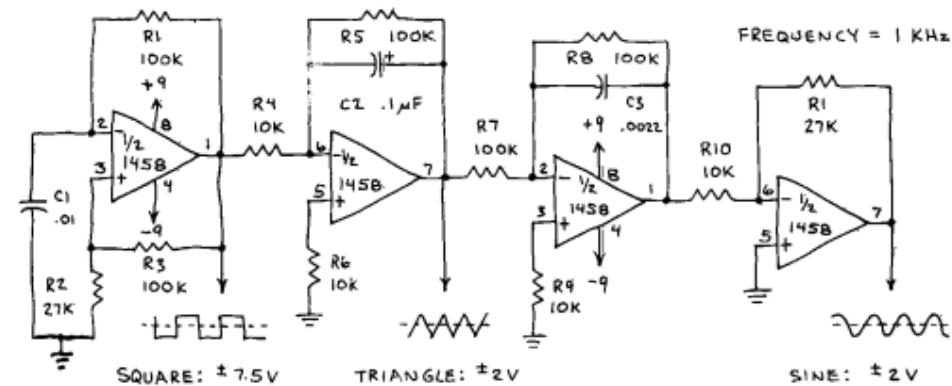

OPERATIONAL AMPLIFIER (CONTINUED)


741C

OPTICAL POWER METER

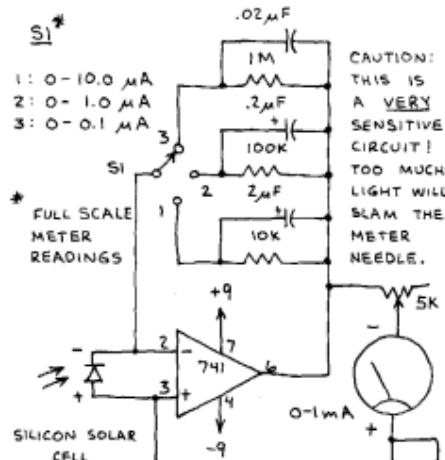


THIS CIRCUIT CAN BE USED AS A FAIRLY GOOD QUALITY RADIOMETER.

ELECTRONIC BELL

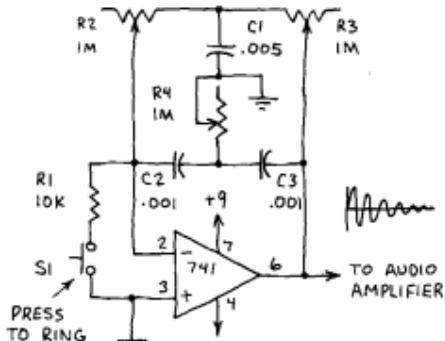


ADJUST R3 TO JUST BELOW OSCILLATION POINT. ADJUST R2 AND R3 FOR SOUNDS SUCH AS BELL, DRUM, TINKLING, ETC.

BARGRAPH LIGHT METER

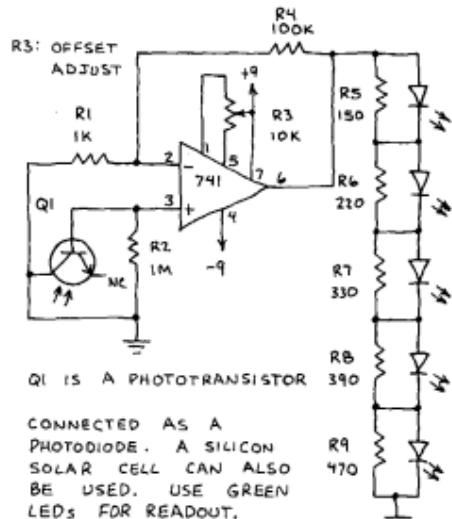

CONNECTED AS A PHOTODIODE. A SILICON SOLAR CELL CAN ALSO BE USED. USE GREEN LEDs FOR READOUT.

AUDIBLE LIGHT SENSOR

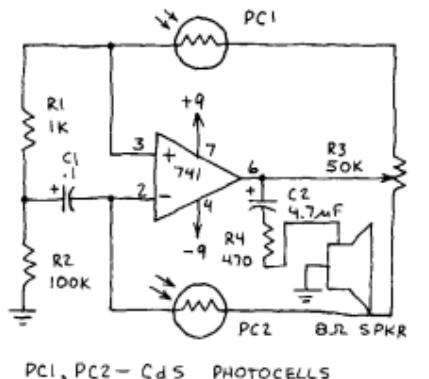


LIGHT ON PC1 DECREASES TONE FREQUENCY.
LIGHT ON PC2 INCREASES TONE FREQUENCY.


TRIPLE 3-INPUT NOR GATE

74LS27

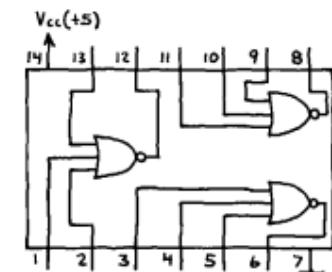USEFUL FOR DATA SELECTORS AND NOR GATE FLIP-FLOPS THAT REQUIRE CLEAR AND PRESET INPUTS.




GATED RS LATCH

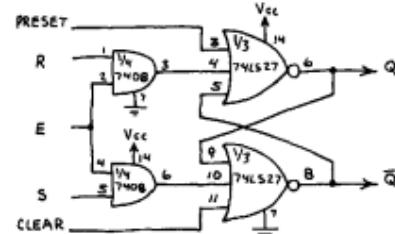


FUNCTIONS AS RS LATCH WHEN E (ENABLE) INPUT IS HIGH. IGNORES RS INPUTS WHEN E IS LOW.

3-INPUT OR GATE

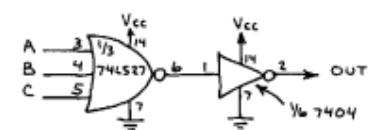


3-INPUT DATA SELECTOR

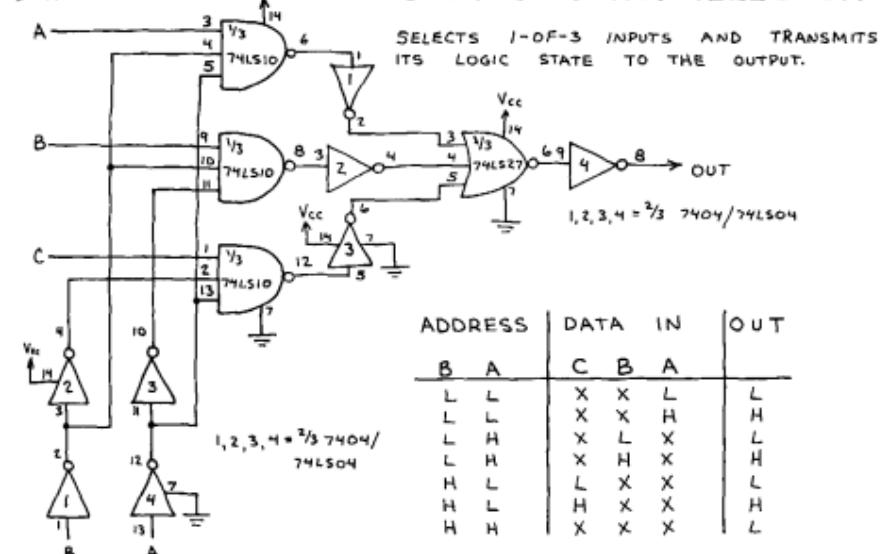


ADDRESS (DATA SELECT)

8-INPUT NAND GATE 74LS30

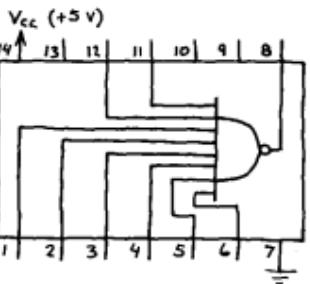HANDY FOR BYTE-SIZE (8-BIT) DECODING APPLICATIONS. CAN DECODE UP TO 256 INPUT COMBINATIONS. ALSO USEFUL AS PROGRAMMABLE NAND GATE.




8-BIT DECODER

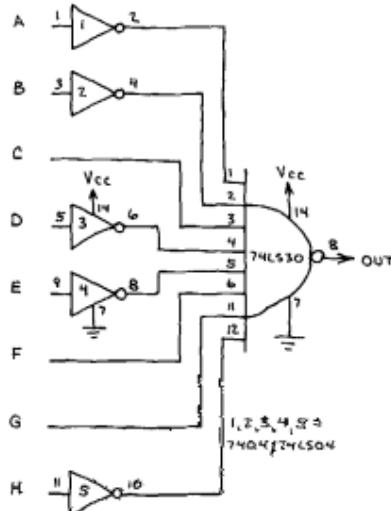

OUTPUT GOES LOW ONLY WHEN INPUT IS LHHLLHLL (DECIMAL 100). UP TO 256 INPUTS CAN BE DECODED BY REARRANGING UP TO 8 INPUT INVERTERS.


UNANIMOUS VOTE DETECTOR

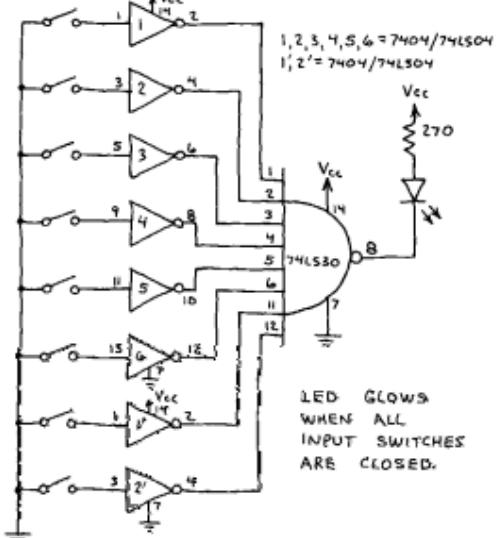


LED GLOWS WHEN ALL INPUT SWITCHES ARE CLOSED.

PROGRAMMABLE NAND GATES


5-INPUT

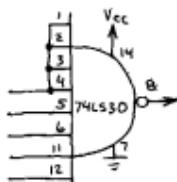

6-INPUT

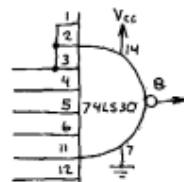


7-INPUT

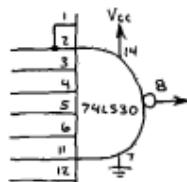


OPERATIONAL AMPLIFIER (CONTINUED) 741C

LIGHT WAVE RECEIVER

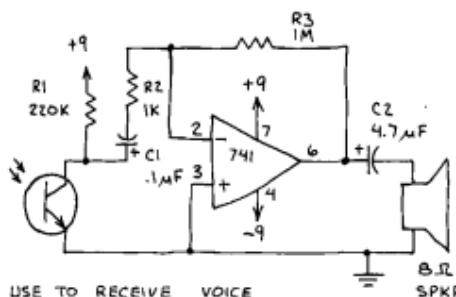


USE TO RECEIVE VOICE MODULATED LIGHT WAVES. OK TO USE SINGLE POLARITY POWER SUPPLY FOR NON-VOICE RECEPTION.

60-Hz NOTCH FILTER

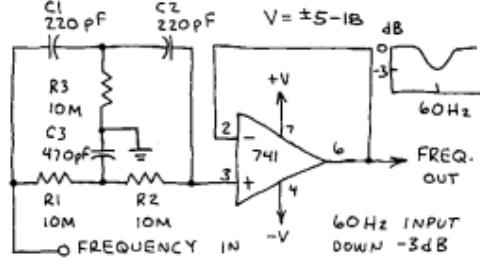

60Hz INPUT DOWN -3dB

4-BIT D/A CONVERTER

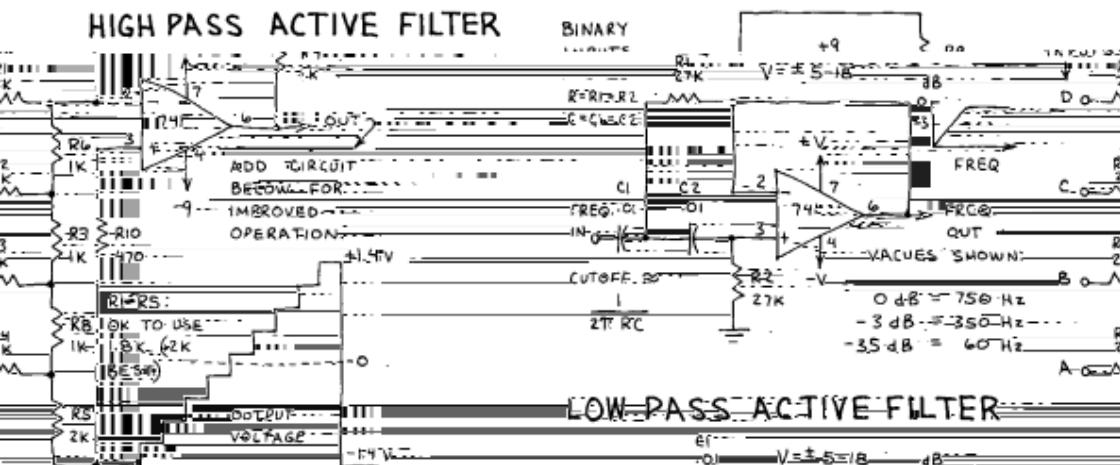

VALUES SHOWN:

0 dB = 750 Hz
-3 dB = 350 Hz
-3.5 dB = 60 Hz

LOW-PASS ACTIVE FILTER




VALUES SHOWN:

0 dB = 50Hz
-3 dB = 250 Hz
-5.5 dB = 10 kHz


OPERATIONAL AMPLIFIER (CONTINUED)

741C


BASIC INTEGRATOR

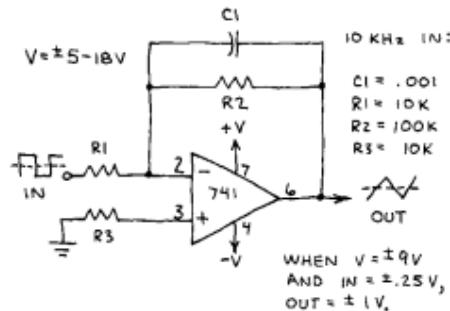


BASIC DIFFERENTIATOR

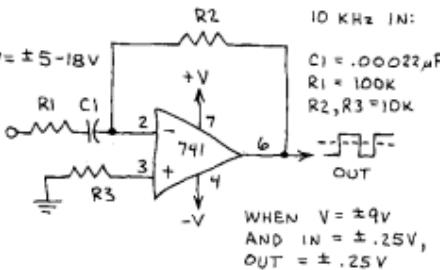


CLIPPING AMPLIFIER

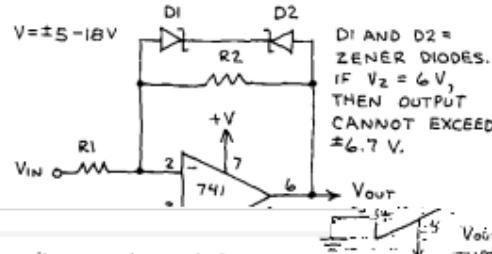


BRIDGE AMPLIFIER

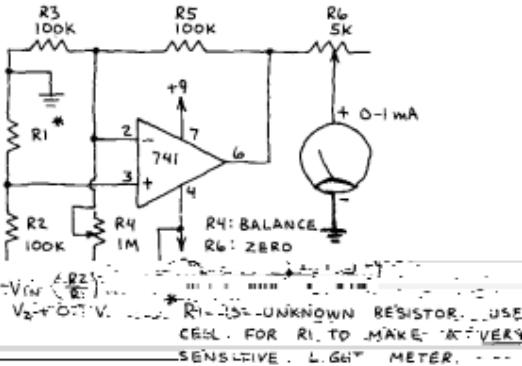

SUMMING AMPLIFIER

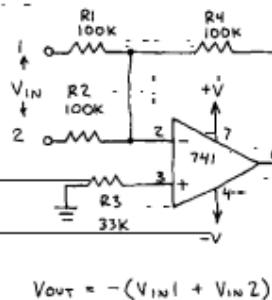


DIFFERENCE AMPLIFIER

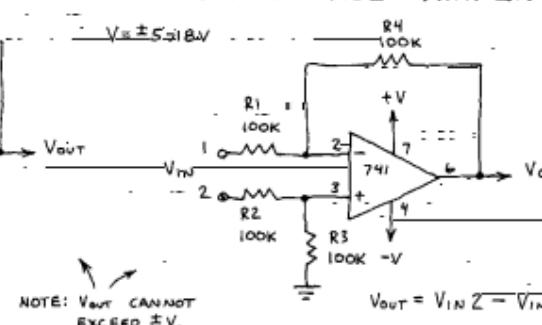


DUAL AND-OR-INVERT GATE

74LS51

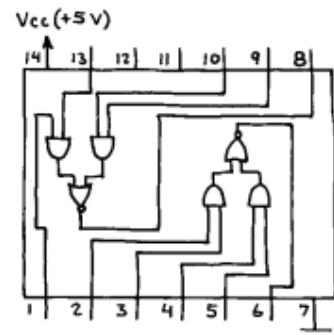
VERY VERSATILE BUILDING BLOCK CHIP. IDEAL FOR CUSTOMIZED DATA SELECTORS, LATCHES AND EXPANSION OF A SINGLE INPUT TO AN AND-OR INPUT.



LATCH WITH ENABLE INPUT

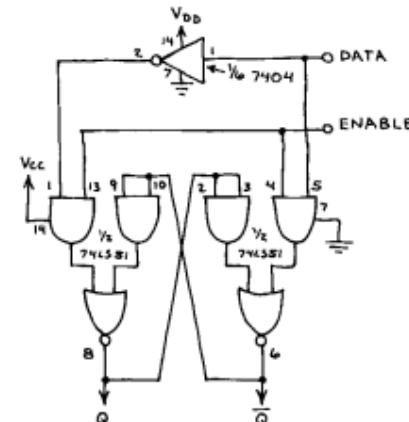


TYPICAL AND-OR INPUT

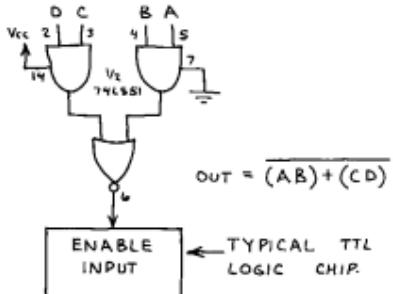

Q OUTPUT FOLLOWS DATA INPUT WHEN ENABLE INPUT IS HIGH. NO CHANGE WHEN ENABLE IS LOW.


1-OF-2 DATA SELECTOR

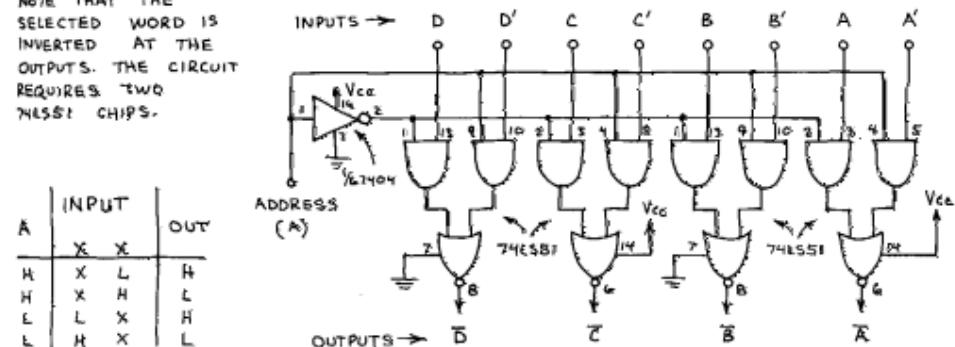


DUAL NAND SCHMITT TRIGGER 74LS13

TWO 4-INPUT NAND GATES WITH A SWITCHING THRESHOLD. OUTPUTS GO LOW WHEN INPUTS EXCEED 1.7 VOLTS. OUTPUTS GO HIGH WHEN INPUTS FALL TO 0.9 VOLT. IF ANY INPUT IS LOW, THE RESPECTIVE OUTPUT WILL STAY HIGH AND THE GATE WILL NOT TRIGGER.


GATED THRESHOLD DETECTOR

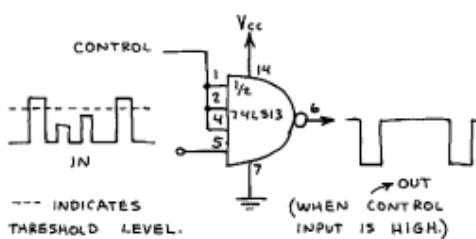


PHOTOTRANSISTOR RECEIVER

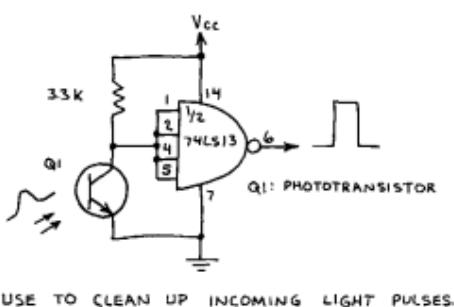

GATED OSCILLATOR

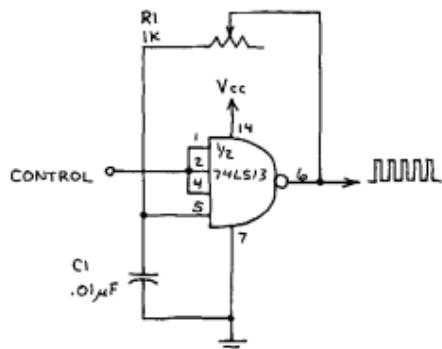


TWO-STATE LED FLASHER

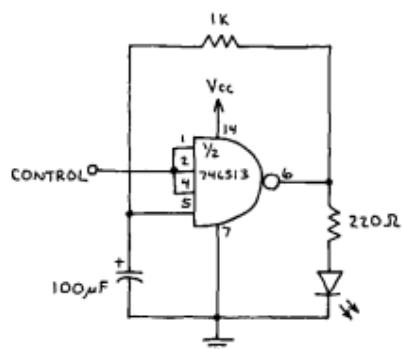


OPERATIONAL AMPLIFIER 741C

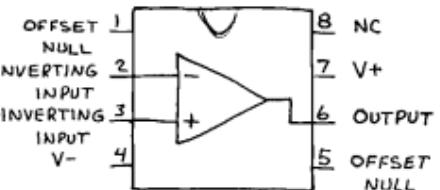
THE MOST POPULAR OP-AMP. USE FOR ALL GENERAL PURPOSE APPLICATIONS. (FOR SINGLE SUPPLY OPERATION AND VERY HIGH INPUT IMPEDANCE, USE OTHER OP-AMPS IN THIS NOTEBOOK.)




INVERTING AMPLIFIER

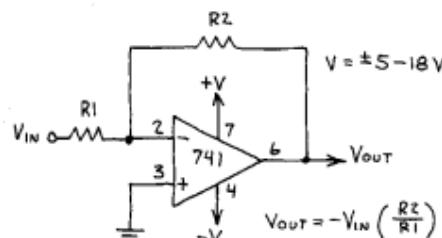


NON-INVERTING AMPLIFIER

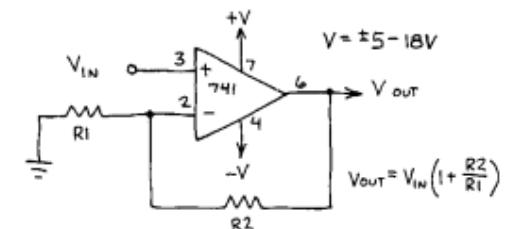


UNITY GAIN FOLLOWER

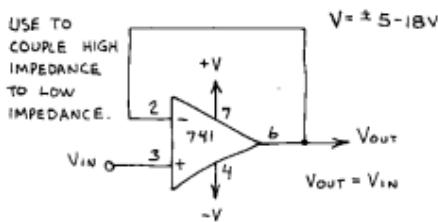

COMPARATOR

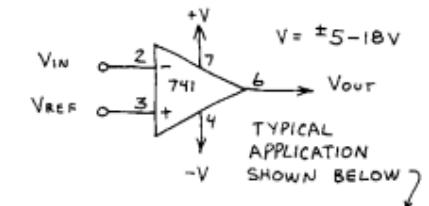

LEVEL DETECTOR

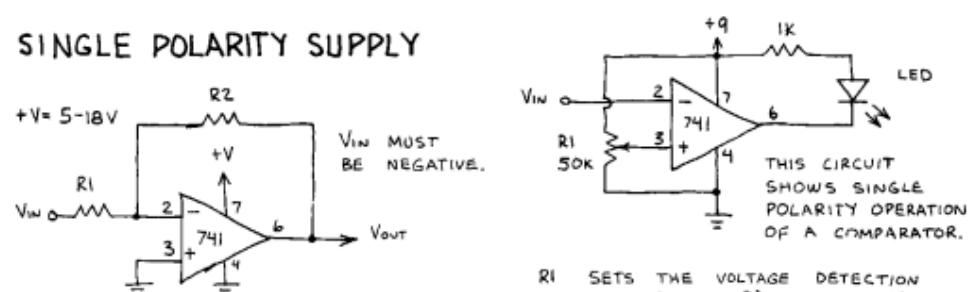


R1 SETS THE VOLTAGE DETECTION THRESHOLD (UP TO +9). WHEN V_{IN} EXCEEDS THE THRESHOLD (ALSO CALLED THE REFERENCE), THE LED GLOWS.

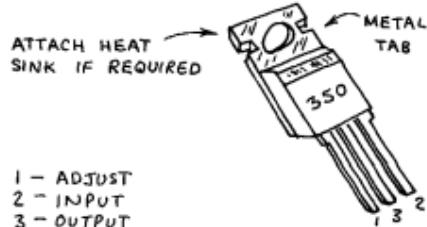
1.2 TO 33 VOLT REGULATOR

350T


CAN SUPPLY UP TO 3 AMPERES OVER 1.2 TO 33 VOLT OUTPUT RANGE. FEW EXTERNAL COMPONENTS REQUIRED. HEAT SINK REQUIRED FOR FULL POWER OUTPUT.



1.2 TO 20 VOLT REGULATOR

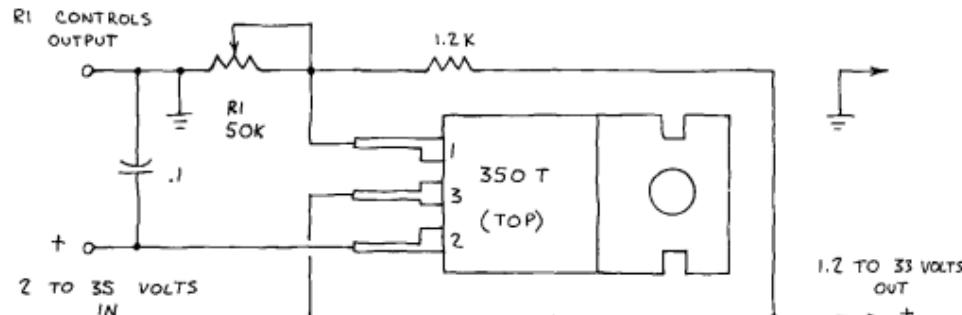



POWER PULSE GENERATOR

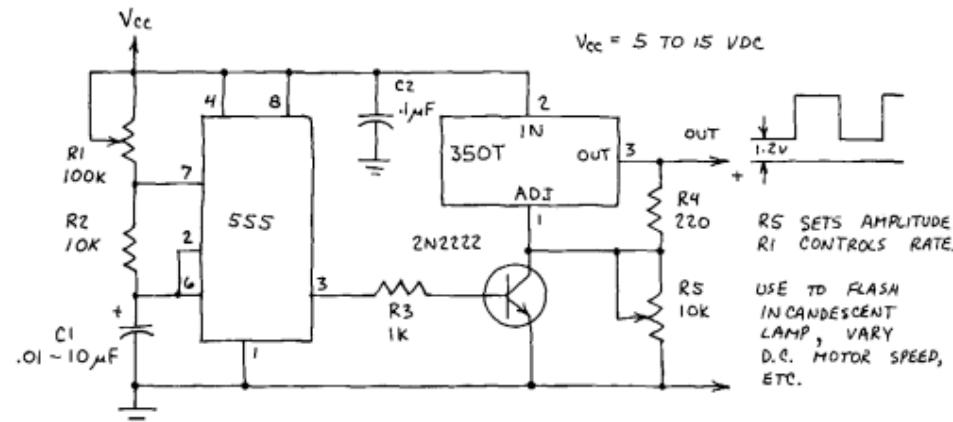


HEX INVERTER 7404/74LS04

VERY IMPORTANT IN ALMOST ALL LOGIC CIRCUITS. CHANGES AN INPUT TO ITS COMPLEMENT (i.e. H → L AND L → H).


BOUNCEFREE SWITCH

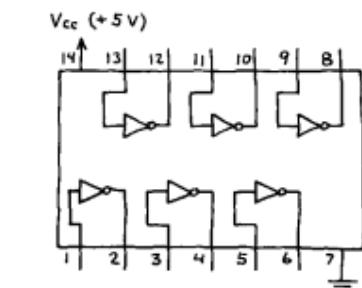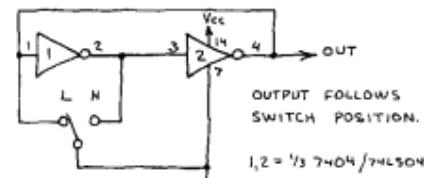


AUDIO OSCILLATOR

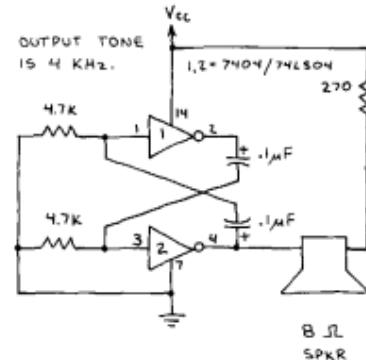

UNIVERSAL EXPANDER

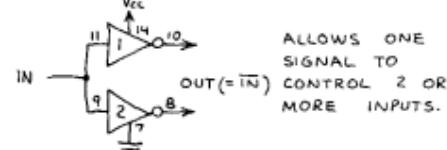

1-OF-2 DEMULTIPLEXER

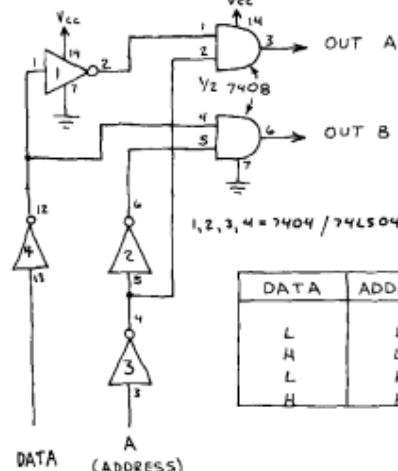

THIS CIRCUIT STEERS THE INPUT BIT TO THE OUTPUT SELECTED BY THE ADDRESS.

THIS TECHNIQUE CAN BE USED TO MAKE MULTIPLE OUTPUT DEMULTIPLEXERS.

DATA	ADDRESS	OUT A	OUT B
L	L	L	L
H	L	H	L
L	H	L	H
H	H	L	L


HEX 3-STATE BUS DRIVER

74LS367



EACH GATE FUNCTIONS AS A NON-INVERTING BUFFER WHEN ITS ENABLE INPUT (G1 OR G2) IS LOW. OTHERWISE EACH GATE'S OUTPUT ENTERS THE HIGH IMPEDANCE (HI-Z) STATE.

G	IN	OUT
H	X	HI-Z
L	L	L
L	H	H


1-OF-2 DATA SELECTOR

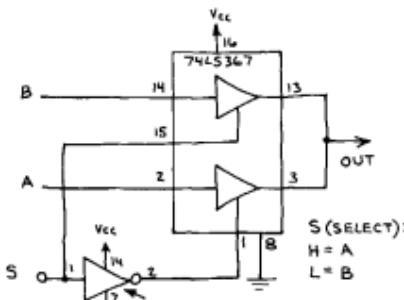


1-OF-2 DATA SELECTOR

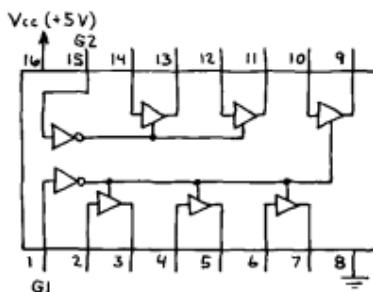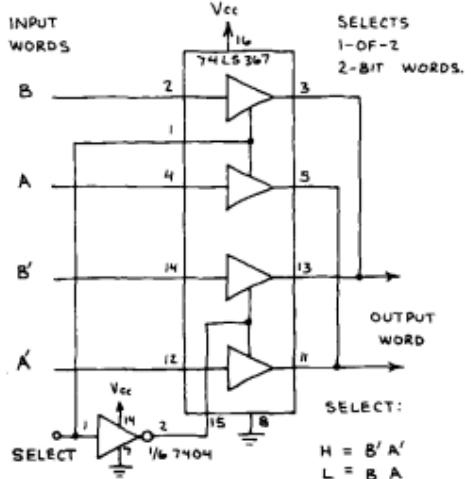

ADDING 3-STATE OUTPUT TO TTL

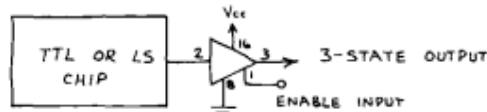


BIDIRECTIONAL DATA BUS

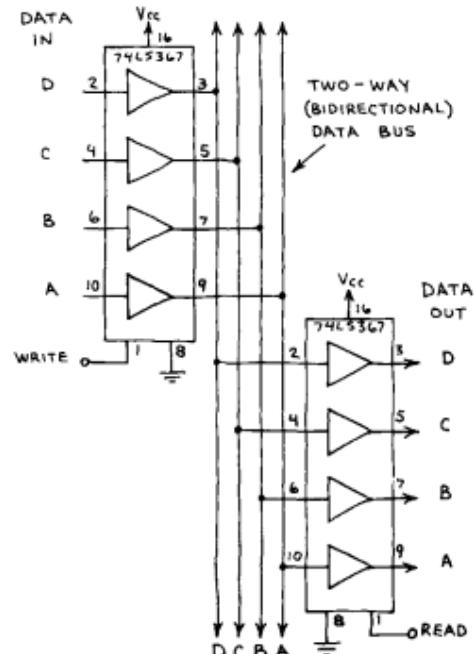


ADJUSTABLE SHUNT (ZENER) REGULATOR

TL431

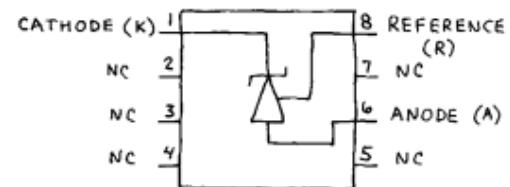EASY TO USE THREE TERMINAL ADJUSTABLE PRECISION SHUNT REGULATOR. OUTPUT CAN BE SET TO FROM 2.5 TO 36 VOLTS.




ADJUSTABLE REGULATOR

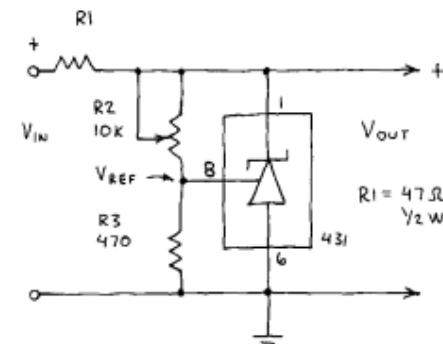


$$V_{\text{OUT}} = (1 + R_1/R_2) V_{\text{REF}} = 3-30 \text{V}$$

VOLTAGE DETECTOR

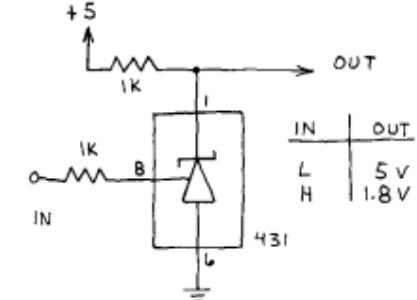


USE TO DETECT TTL LOGIC LEVELS.

SIMPLE TIMER

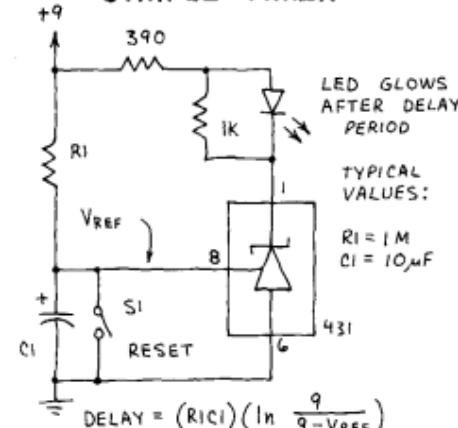


1.5 TO 5 V POWER SUPPLY

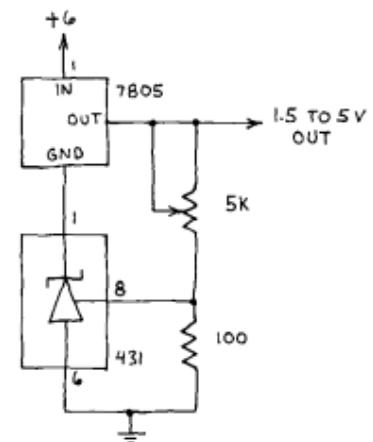

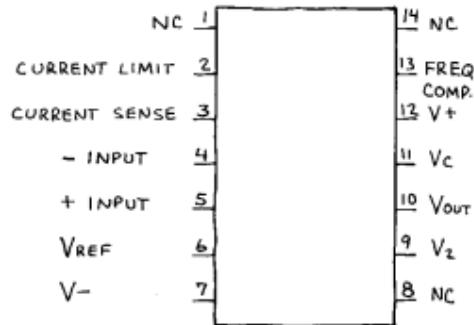
2-37 VOLT REGULATOR

723


VERY VERSATILE SERIES REGULATOR. UP TO 40 VOLTS INPUT AND 2-37 VOLT OUTPUT. MAXIMUM OUTPUT CURRENT OF 150 mA CAN BE EXTENDED TO 10 A BY ADDING EXTERNAL POWER TRANSISTORS. SHOWN BELOW ARE TWO BASIC CIRCUITS. TRY THESE, THEN SEE APPROPRIATE DATA BOOK FOR ADDITIONAL CIRCUITS.



2-7 VOLT REGULATOR

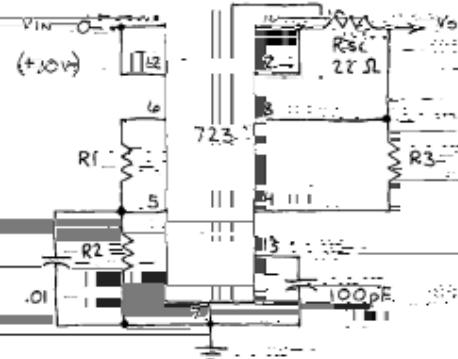

7-37 VOLT REGULATOR

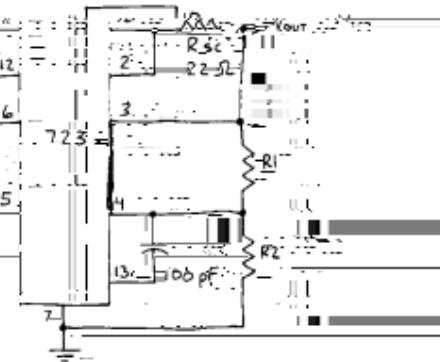

TYPICAL VALUES

V _{OUT}	R ₁	R ₂	R ₃
3.0	4.12K	3.01 K	1.74K
3.6	3.57 K	3.65 K	1.80K
5.0	2.15 K	4.99 K	1.50K
6.0	1.15 K	6.04 K	966

TYPICAL VALUES

V _{OUT}	R ₁	R ₂	R ₃
9	1.87 K	7.15 K	.48K
12	4.87 K	7.15 K	2.90K
15	7.87 K	7.15 K	3.75K
28	21.0 K	7.15 K	5.33K

FOR ANY VOLTAGE BETWEEN 2-7 VOLTS:

$$V_{out} = (V_{ref}) \times \left(\frac{R_2}{R_1 + R_2} \right)$$

*V_{ref} = 6.8-7.5 V (MEASURE AT PIN 6)

$$R_3 = \frac{R_1 R_2}{R_1 + R_2}$$

FOR ANY VOLTAGE BETWEEN 7-37 VOLTS:

$$V_{out} = (V_{ref}) \times \left(\frac{R_1 + R_2}{R_3} \right)$$

$$R_3 = \frac{R_1 R_2}{R_1 + R_2} \quad (\text{R}_3 \text{ WHICH IS OPTIONAL, GIVES TEMPERATURE STABILITY})$$


HEX 3-STATE BUS DRIVER

74LS368


EACH GATE FUNCTIONS AS AN INVERTER WHEN ITS ENABLE INPUT (G1 OR G2) IS LOW. OTHERWISE EACH GATE'S OUTPUT ENTERS THE HIGH IMPEDANCE (HI-Z) STATE.

HERE'S THE TRUTH TABLE:


G	IN	OUT
H	X	HI-Z
L	L	H
L	H	L

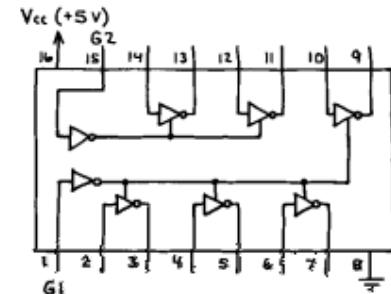

GATED LED FLASHER

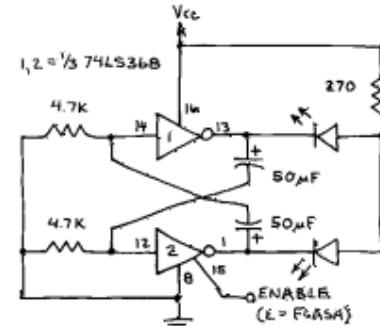


BIDIRECTIONAL DATA BUS

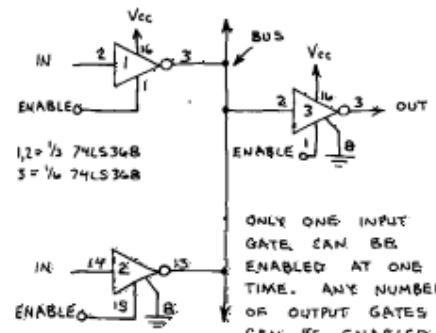


ONLY ONE INPUT GATE CAN BE ENABLED AT ONE TIME. ANY NUMBER OF OUTPUT GATES CAN BE ENABLED.

GATED TONE SOURCE

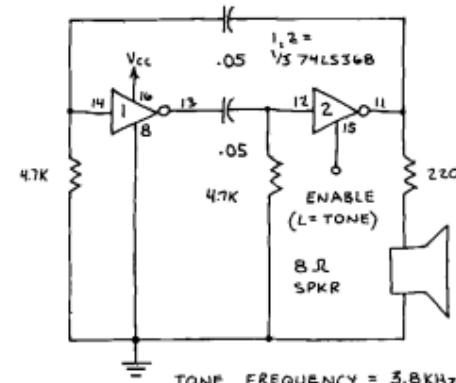


TONE FREQUENCY = 3.8kHz

BOUNCELESS SWITCH (WITH ENABLE)

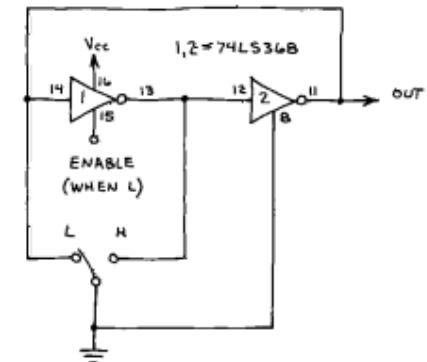


4-BIT MAGNITUDE COMPARATOR 74LS85

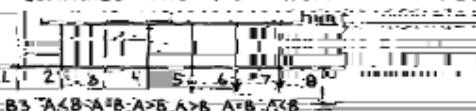
COMPARES TWO 4-BIT WORDS. INDICATES WHICH IS LARGER OR IF THEY MAKE EQUAL.



(LEDs ARE OPTIONAL)

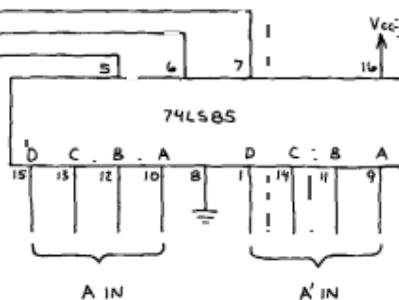

GAME

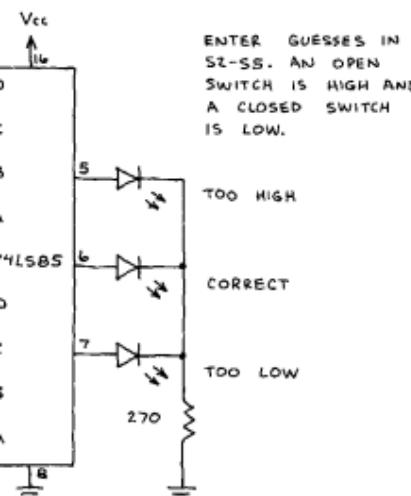


ENTER GUESSES IN S2-S5. AN OPEN SWITCH IS HIGH AND A CLOSED SWITCH IS LOW.


TOO HIGH

CORRECT


TOO LOW

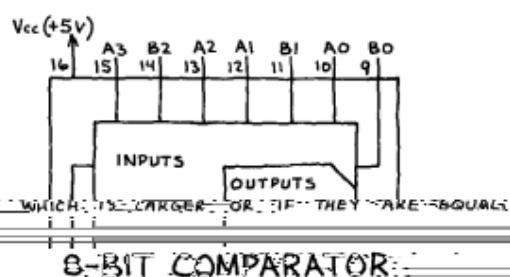

HIGH EQUAL LOW

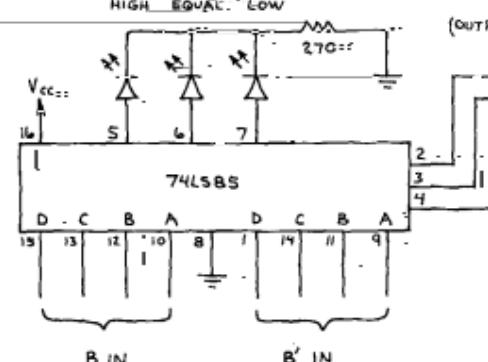


BINARY HI-LO

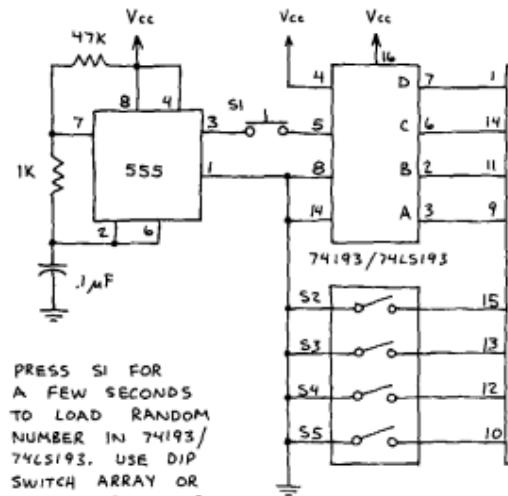

PRESS S1 FOR A FEW SECONDS TO LOAD RANDOM NUMBER IN 74193/74LS193. USE DIP SWITCH ARRAY OR TOGLES FOR S2-S5


-1.2 TO -37 VOLT REGULATOR

337T

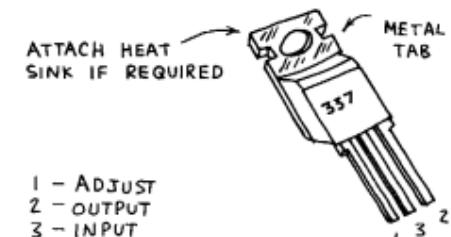


CAN SUPPLY UP TO -1.5 AMPERES OVER A -1.2 TO -37 VOLT OUTPUT RANGE. FEW EXTERNAL COMPONENTS REQUIRED. COMPLEMENTS LM317 ADJUSTABLE POSITIVE REGULATOR.

ADJUSTABLE NEGATIVE REGULATOR

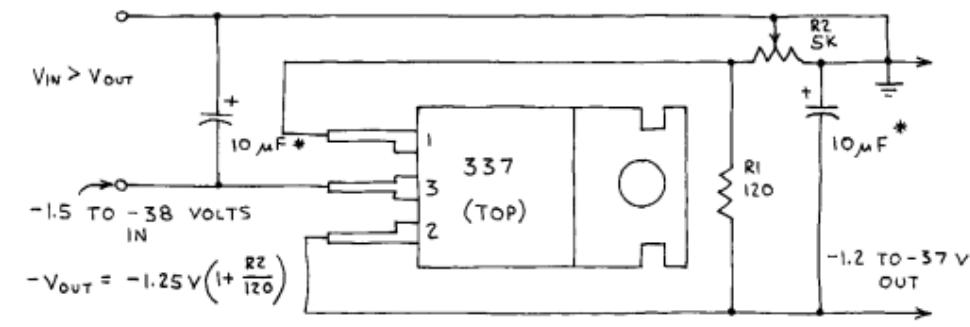

* WORKING VOLTAGE MUST EXCEED VIN.


PRECISION LED REGULATOR

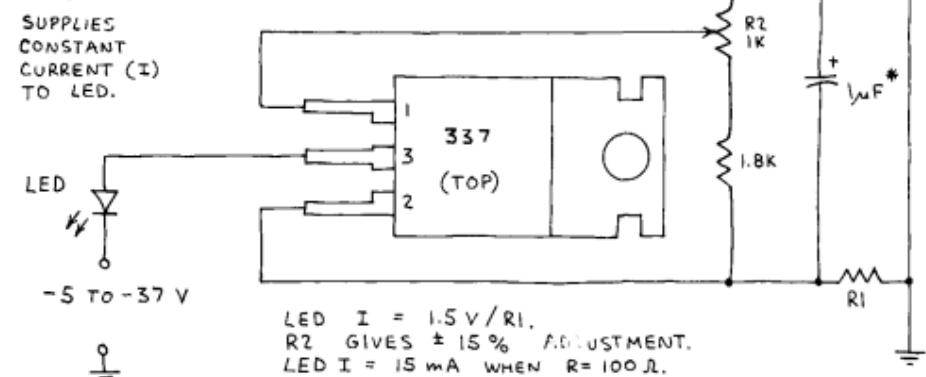


LED $I = 1.5V/R_1$.
R2 GIVES $\pm 15\%$ ADJUSTMENT.
LED $I = 15mA$ WHEN $R = 100\Omega$.

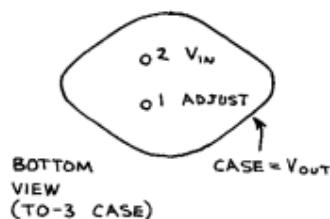1.2-37 VOLT REGULATOR LM317

CAN SUPPLY UP TO 1.5 AMPERES OVER A 1.2-37 VOLT OUTPUT RANGE. NOTE MINIMUM NUMBER OF EXTERNAL COMPONENTS IN BASIC REGULATOR CIRCUIT BELOW. USE HEAT SINK FOR APPLICATIONS REQUIRING FULL POWER OUTPUT. SEE APPROPRIATE DATA BOOK FOR ADDITIONAL INFORMATION:




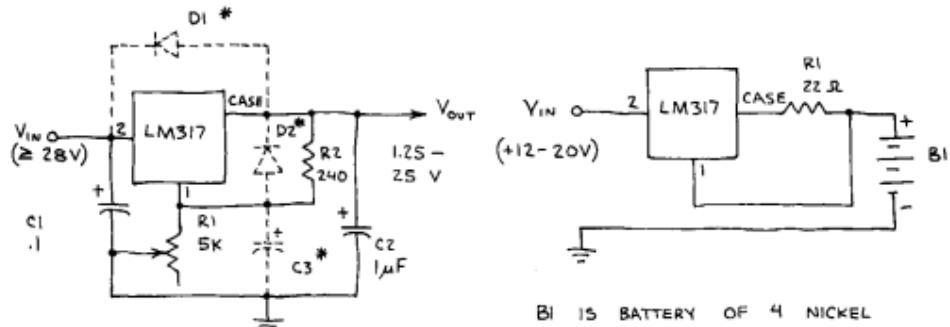1.25-25 VOLT REGULATOR 6-VOLT NICAD CHARGER




V_{IN} SHOULD BE FILTERED. OK TO OMIT C1 IF V_{IN} VERY CLOSE TO LM317.
R1 CONTROLS OUTPUT VOLTAGE.
* ADD IF OUTPUT > 25 V AND C2 > 25 μ F.

PROGRAMMABLE POWER SUPPLY

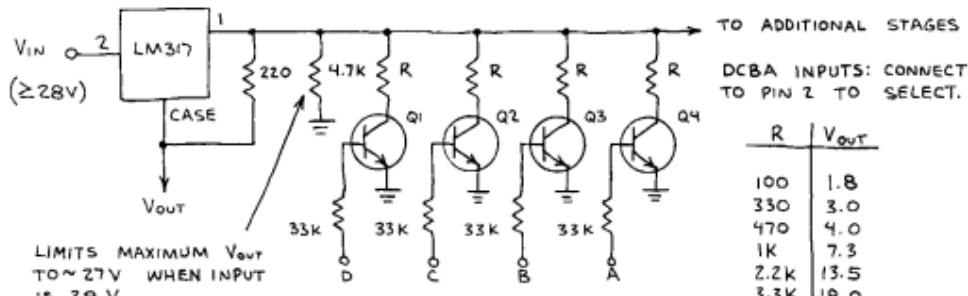


BCD-TO-DECIMAL DECODER 7441

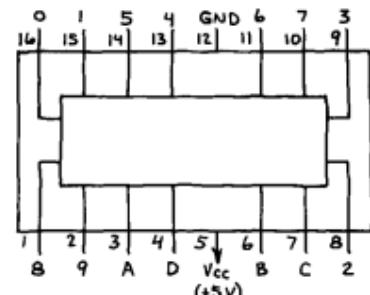
DECODES 4-BIT BCD INPUT INTO 1-OF-10 OUTPUTS. SELECTED OUTPUT GOES LOW; ALL OTHERS STAY HIGH. ORIGINALLY DESIGNED TO DRIVE GASEOUS GLOW DISCHARGE TUBES. ALL OUTPUTS GO HIGH FOR BINARY INPUTS EXCEEDING HLLH (100).



1-OF-10 DECODED COUNTER

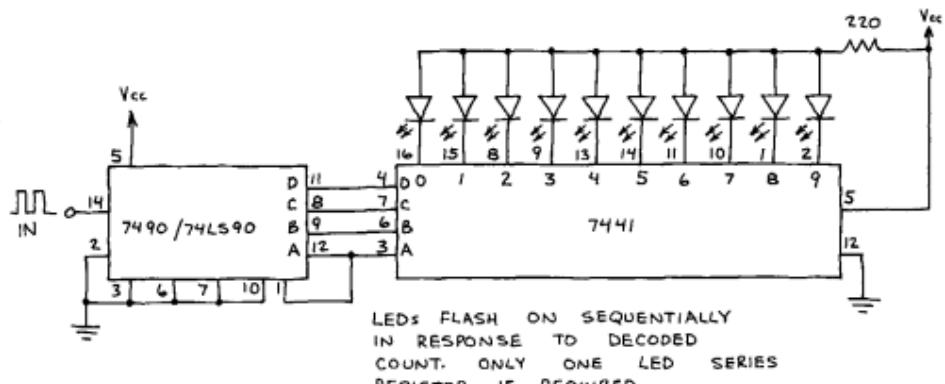

10-NOTE TONE SEQUENCER


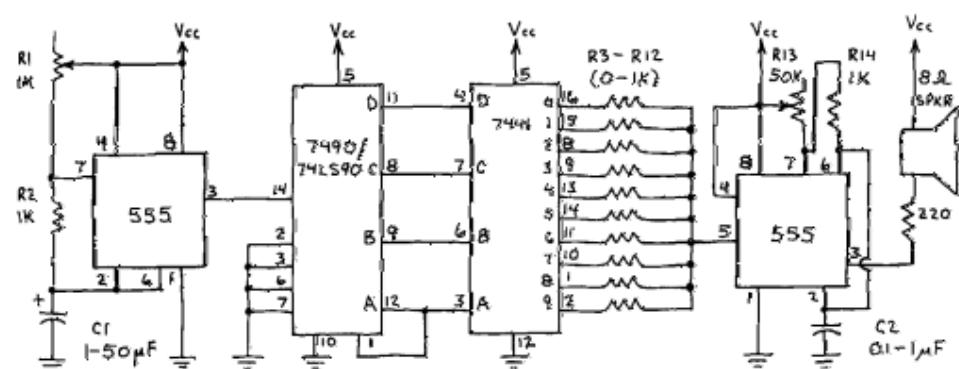


INCREASE C1 TO DECREASE TEMPO. INCREASE C2 TO INCREASE TONE FREQUENCIES. TONES ARE DETERMINED BY R3-R12.


BCD-TO-7 SEGMENT DECODER/DRIVER 7447 / 74LS47

CONVERTS BCD DATA INTO FORMAT SUITABLE FOR PRODUCING DECIMAL DIGITS ON COMMON ANODE LED 7-SEGMENT DISPLAY. WHEN LAMP TEST INPUT IS LOW, ALL OUTPUTS ARE LOW (ON). WHEN BI/RBO (BLANKING INPUT) IS LOW, ALL OUTPUTS ARE HIGH (OFF). WHEN DCBA INPUT IS LLLL (DECIMAL 0) AND RBI (RIPPLE BLANKING INPUT) IS LOW, ALL OUTPUTS ARE HIGH (OFF). THIS PERMITS UNWANTED LEADING 0's IN A ROW OF DIGITS TO BE BLANKED.


MANUALLY SWITCHED DISPLAY

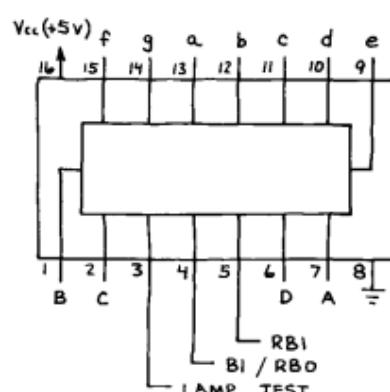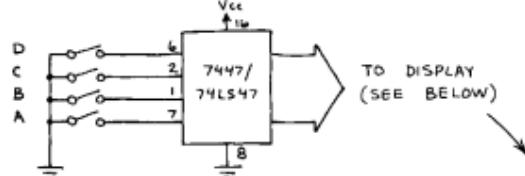

DISPLAY FLASHER

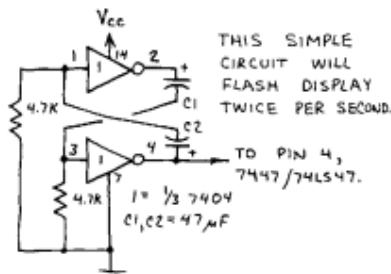


0-9 SECOND / MINUTE TIMER

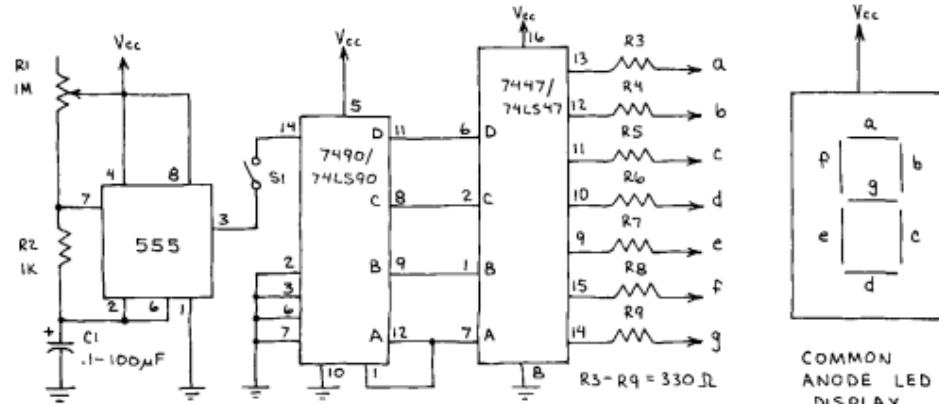

CLOSE SI TO START TIMING CYCLE. CALIBRATE 555 FOR 1 PULSE (COUNT) PER SECOND OR 1 COUNT PER MINUTE.


-5 VOLT REGULATOR 7905

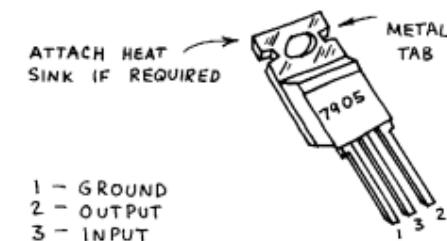


FIXED -5 VOLT REGULATOR. CAN BE USED TO GIVE ADJUSTABLE VOLTAGE OUTPUT UP TO 1.5 AMPERES OUTPUT IF PROPERLY HEAT SUNK AND SUFFICIENT INPUT CURRENT AVAILABLE. THERMAL SHUTDOWN CIRCUIT TURNS REGULATOR OFF IF HEATSINK TOO SMALL.

1 - GROUND
2 - OUTPUT
3 - INPUT

FIXED -5 VOLT REGULATOR

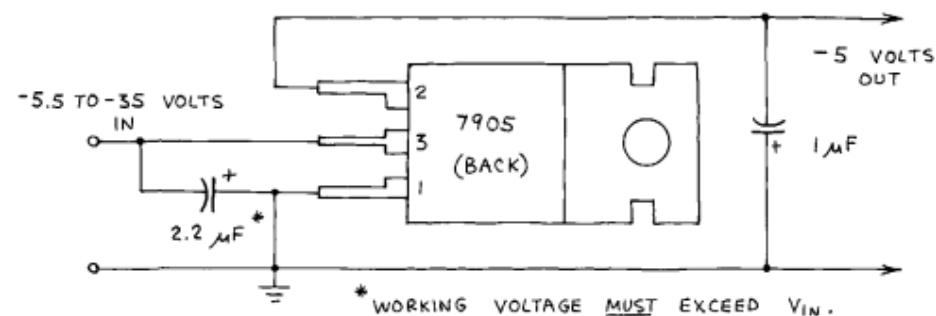

ADJUSTABLE NEGATIVE POWER SUPPLY

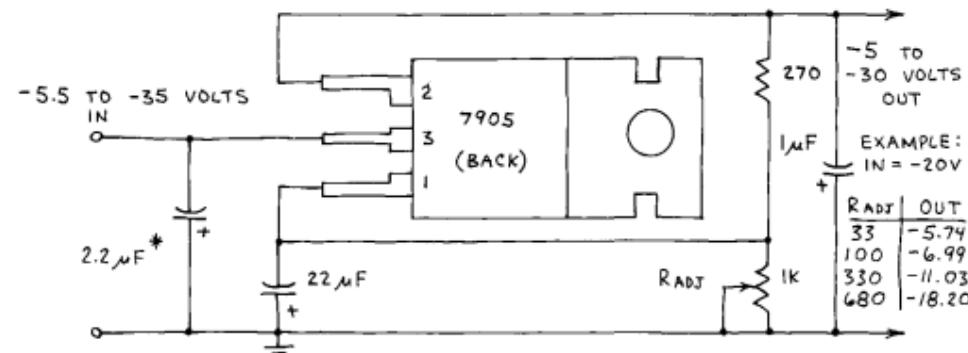


VOLTAGE REGULATORS

7805 (5-VOLTS)


7812 (12-VOLTS)

7815 (15-VOLTS)

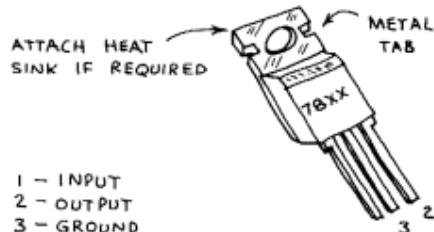
FIXED VOLTAGE REGULATORS.
IDEAL FOR STAND-ALONE
POWER SUPPLIES, ON-CARD
REGULATORS, AUTOMOBILE
BATTERY POWERED PROJECTS,
ETC. UP TO 1.5 AMPERES
OUTPUT IF PROPERLY HEAT
SUNK AND SUFFICIENT INPUT
CURRENT AVAILABLE. THERMAL
SHUTDOWN CIRCUIT TURNS OFF
REGULATOR IF HEATSINK TOO SMALL.




5-VOLT LINE POWERED TTL/LS POWER SUPPLY

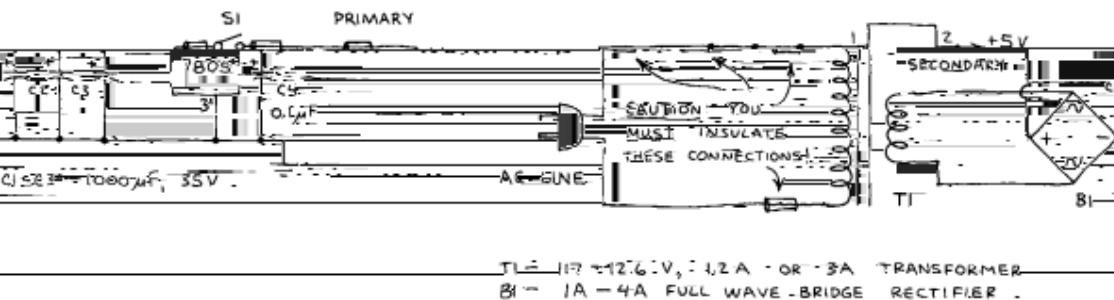

VOLTAGE REGULATOR

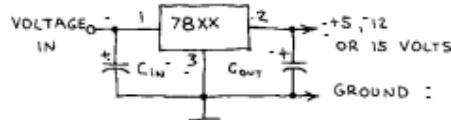


CURRENT REGULATOR

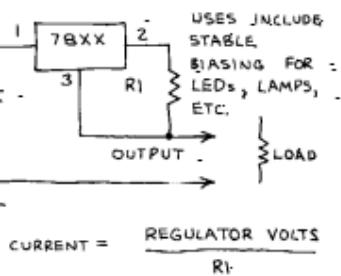

C_{IN} - OPTIONAL; USE .033 μF OR SO IF REGULATOR FAR FROM POWER SUPPLY.
C_{OUT} - OPTIONAL; USE 0.1μF OR MORE TO TRAP SPIKES THAT BOTHER LOGIC IC'S.


BCD-TO-7-SEGMENT DECODER/DRIVER 7448

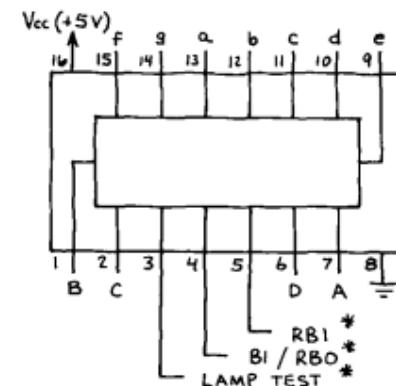CONVERTS BCD DATA INTO FORMAT SUITABLE FOR PRODUCING DECIMAL DIGITS ON COMMON CATHODE LED 7-SEGMENT DISPLAY.




* SEE 7447 FOR EXPLANATIONS.

DISPLAY DIMMER

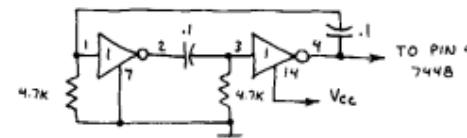


0-99 TWO DIGIT COUNTER

LOWEST ORDER DISPLAY


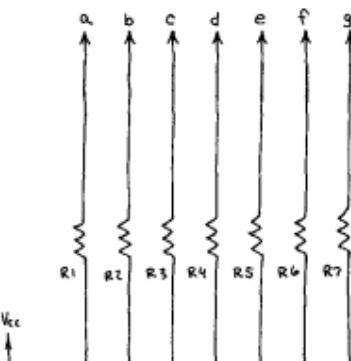


HIGHEST ORDER DISPLAY

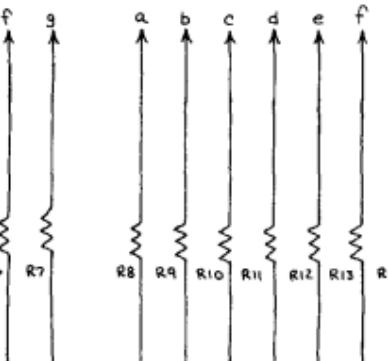


R1-R14: 330 Ω

CUR

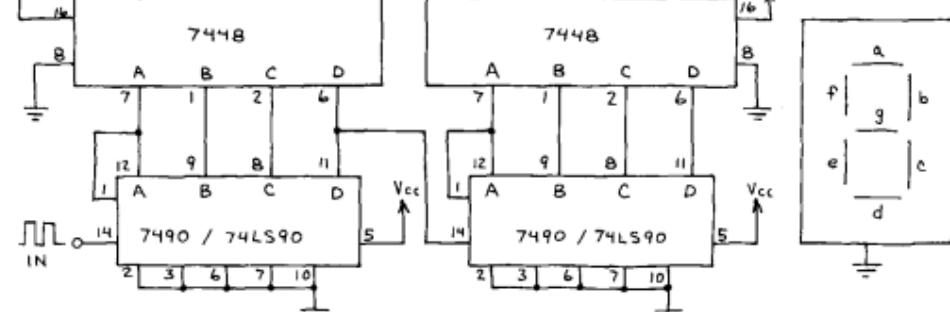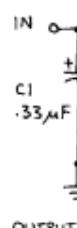


3-LINE TO 8-LINE DECODER 74LS138

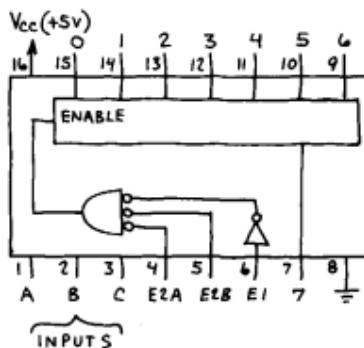
EACH 3-BIT ADDRESS DRIVES ONE OUTPUT LOW. ALL OTHERS STAY HIGH. THIS CHIP HAS THREE ENABLE INPUTS. WHEN E2 IS HIGH, ALL OUTPUTS ARE HIGH. WHEN EI IS LOW, ALL OUTPUTS ARE HIGH. TO ENABLE CHIP, MAKE EI HIGH AND E2 LOW. (NOTE: E2 = E2A + E2B.)



I-TO-8 DEMULTIPLEXER

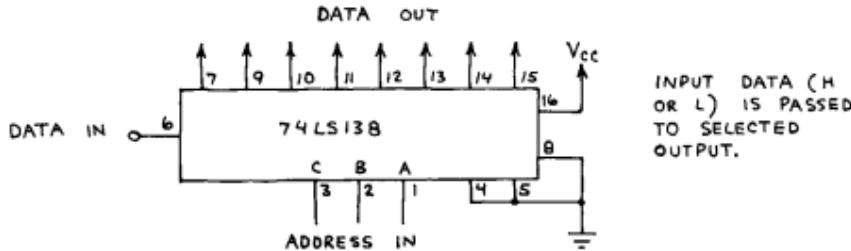


2-TO-8 STEP SEQUENCER

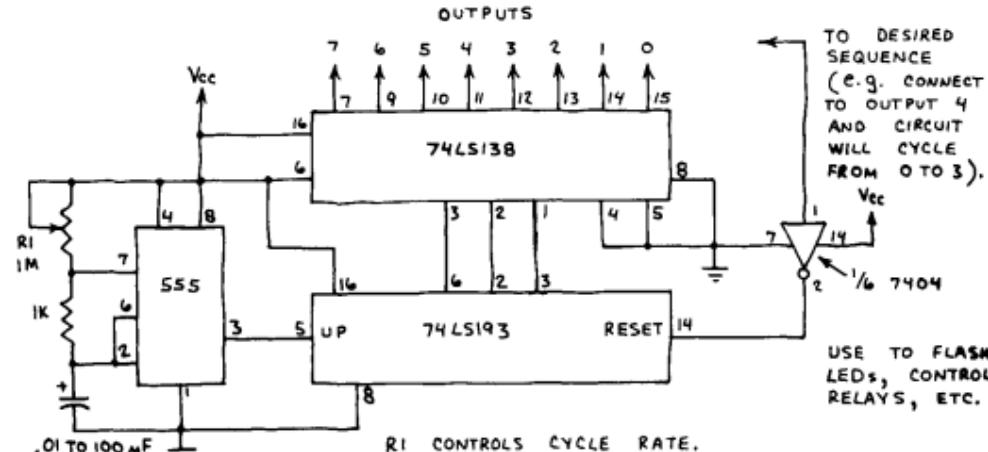

LINEAR INTEGRATED CIRCUITS

INTRODUCTION

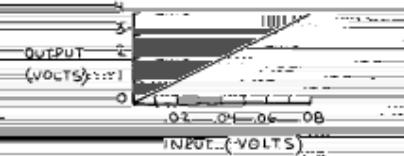THE OUTPUT OF A LINEAR IC IS PROPORTIONAL TO THE SIGNAL AT ITS INPUT. THE CLASSIC LINEAR IC IS THE OPERATIONAL AMPLIFIER. THIS GRAPH SHOWS THE LINEAR INPUT-OUTPUT RELATIONSHIP OF A TYPICAL OP-AMP CIRCUIT:



EASILY CONTROLLED WITH A SINGLE FEEDBACK RESISTOR. FET INPUT OP-AMPS (BIFETS) HAVE A VERY HIGH FREQUENCY RESPONSE. IT'S USUALLY OK TO SUBSTITUTE OP-AMPS IF BOTH ARE NORMALLY POWERED BY A DUAL POLARITY SUPPLY (1/2 LF353 FOR 741C, ETC.). BUT... PERFORMANCES SWING INAPPROPRIATELY OR DECREASE ACCORDING TO THE NEW OP-AMPS SPECIFICATIONS.

COMPARATOR

SAME AS AN OP-AMP... WITHOUT A FEEDBACK RESISTOR... ULTRA-HIGH GAIN GIVES A SNAP-LIKE RESPONSE TO AN INPUT VOLTAGE AT ONE INPUT THAT EXCEEDS A REFERENCE VOLTAGE AT THE SECOND INPUT.

TIMERS

LINEAR ICs GENERALLY REQUIRE MORE EXTERNAL COMPONENTS THAN DIGITAL ICs. THIS INCREASES THEIR SUSCEPTIBILITY TO EXTERNAL NOISE AND MAKES THEM A LITTLE TRICKIER TO USE. ON THE OTHER HAND, SOME LINEAR ICs CAN DO ESSENTIALLY THE SAME THING AS A NETWORK OF DIGITAL CHIPS.

USE ALONE OR WITH OTHER ICs FOR NUMEROUS TIMING AND PULSE GENERATION APPLICATIONS.

LED CHIPS

MOST IMPORTANT ARE A FLASHER CHIP AND A DOT-BARGRAPH ANALOG-TO-DIGITAL DISPLAY. VERY EASY TO USE.

OSCILLATORS

A VOLTAGE CONTROLLED OSCILLATOR AND A COMBINED VOLTAGE-TO-FREQUENCY AND FREQUENCY-TO-VOLTAGE CONVERTER. ALSO INCLUDED IS A TONE DECODER THAT CAN BE SET TO INDICATE A SPECIFIC FREQUENCY.

VOLTAGE REGULATORS

PROVIDE A STEADY VOLTAGE, EITHER FIXED OR ADJUSTABLE, THAT IS UN-AFFECTED BY CHANGES IN THE SUPPLY VOLTAGE AS LONG AS THE SUPPLY VOLTAGE IS ABOVE THE DESIRED OUTPUT VOLTAGE.

OPERATIONAL AMPLIFIERS

THE IDEAL AMPLIFIER... ALMOST. HIGH INPUT IMPEDANCE AND GAIN. LOW OUTPUT IMPEDANCE. GAIN IS


THIS SECTION INCLUDES SEVERAL EASY TO USE POWER AMPLIFIERS THAT ARE IDEAL FOR DO-IT-YOURSELF STEREO, PUBLIC ADDRESS SYSTEMS, INTERCOMS AND OTHER AUDIO APPLICATIONS.

AUDIO AMPLIFIERS

OCTAL BUS TRANSCEIVER 74LS245

ALLOWS DATA TO BE TRANSFERRED IN EITHER DIRECTION BETWEEN TWO BUSES. INCLUDES HIGH IMPEDANCE (HI-Z) OUTPUTS.

BUS TRANSCEIVER

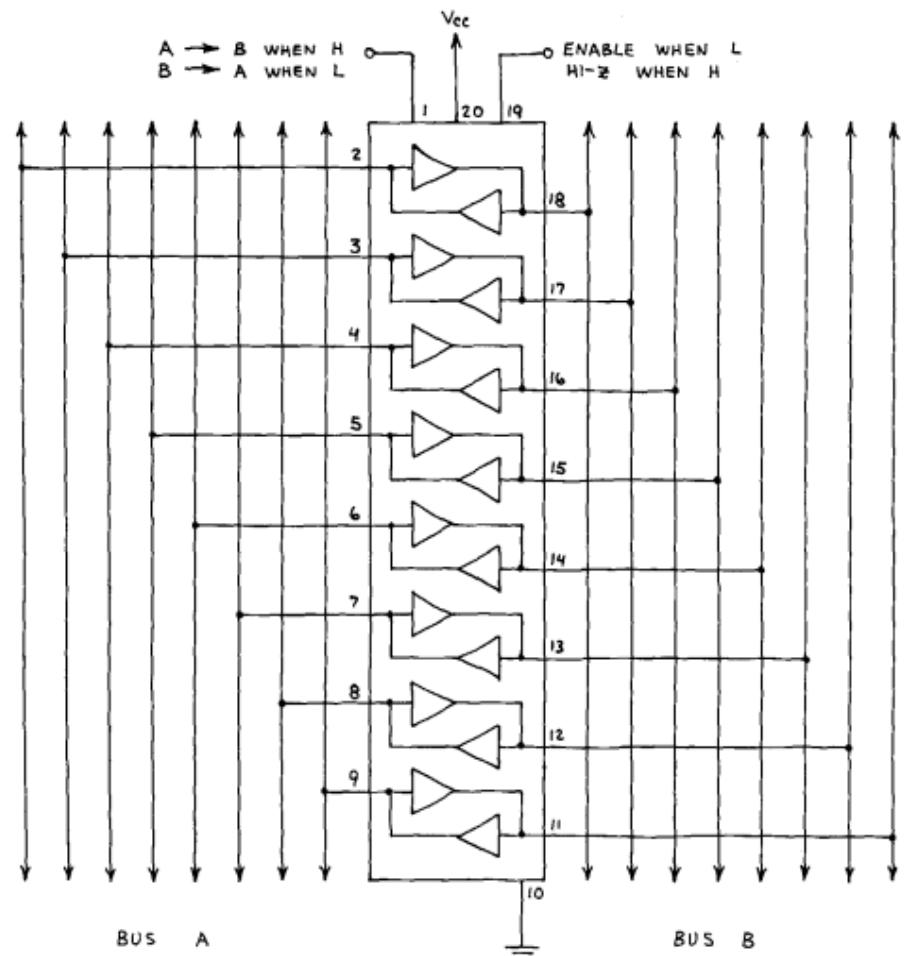


4-LINE TO 16-LINE


DECODER

74154

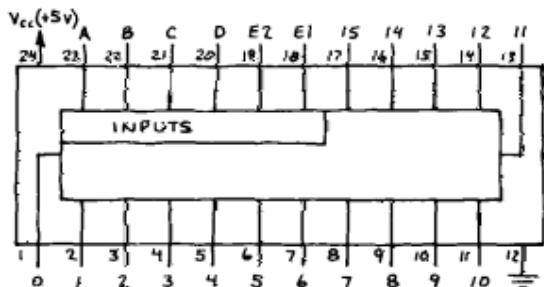
EACH 4-BIT ADDRESS DRIVES ONE OUTPUT LOW. ALL OTHERS STAY HIGH. ENABLE INPUTS (E1 AND E2) MUST BE LOW. IF ONE OR BOTH ARE HIGH, ALL OUTPUTS GO LOW.



1-TO-16 DEMULTIPLEXER

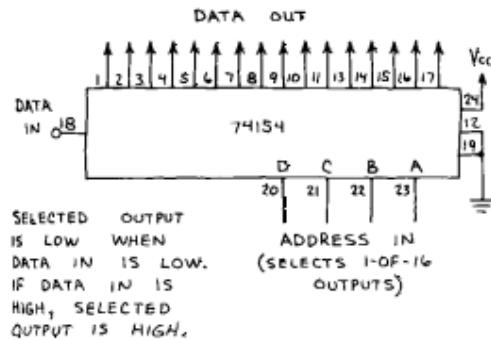

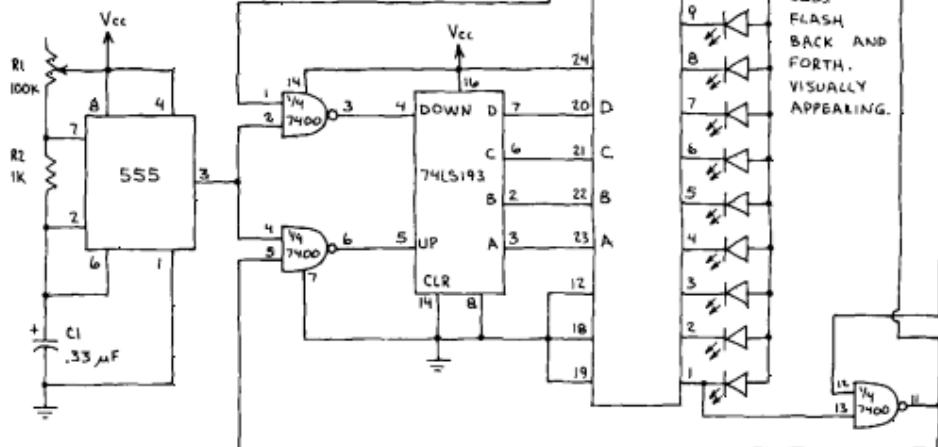SELECTED OUTPUT IS LOW WHEN DATA IN IS LOW. IF DATA IN IS HIGH, SELECTED OUTPUT IS HIGH.





INCREASE R1 TO SLOW FLASH RATE.

BACK AND FORTH FLASHER


QUAD 1-OF-2 DATA SELECTOR 74LS157

FOUR 2-LINE TO 1-LINE MULTIPLEXERS.
MANY USES IN ROUTING DATA. ALL
4 DATA SELECTORS ARE ENABLED
WHEN PIN 15 IS LOW.


DOUBLE DUTY DISPLAY

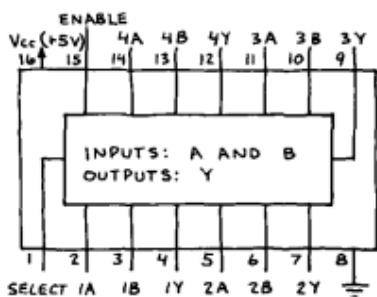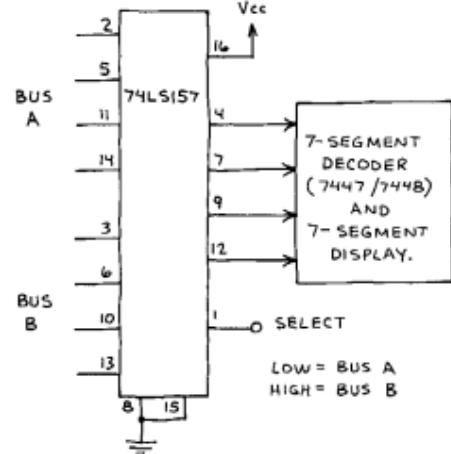

BUS SELECTOR

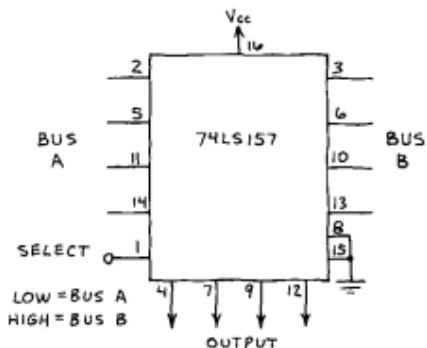


WORD SORTER

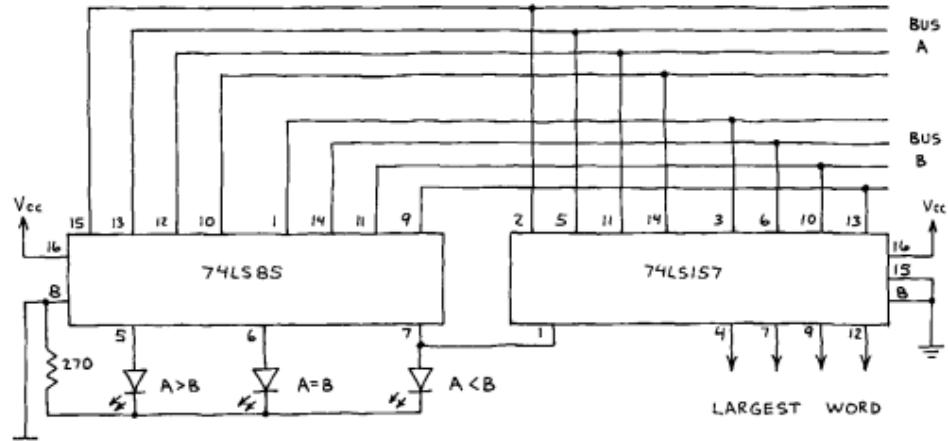


THIS CIRCUIT CONTINUALLY MONITORS TWO DATA BUSES. BUS WITH HIGHEST MAGNITUDE DATA WORD IS ROUTED AUTOMATICALLY TO OUTPUT.

OCTAL D FLIP-FLOP 74LS374

EIGHT D-TYPE EDGE TRIGGERED FLIP-FLOPS. UNLIKE 74LS373, OUTPUTS DO NOT FOLLOW INPUTS. INSTEAD, A RISING CLOCK PULSE AT PIN 11 LOADS DATA APPEARING AT INPUTS. THIS CHIP HAS 3-STATE OUTPUTS WHICH ARE CONTROLLED BY PIN 1.

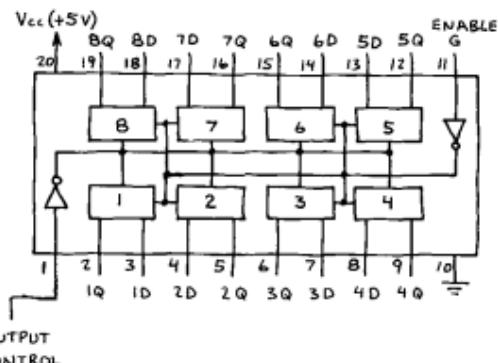


CLOCKED 3-STATE REGISTER

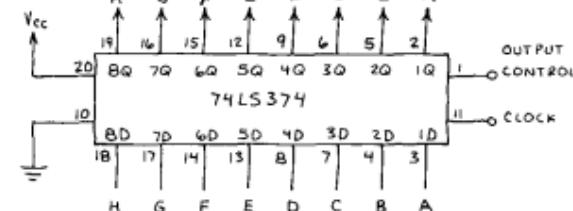

GENERAL PURPOSE CLOCKED REGISTER. HERE'S THE TRUTH TABLE:

OUTPUT CONTROL	CLOCK	D	Q
L	—	H	H
L	—	L	L
L	—	X	X
H	X	X	HI-Z

COMMON INPUT/OUTPUT BUS REGISTER

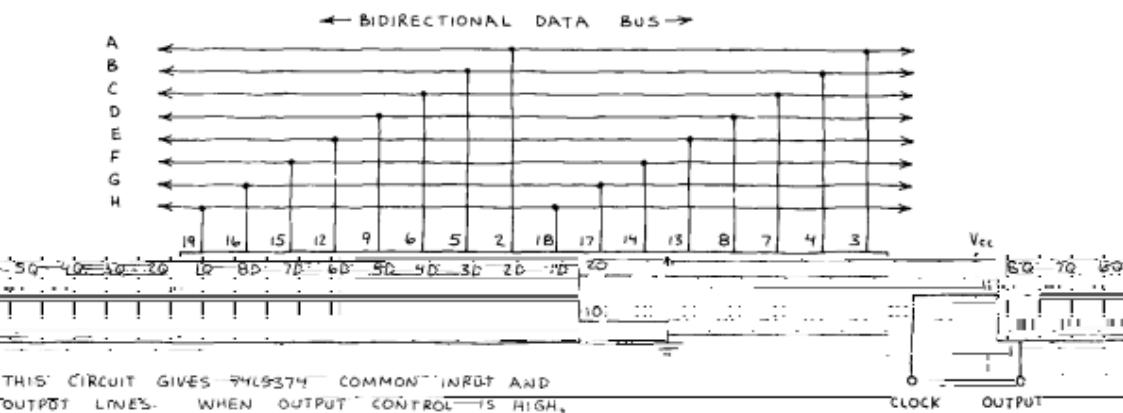


THIS CIRCUIT GIVES 74LS374 COMMON INPUT AND OUTPUT LINES. WHEN OUTPUT CONTROL IS HIGH, DATA ON BUS 15 IS LOADED INTO THE 74LS374 ON THE RISING EDGE (J) OF THE CLOCK PULSE. WHEN OUTPUT CONTROL IS LOW, DATA IN THE 74LS374 IS WRITTEN ONTO THE BUS.


OCTAL D-TYPE LATCH

74LS373

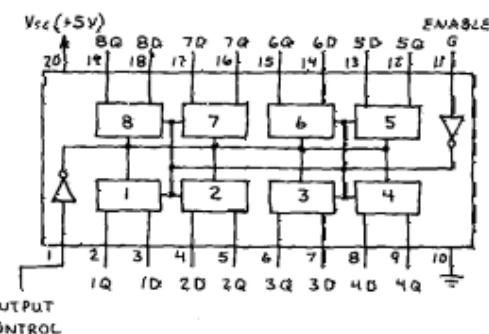EIGHT "TRANSPARENT" D-TYPE LATCHES. OUTPUT FOLLOWS INPUT WHEN ENABLE IS HIGH. THE DATA AT THE INPUTS IS LOADED WHEN THE ENABLE INPUT IS LOW. THIS CHIP HAS 3-STATE OUTPUTS WHICH ARE CONTROLLED BY PIN 1. SEE TRUTH TABLE BELOW.




3-STATE REGISTER

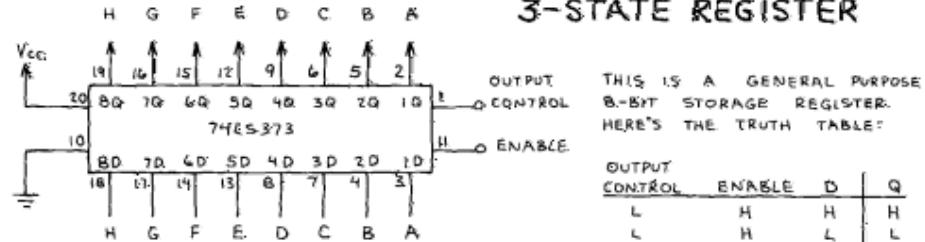

THIS IS A GENERAL PURPOSE 8-BIT STORAGE REGISTER. HERE'S THE TRUTH TABLE:

OUTPUT CONTROL	ENABLE	D	Q
L	H	H	H
L	H	L	L
L	L	X	Q
H	X	X	H-Z

DATA BUS REGISTERS

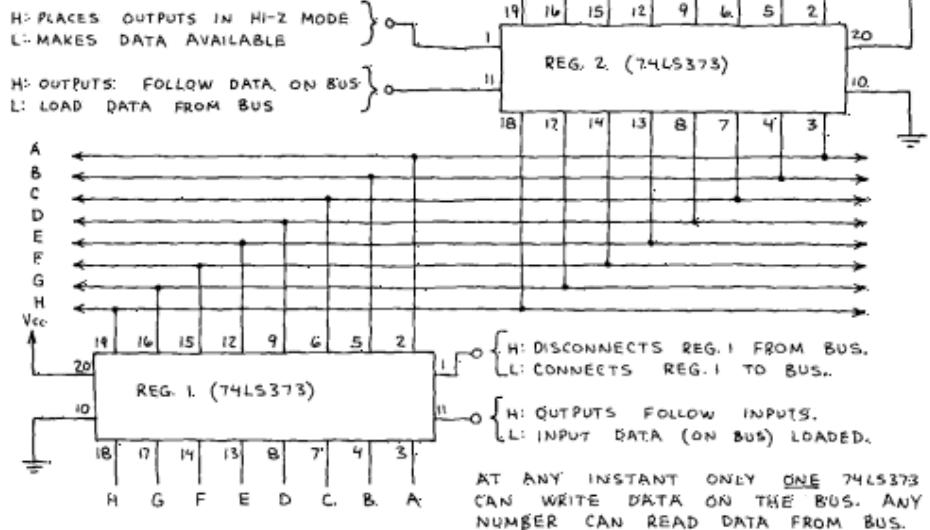

H: PLACES OUTPUTS IN HI-Z MODE
L: MAKES DATA AVAILABLE

H: OUTPUTS FOLLOW DATA ON BUS
L: LOAD DATA FROM BUS

A
B
C
D
E
F
G
H
Vcc
14 16 15 12 9 6 5 2
REG. 1 (74LS373)
10
18 17 14 13 8 7 4 3
H G F E D C B A

H: DISCONNECTS REG. 1 FROM BUS.
L: CONNECTS REG. 1 TO BUS.

H: OUTPUTS FOLLOW INPUTS.
L: INPUT DATA (ON BUS) LOADED.

AT ANY INSTANT ONLY ONE 74LS373 CAN WRITE DATA ON THE BUS. ANY NUMBER CAN READ DATA FROM BUS.


I-OF-8 DATA SELECTOR

74LS151


EQUIVALENT TO 8-LINE TO 1-LINE MULTIPLEXER.

PROGRAMMABLE GATE

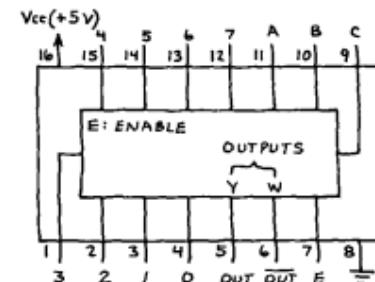3-BIT ADDRESS SELLECTS ONE SWITCH AND APPLIES ITS STATUS (OPEN HIGH AND CLOSED = LOW) TO THE OUTPUT. ANY 3-INPUT LOGIC FUNCTION CAN BE PROGRAMMED IN SECONDS.



PATTERN GENERATOR

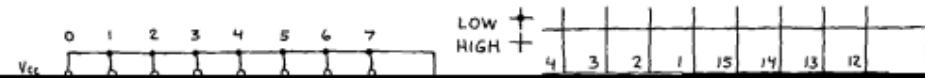



DUAL ONE-SHOT

V_{cc} (+5 v)

2 IN 2 IN

OCTAL BUFFER 74LS244

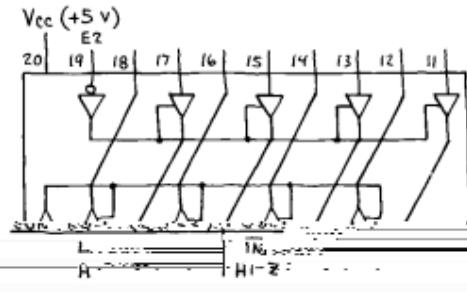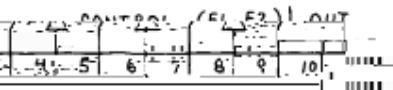NON-INVERTING VERSION
OF 74LS240. IDEAL FOR
COMPUTER INTERFACING.




TRANSFER

4-BIT BUS TRANSFER

FROM BUS


TO BUS

FRO

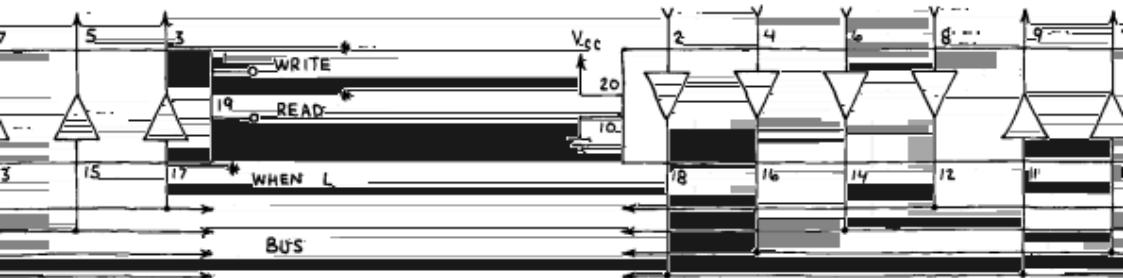

TRANSFER


8-BIT BUS BUFFER

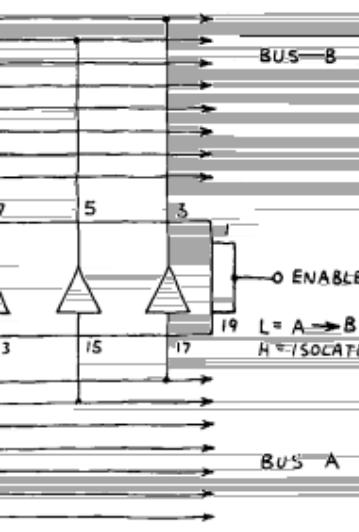


OCTAL BUFFER

74LS240

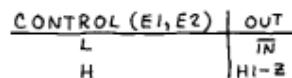
IDEAL FOR INTERFACING
EXTERNAL CIRCUITS TO
HOME COMPUTERS.
INVERTS DATA.



4-BIT BUS TRANSFER

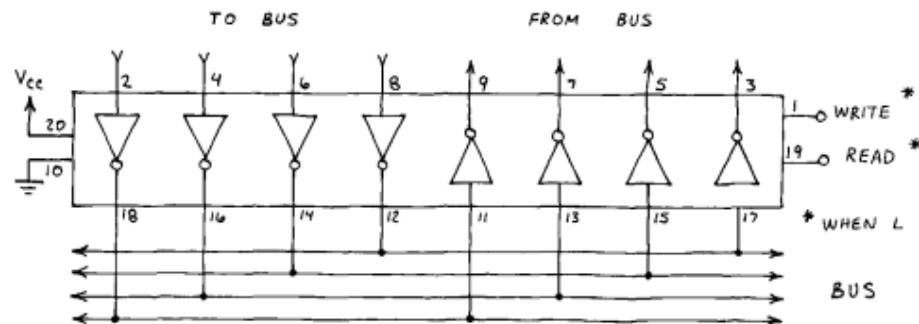

8-BIT BUS BUFFER

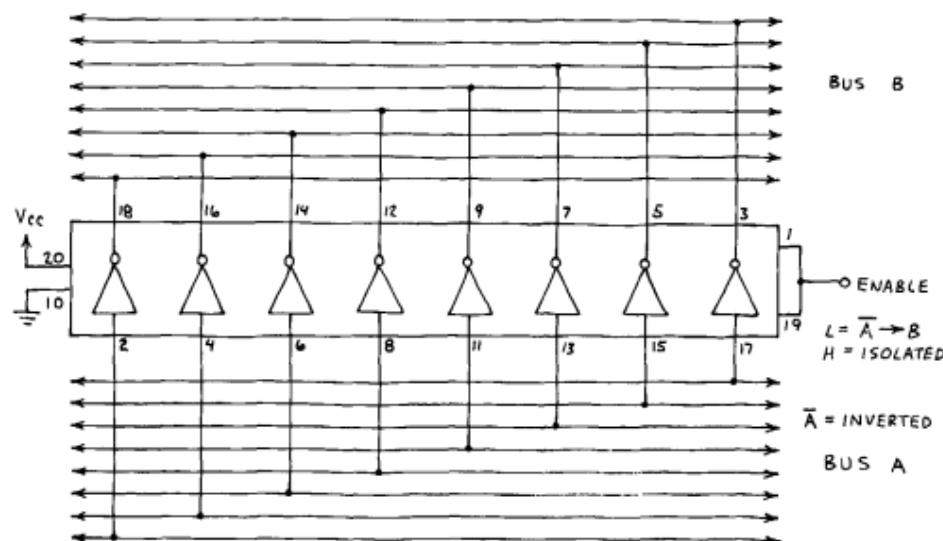


DUAL D FLIP-FLOP

7474 / 74LS74

TWO D (DATA) FLIP-FLOPS IN A SINGLE PACKAGE. DATA AT D INPUT IS STORED AND MADE AVAILABLE AT Q OUTPUT WHEN CLOCK PULSE (ϕ) GOES HIGH. HERE'S THE TRUTH TABLE:


RESET	CLEAR	CLOCK	D	Q	\bar{Q}
L	H	X	X	H	L
H	L	X	X	L	H
H	H	↑	H	H	L
H	H	↑	L	L	H

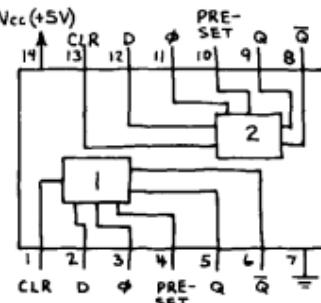


ϕ IS CLOCK INPUT.

↑ IS RISING EDGE OF CLOCK PULSE.


2-BIT STORAGE REGISTER

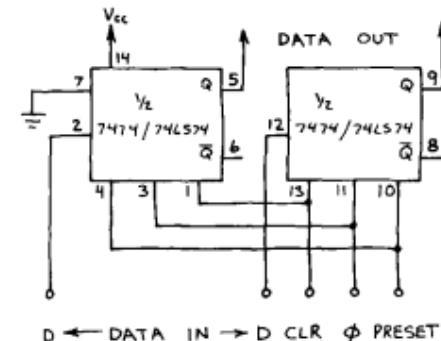

WAVE SHAPER

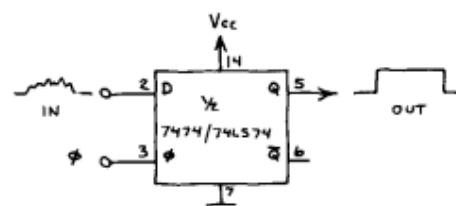


PHASE DETECTOR

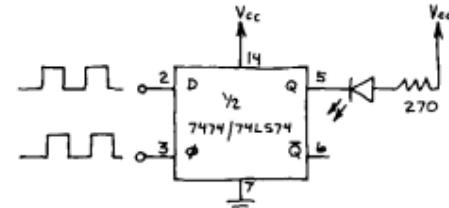

THE LED GLOWS WHEN INPUT FREQUENCIES F1 AND F2 ARE UNEQUAL OR OUT OF PHASE.
F1 AND F2 SHOULD BE SQUARE WAVES.

DIVIDE-BY-TWO COUNTER

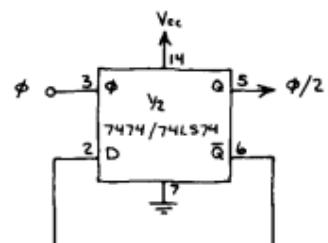


DUAL J-K FLIP-FLOP

7473


TWO JK FLIP-FLOPS IN A SINGLE PACKAGE. NOTE THE CLEAR INPUTS. THESE FLIP-FLOPS WILL TOGGLE (SWITCH OUTPUT STATES) IN RESPONSE TO INCOMING CLOCK PULSES WHEN BOTH J AND K INPUTS ARE HIGH. HERE'S THE TRUTH TABLE:

CLEAR	CLOCK	J	K	Q	\bar{Q}
L	X	X	X	L	H
H	L	H	L	H	L
H	L	L	H	L	H
H	L	H	H	TOGGLE	

DIVIDE-BY-TWO

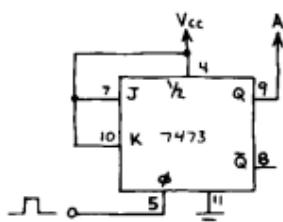

DIVIDE-BY-THREE

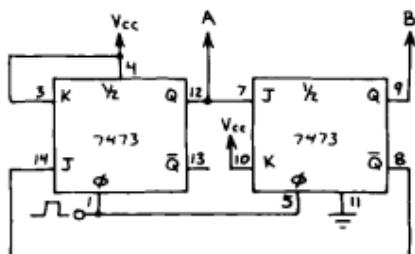


BINARY COUNTERS

THE THREE CIRCUITS ON THIS PAGE ARE BINARY COUNTERS THAT COUNT UP TO THE MAXIMUM COUNT AND AUTOMATICALLY RECYCLE. CONNECT A DECODER TO OUTPUT OF DIVIDE-BY-THREE AND DIVIDE-BY-FOUR COUNTERS TO OBTAIN ONE-OF-THREE AND ONE-OF-FOUR OPERATION. THIS TRUTH TABLE SUMMARIZES OPERATION OF THESE COUNTERS:

DIVIDE-BY: TWO		THREE		FOUR	
OUTPUTS:	A	B	A	B	A
L	L	L	L	L	L
H	L	H	L	H	L
H	L	L	H	L	H
					H


DIVIDE-BY-FOUR

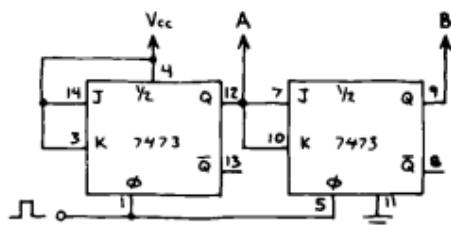

8-BIT SHIFT REGISTER


74LS164

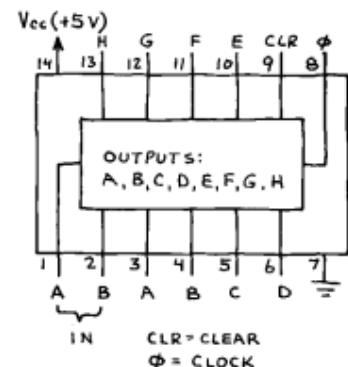DATA AT ONE OF THE TWO SERIAL INPUTS IS ADVANCED ONE BIT FOR EACH CLOCK PULSE. DATA CAN BE EXTRACTED FROM THE 8 PARALLEL OUTPUTS OR IN SERIAL FORM AT ANY SINGLE OUTPUT. ENTER DATA AT EITHER INPUT. THE UNUSED INPUT MUST BE HELD HIGH OR CLOCKING WILL BE INHIBITED. MAKING PIN 9 LOW CLEARS THE REGISTER TO LLLL.




8-BIT SERIAL-TO-PARALLEL DATA CONVERTER

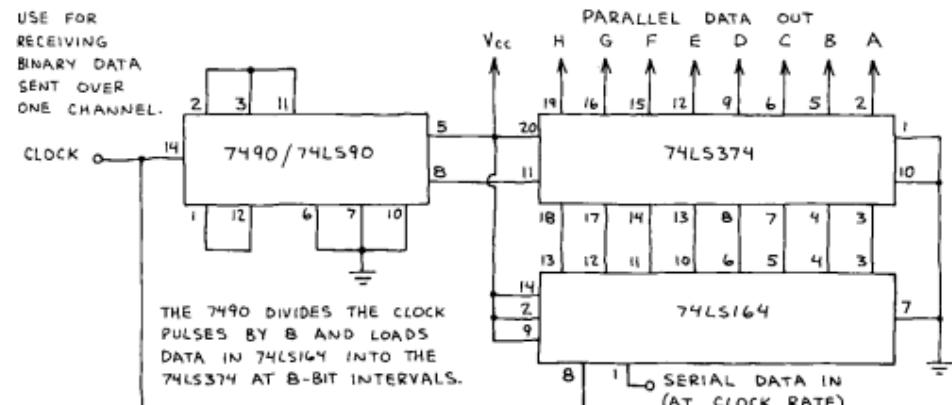USE FOR RECEIVING BINARY DATA SENT OVER ONE CHANNEL.



THE 7490 DIVIDES THE CLOCK PULSES BY B AND LOADS DATA IN 74LS164 INTO THE 74LS374 AT B-BIT INTERVALS.

PSEUDO-RANDOM VOLTAGE GENERATOR

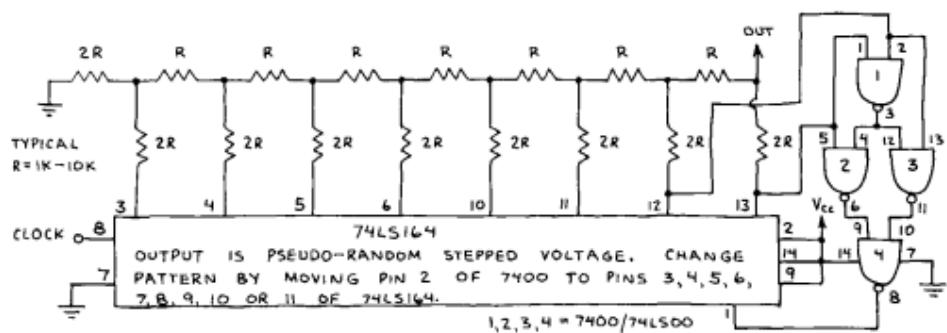


TYPICAL R=1K-10K
CLOCK 0 8
74LS164
OUTPUT IS PSEUDO-RANDOM STEPPED VOLTAGE. CHANGE PATTERN BY MOVING PIN 2 OF 7400 TO PINS 3,4,5,6,7,8,9,10 OR 11 OF 74LS164.

1,2,3,4 = 7400/74LS00

4-BIT SHIFT REGISTER 74LS194


BIDIRECTIONAL UNIVERSAL SHIFT REGISTER. SHIFTS RIGHT WHEN SO IS HIGH AND SI IS LOW. SHIFTS LEFT WHEN SO IS LOW AND SI IS HIGH. SHIFTS ONE POSITION PER CLOCK PULSE. LOADS DATA AT INPUTS WHEN SO AND SI ARE HIGH. IMPORTANT: BYPASS POWER SUPPLY PINS WITH 0.1MF CAPACITOR!

SEQUENCE GENERATOR

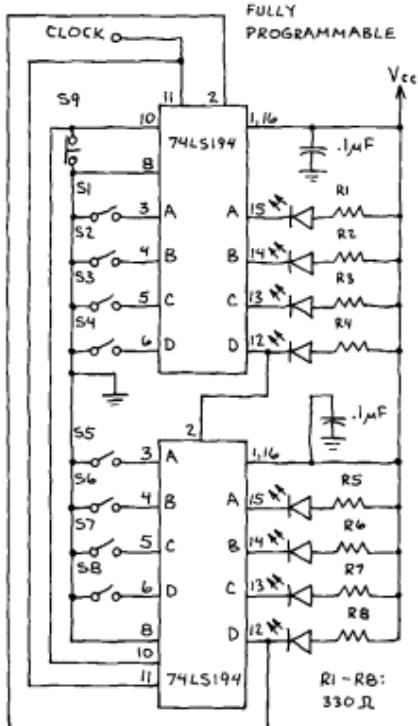


LOAD ANY DESIRED BIT PATTERN INTO S1-S8 (OPEN = HIGH AND CLOSED = LOW). PRESS S9 (NORMALLY CLOSED) TO LOAD. DATA WILL MOVE RIGHT ONE OUTPUT PER CLOCK PULSE. LEDs ARE OPTIONAL.

78

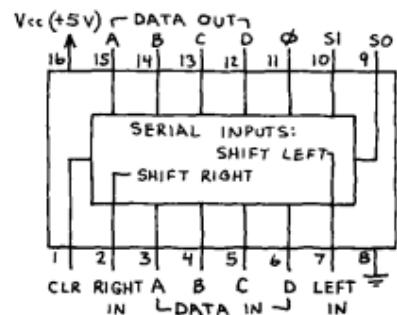

BARGRAPH GENERATOR

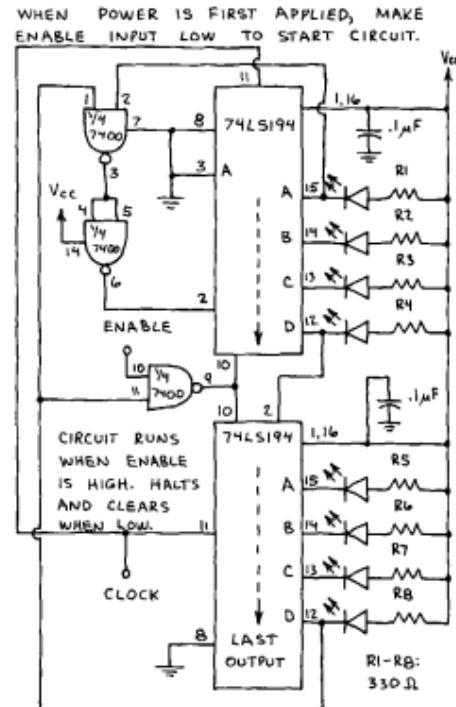


OUTPUTS GO LOW AND STAY LOW ONE AT A TIME FROM LEFT TO RIGHT (A → D) IN SEQUENCE WITH CLOCK. WHEN FINAL OUTPUT GOES LOW, ALL OUTPUTS BUT THE FIRST GO HIGH AND RECYCLE.

DUAL J-K FLIP-FLOP 7476

TWO JK FLIP-FLOPS IN A SINGLE PACKAGE. SIMILAR TO 7473/74LS73 BUT HAS BOTH PRESET AND CLEAR INPUTS. FLIP-FLOPS WILL TOGGLE (SWITCH OUTPUT STATES) IN RESPONSE TO INCOMING CLOCK PULSES WHEN BOTH J AND K INPUTS ARE HIGH. HERE'S THE TRUTH TABLE:


PRE	CLR	CLK	J	K	Q	\bar{Q}
L	H	X	X	X	H	L
H	L	X	X	X	L	H
H	H	X	H	L	H	L
H	H	X	L	H	L	H
H	H	X	H	H	TOGGLE	

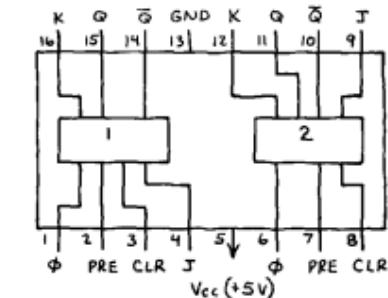


PRE = PRESET
CLR = CLEAR
 ϕ = CLOCK (OR CLK)

TOGGLE = FLIP-FLOP SWITCHES
OUTPUT STATES IN
RESPONSE TO CLOCK
PULSES.

4-BIT SERIAL SHIFT REGISTER

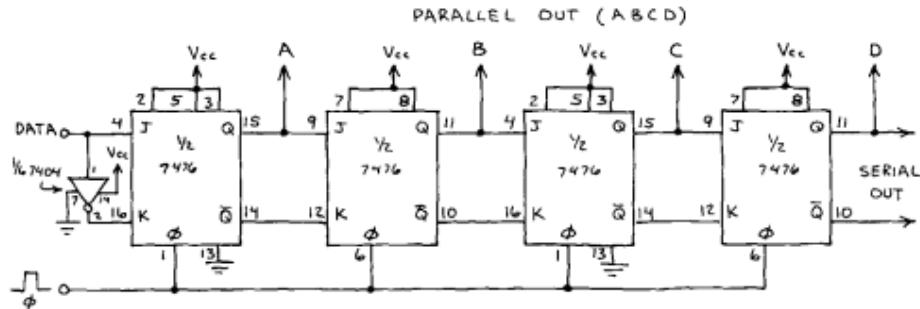


4-BIT BINARY UP COUNTER

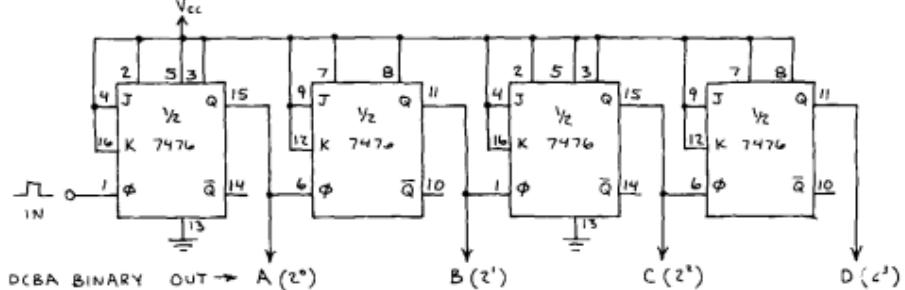

67


QUAD LATCH 7475/74LS75

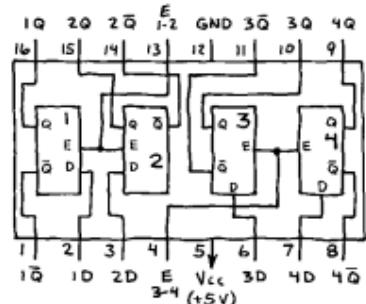A 4-BIT BISTABLE LATCH. PRIMARILY USED TO STORE THE COUNT IN DECIMAL COUNTING UNITS. NOTE THAT BOTH Q AND \bar{Q} OUTPUTS ARE PROVIDED. ALSO NOTE THE E (ENABLE) INPUTS. WHEN E IS HIGH, Q FOLLOWS D.




4-BIT DATA LATCH

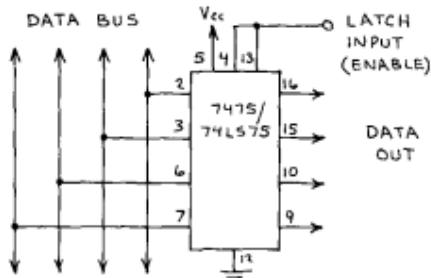DATA ON BUS APPEARS AT OUTPUTS WHEN LATCH INPUT IS HIGH. DATA ON BUS WHEN LATCH INPUT GOES LOW IS STORED UNTIL LATCH INPUT GOES HIGH. (LATCH INPUT CONTROLS BOTH ENABLE INPUTS) TWO QUAD LATCHES CAN BE USED AS AN 8-BIT DATA LATCH.



NOTES

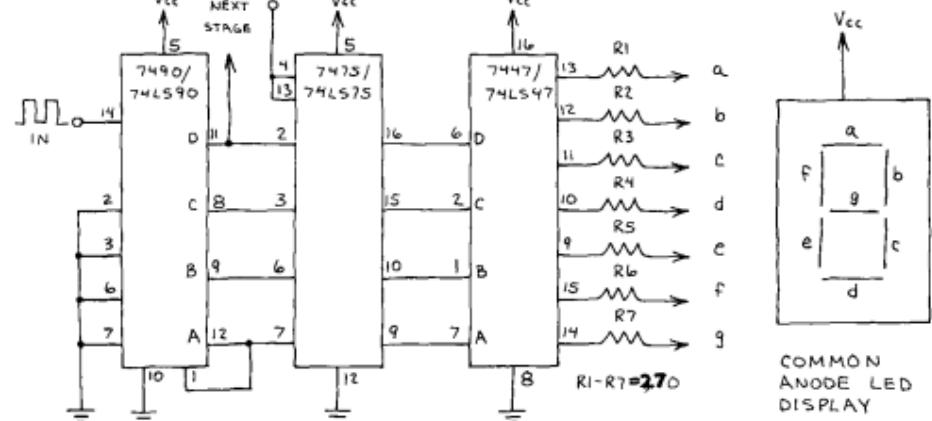


EXPANDABLE DECADE COUNTER. FOR TWO DIGIT COUNT, CONNECT PIN 11 OF 7490/74LS90 OF FIRST UNIT TO INPUT OF SECOND UNIT. A LOW AT THE LATCH INPUT FREEZES THE DATA BEING DISPLAYED.

4-BIT UP-DOWN COUNTER


74193 / 74LS193

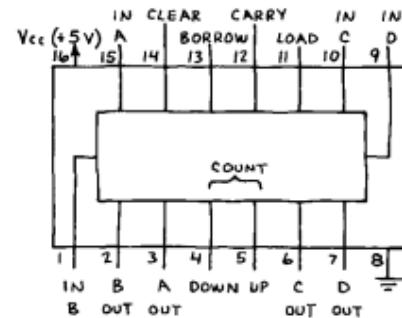VERY VERSATILE 4-BIT COUNTER WITH UP-DOWN CAPABILITY. ANY 4-BIT NUMBER AT THE DCBA INPUTS IS LOADED INTO THE COUNTER WHEN THE LOAD INPUT (PIN 11) IS MADE LOW. THE COUNTER IS CLEARED TO LLLL WHEN THE CLEAR INPUT (PIN 14) IS MADE HIGH. THE BORROW AND CARRY OUTPUTS INDICATE UNDERFLOW OR OVERFLOW BY GOING LOW.




COUNT DOWN FROM N AND RECYCLE

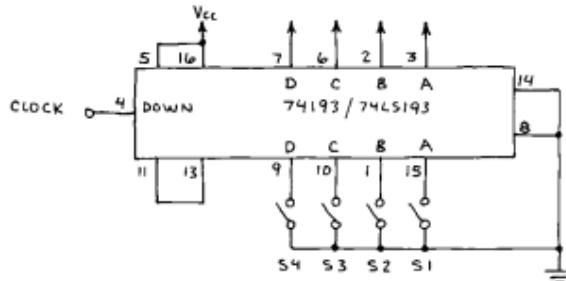SET DESIRED N INTO SI-54 (CLOSED SWITCH = LOW AND OPEN SWITCH = HIGH). WHEN COUNT REACHES LLLL AND THEN UNDERFLOWS, THE BORROW PULSE LOADS N AND THE COUNT RECYCLES.




COUNT UP TO N AND HALT

PRESS SI (NORMALLY CLOSED) TO RESET.

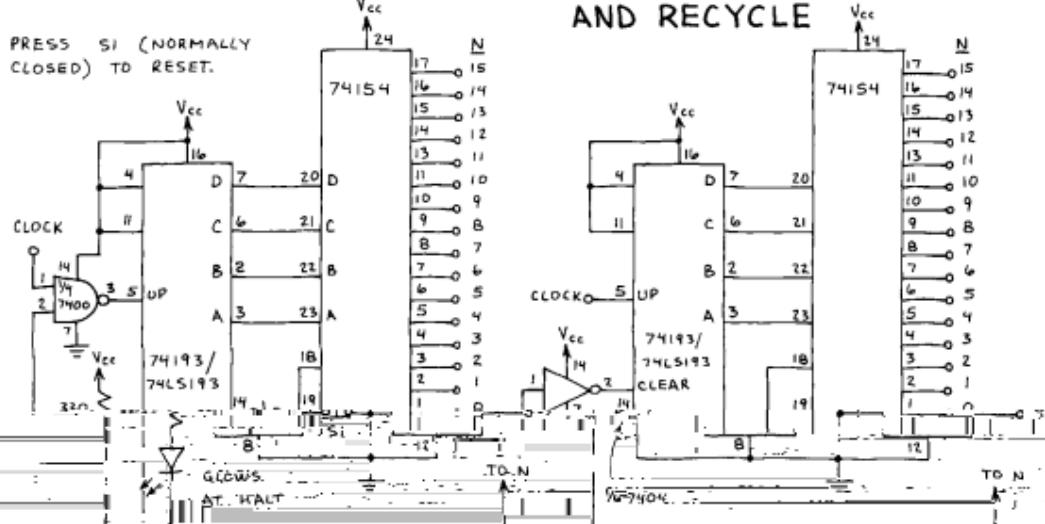


COUNT UP TO N AND RECYCLE

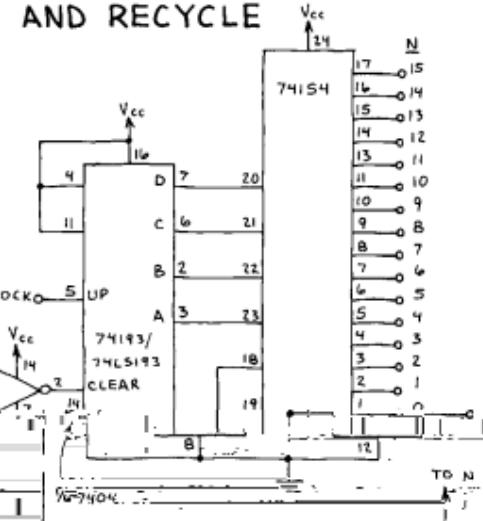

QUAD D FLIP-FLOP


74LS175

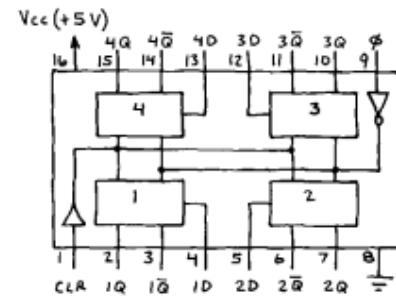HANDY PACKAGE OF FOUR D-TYPE FLIP-FLOPS. DATA AT D-INPUTS IS LOADED WHEN CLOCK GOES HIGH. MAKING CLEAR INPUT LOW MAKES ALL Q OUTPUTS LOW AND \bar{Q} OUTPUTS HIGH.




4-BIT DATA REGISTER

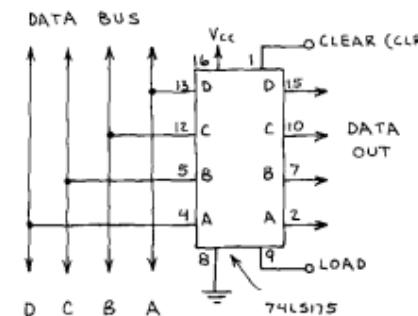
DATA ON BUS IS LOADED INTO 74LS175 WHEN LOAD INPUT GOES HIGH. DATA IS THEN STORED AND MADE AVAILABLE AT OUTPUTS UNTIL NEW LOAD PULSE ARRIVES.



MODULO-8 COUNTER

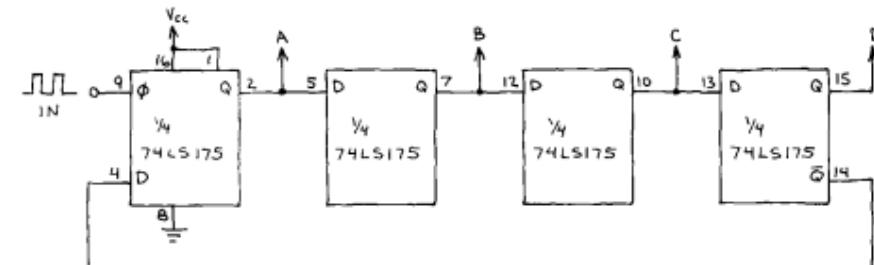


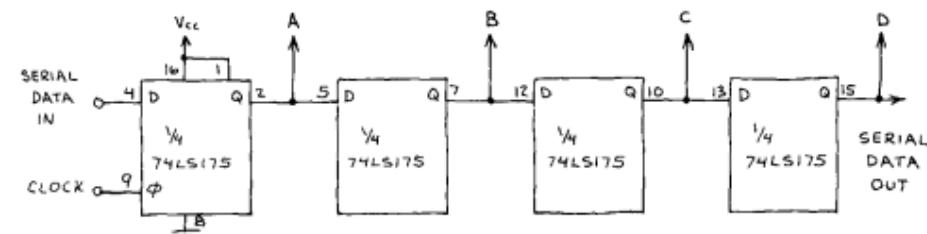SERIAL IN/OUT, PARALLEL OUT SHIFT REGISTER




BCD (DECADE) COUNTER 7490 / 74LS90

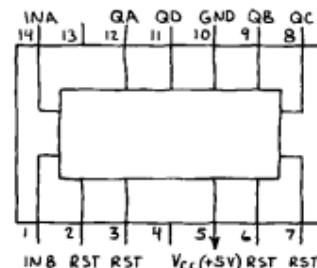
ONE OF THE MOST POPULAR DECADE COUNTERS. EASILY USED FOR DIVIDE-BY-N COUNTERS. LESS EXPENSIVE THAN MORE SOPHISTICATED COUNTERS. RST INDICATES RESET PINS. THIS CHIP IS USUALLY USED IN DECIMAL COUNTING UNITS, BUT CIRCUITS ON THIS PAGE SHOW MANY OTHER POSSIBILITIES.




DIVIDE-BY-5 COUNTER

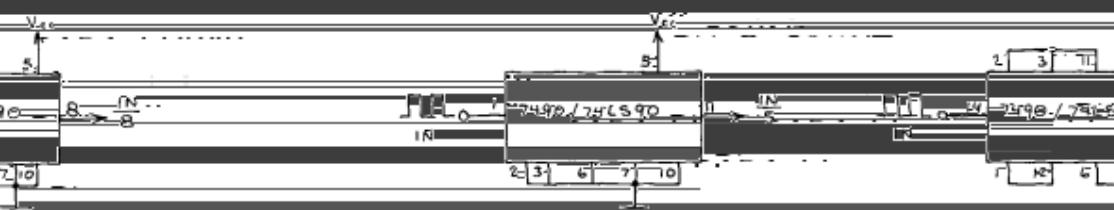

9 COUNTER

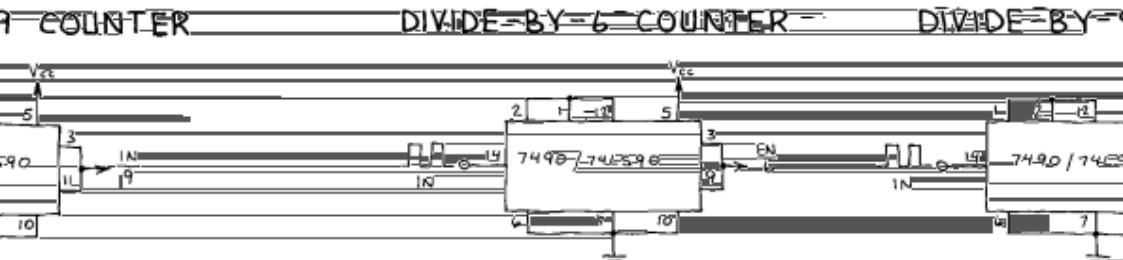


6 COUNTER

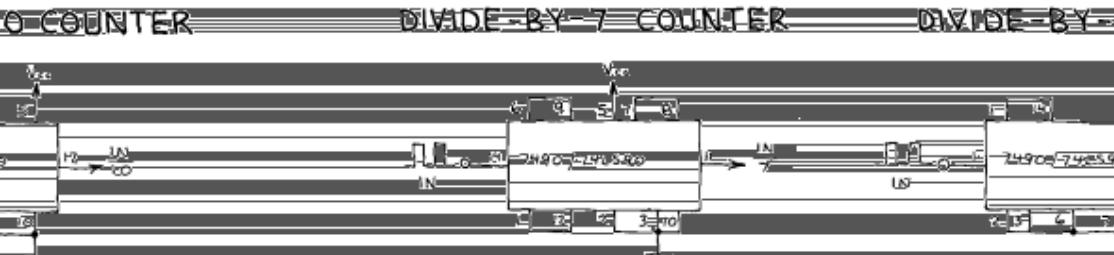


4-BIT UP COUNTER 74LS161

GENERAL PURPOSE BINARY COUNTER WITH PROGRAMMABLE INPUTS. COUNTER ACCEPTS DATA AT INPUTS WHEN LOAD INPUT GOES LOW. A LOW AT THE CLEAR INPUT RESETS THE COUNTER TO LLLL UPON THE NEXT CLOCK PULSE. P AND T ARE COUNT ENABLE INPUTS. BOTH P AND T MUST BE HIGH TO COUNT. THESE ENABLE INPUTS ARE NOT AVAILABLE WITH THE OTHERWISE MORE ADVANCED 74LS193.



8-BIT COUNTER

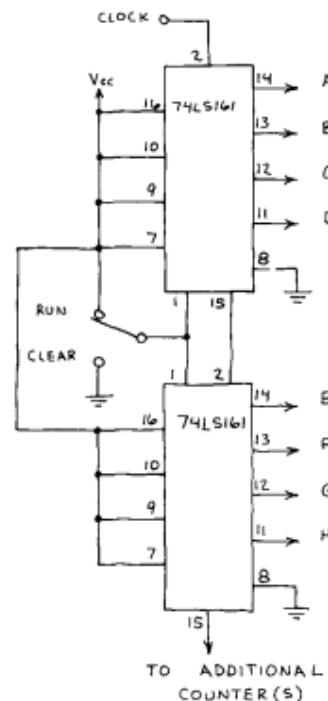

OUTPUT A IS LOWEST ORDER BIT.

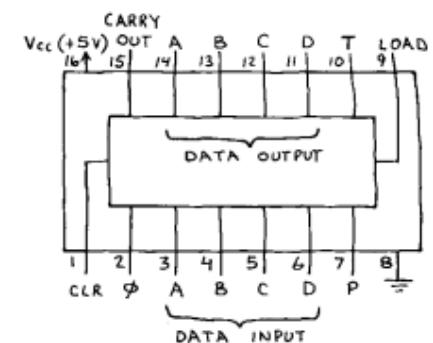

RAMP SYNTHESIZER

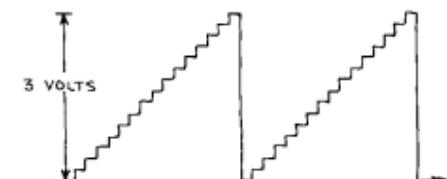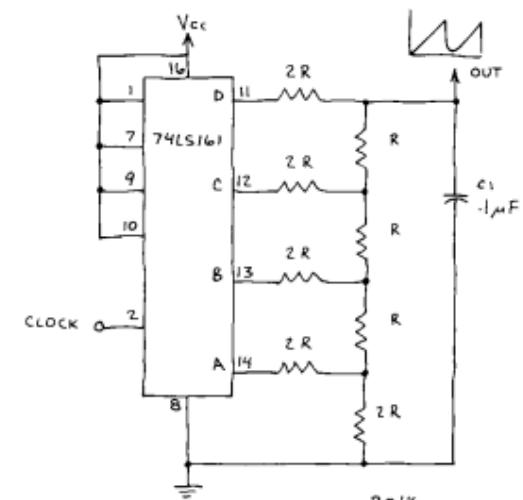


REMOVE C1 TO OBTAIN THIS STAIRCASE. FREQUENCY OF RAMP AND STAIRCASE IS $1/16$ CLOCK FREQUENCY.


BCD UP-DOWN COUNTER

74192

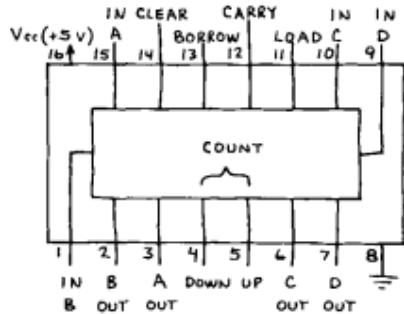FULLY PROGRAMMABLE BCD COUNTER. OPERATION IS IDENTICAL TO 74193/74LS193 EXCEPT COUNT IS 10-STEP BCD (LLLL-HLLH) INSTEAD OF 16-STEP BINARY. MANY APPLICATIONS FOR 74192/74LS192 AND 74193/74LS193 ARE INTERCHANGEABLE.




CASCADED COUNTERS

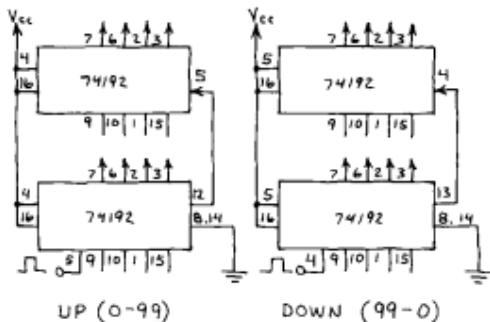


UP (0-99)

DOWN (99-0)

SINGLE UP-DOWN INPUT

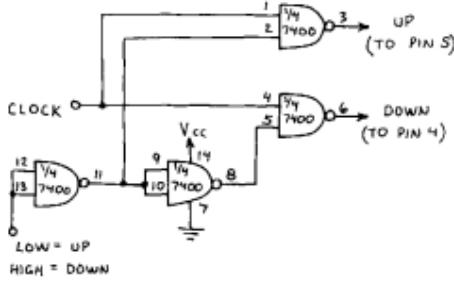

PROGRAMMABLE COUNT DOWN TIMER

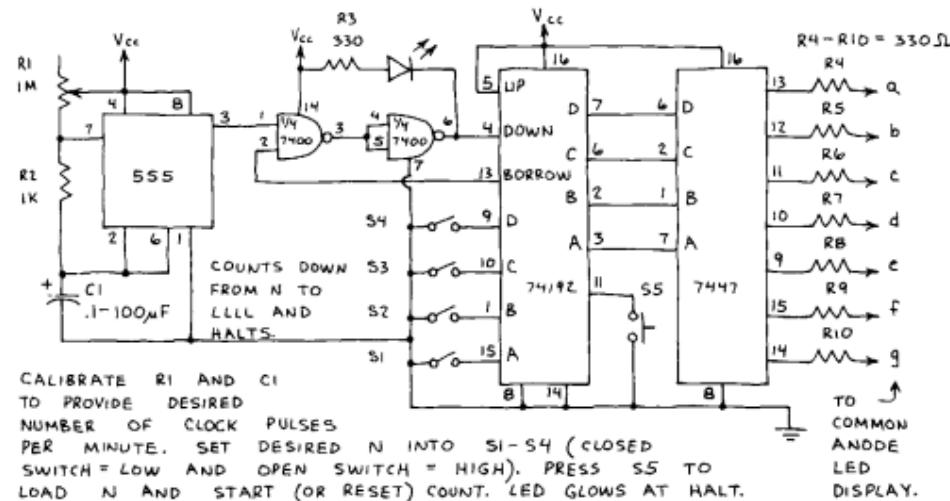


CALIBRATE RI AND CI
TO PROVIDE DESIRED
NUMBER OF CLOCK PULSES

PER MINUTE. SET DESIRED N INTO SI-S4 (CLOSED
SWITCH = LOW AND OPEN SWITCH = HIGH). PRESS S5 TO
LOAD N AND START (OR RESET) COUNT. LED GLOWS AT HALT.


BCD (DECADE) COUNTER

74LS196

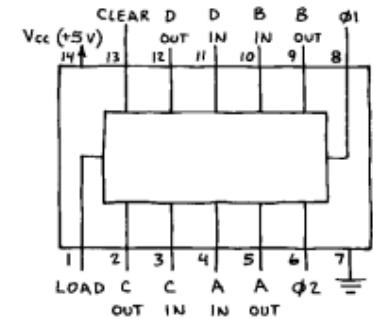
MORE SOPHISTICATED VERSION OF THE POPULAR 7490/74LS90 BCD COUNTER. INCLUDES 4-PRESET INPUTS WHICH PERMIT ANY BCD NUMBER TO BE LOADED WHEN PIN 1 IS MADE LOW. THE COUNTER IS CLEARED TO LLLL WHEN PIN 13 IS MADE LOW. φ INDICATES CLOCK INPUT.



DECADE COUNTER

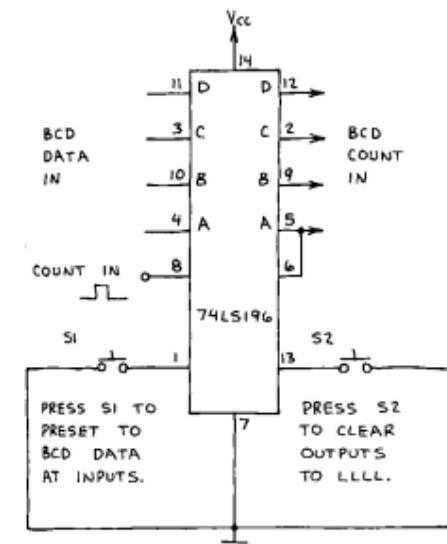


4-BIT LATCH

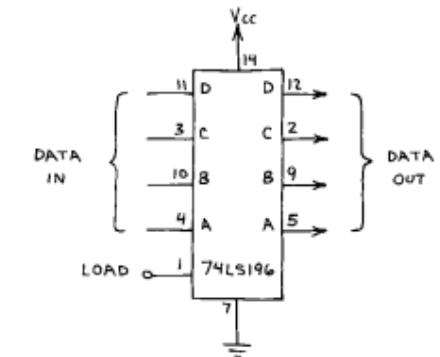


WHEN LOAD INPUT IS LOW,
OUTPUTS FOLLOW INPUTS. NO
CHANGE WHEN LOAD INPUT
IS HIGH. NOTE THAT A PAIR
OF 74LS196'S CAN BE USED
IN A DECIMAL COUNTING
UNIT (COUNTER PLUS REGISTER).

DIVIDE-BY-5 COUNTER

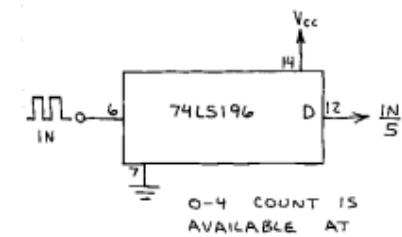


DIVIDE-BY-10 COUNTER

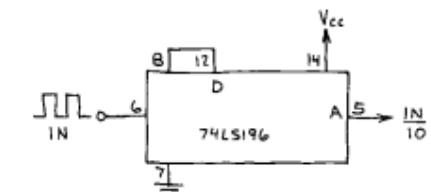


DIVIDE-BY-12 BINARY COUNTER

7492

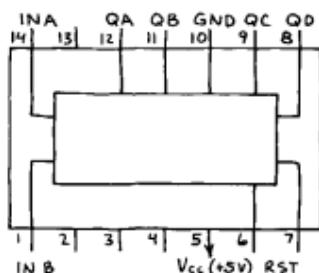
OFTEN USED TO DIVIDE CONDITIONED 60 HZ PULSES FROM AC POWER LINE INTO 10 HZ PULSES. OTHER DIVIDER APPLICATIONS ALSO. RST INDICATES RESET PINS.




DIVIDE-BY-7 COUNTER

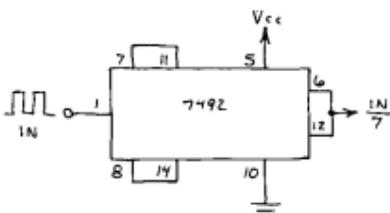


DIVIDE-BY-12 COUNTER

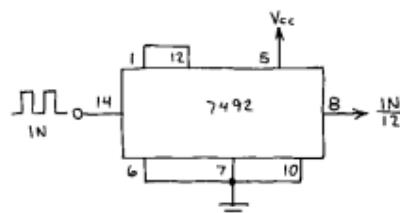


DIVIDE-BY-9 COUNTER

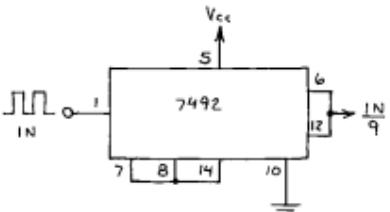

10-HZ PULSE SOURCE

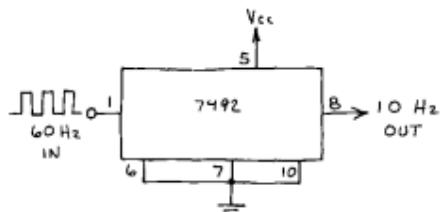


DIVIDE-BY-120 COUNTER

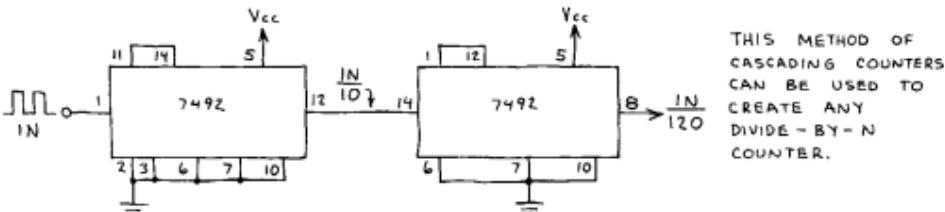


4-BIT (BINARY) COUNTER

7493 / 74LS93

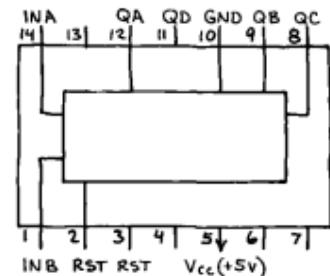
EASY TO USE 4-BIT BINARY COUNTER. LESS EXPENSIVE THAN MORE SOPHISTICATED COUNTERS. RST INDICATES RESET PINS. NOTE UNUSUAL LOCATION OF POWER SUPPLY PINS.




DIVIDE-BY-10 COUNTER

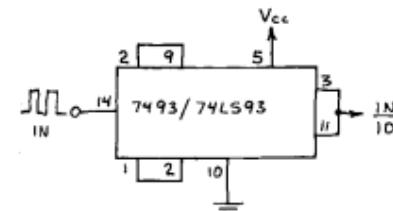


DIVIDE-BY-12 COUNTER

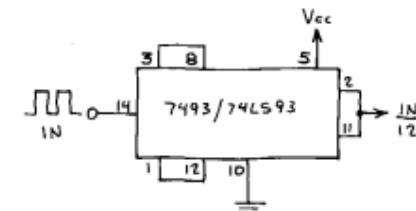


DIVIDE-BY-11 COUNTER

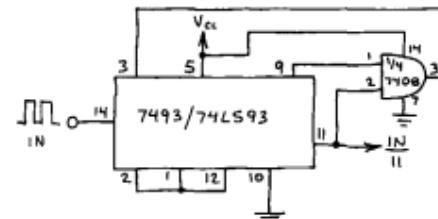

DIVIDE-BY-16 COUNTER

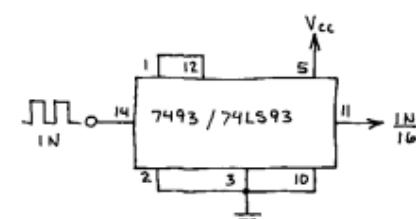

4-BIT BINARY COUNTER

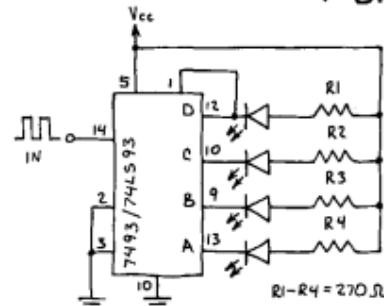

COUNTS FROM 0-15 IN BINARY AND RECYCLES. GLOWING LED = L (0); OFF LED = H (1). 555 TIMER IC MAKES GOOD INPUT CLOCK.

TRUTH TABLE	DCBA	DCBA
L L L L	L	H L L L
L L L H	L	H L L H
L L H L	L	H L H L
L L H H	L	H L H H
L H L L	L	H H L L
L H L H	L	H H L H
L H H L	L	H H H L
L H H H	L	H H H H